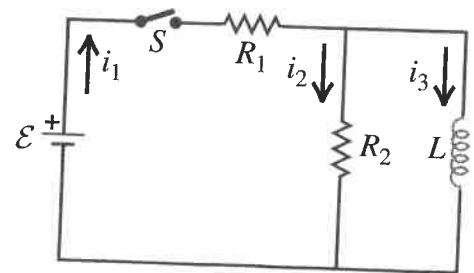


30.35 • L-C Oscillations. A capacitor with capacitance $6.00 \times 10^{-5} \text{ F}$ is charged by connecting it to a 12.0-V battery. The capacitor is disconnected from the battery and connected across an inductor with $L = 1.50 \text{ H}$. (a) What are the angular frequency ω of the electrical oscillations and the period of these oscillations (the time for one oscillation)? (b) What is the initial charge on the capacitor? (c) How much energy is initially stored in the capacitor? (d) What is the charge on the capacitor 0.0230 s after the connection to the inductor is made? Interpret the sign of your answer. (e) At the time given in part (d), what is the current in the inductor? Interpret the sign of your answer. (f) At the time given in part (d), how much electrical energy is stored in the capacitor and how much is stored in the inductor?

30.52 ••• CALC An inductor with inductance $L = 0.200 \text{ H}$ and negligible resistance is connected to a battery, a switch S , and two resistors, $R_1 = 8.00 \Omega$ and $R_2 = 6.00 \Omega$ (Fig. P30.52). The battery has emf 48.0 V and negligible internal resistance.

Figure P30.52




S is closed at $t = 0$. (a) What are the currents i_1 , i_2 , and i_3 just after S is closed? (b) What are i_1 , i_2 , and i_3 after S has been closed a long time? (c) Apply Kirchhoff's rules to the circuit and obtain a differential equation for $i_3(t)$. Integrate this equation to obtain an equation for i_3 as a function of the time t that has elapsed since S was closed. (d) Use the equation that you derived in part (c) to calculate the value of t for which i_3 has half of the final value that you calculated in part (b). (e) When i_3 has half of its final value, what are i_1 and i_2 ?

30.41 • For the circuit of Fig. 30.17, let $C = 15.0 \text{ nF}$, $L = 22 \text{ mH}$, and $R = 75.0 \Omega$. (a) Calculate the oscillation frequency of the circuit once the capacitor has been charged and the switch has been connected to point a . (b) How long will it take for the amplitude of the oscillation to decay to 10.0% of its original value? (c) What value of R would result in a critically damped circuit?

30.59 •• CP In the circuit shown in **Fig. P30.59**, switch S is closed at time $t = 0$ with no charge initially on the capacitor. (a) Find the reading of each ammeter and each voltmeter just after S is closed. (b) Find the reading of each meter after a long time has elapsed. (c) Find the maximum charge on the capacitor. (d) Draw a qualitative graph of the reading of voltmeter V_2 as a function of time.

Figure **P30.59**

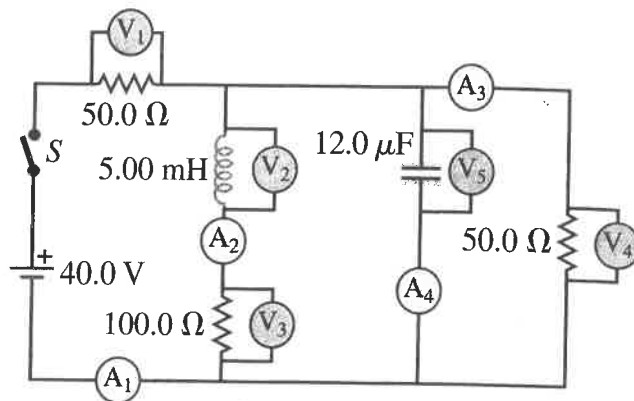

30.65 •• CP In the circuit shown in **Fig. P30.65**, switch S is closed at time $t = 0$. (a) Find the reading of each meter just after S is closed. (b) What does each meter read long after S is closed?

Figure **P30.65**

