

31.18 •• A resistor with $R = 300 \Omega$ and an inductor are connected in series across an ac source that has voltage amplitude 500 V. The rate at which electrical energy is dissipated in the resistor is 286 W. What is (a) the impedance Z of the circuit; (b) the amplitude of the voltage across the inductor; (c) the power factor?

31.23 • An L - R - C series circuit with $L = 0.120$ H, $R = 240 \Omega$, and $C = 7.30 \mu\text{F}$ carries an rms current of 0.450 A with a frequency of 400 Hz. (a) What are the phase angle and power factor for this circuit? (b) What is the impedance of the circuit? (c) What is the rms voltage of the source? (d) What average power is delivered by the source? (e) What is the average rate at which electrical energy is converted to thermal energy in the resistor? (f) What is the average rate at which electrical energy is dissipated (converted to other forms) in the capacitor? (g) In the inductor?

31.32 • In an L - R - C series circuit, $R = 400 \Omega$, $L = 0.350$ H, and $C = 0.0120 \mu\text{F}$. (a) What is the resonance angular frequency of the circuit? (b) The capacitor can withstand a peak voltage of 670 V. If the voltage source operates at the resonance frequency, what maximum voltage amplitude can it have if the maximum capacitor voltage is not exceeded?

31.44 • A large electromagnetic coil is connected to a 120-Hz ac source. The coil has resistance 400Ω , and at this source frequency the coil has inductive reactance 250Ω . (a) What is the inductance of the coil? (b) What must the rms voltage of the source be if the coil is to consume an average electrical power of 450 W?