

TT → algebra: minterm, maxterm, Karnaugh Map, Look (SOP) (POS)

Eg: half-adder

A	B	C	Σ
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

simple look should show: $\Sigma = A \oplus B$
 $C = A \cdot B$


minterms: look at 1's - write as product
 eg $C = A \cdot B$ $\Sigma = \bar{A}B + A\bar{B}$

maxterms - look at 0's (ie $\bar{1}$)

write $\bar{\Sigma} = \bar{A} \cdot \bar{B} + A \cdot B \Rightarrow \Sigma = \overline{\bar{\Sigma}} = \overline{\bar{A} \cdot \bar{B} + A \cdot B}$
 $= (A + B) \cdot (\bar{A} + \bar{B})$ "Factored"

Full-adder (includes input of carry in = C_{in})

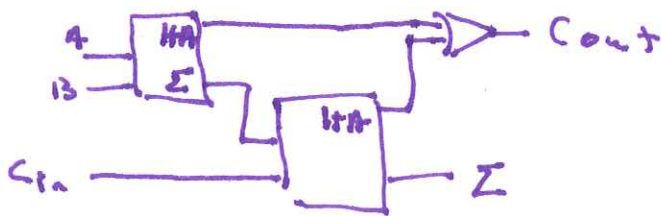Note can build full adder from 2 half-adders (H/A)



Note: building circuits from existing blocks (rather than going back to gates) is a good idea!

A	B	C_{in}	C_{out}	Σ
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

maxterm:

$$\bar{\Sigma} = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}\bar{C} + A\bar{B}C$$

$$\Sigma = (A+B+C) \cdot (A+\bar{B}+\bar{C}) \cdot (\bar{A}+B+\bar{C}) \cdot (\bar{A}+\bar{B}+C)$$

minterm


$$\Sigma = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

minterm = $\bar{A}\bar{B}C + A\bar{B}\bar{C} + A\bar{B}C + ABC$

maxterm: $\bar{C}_{out} = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C}$

$$C_{out} = (A+B+C) \cdot (A+B+\bar{C}) \cdot (A+\bar{B}+C) \cdot (\bar{A}+B+C)$$

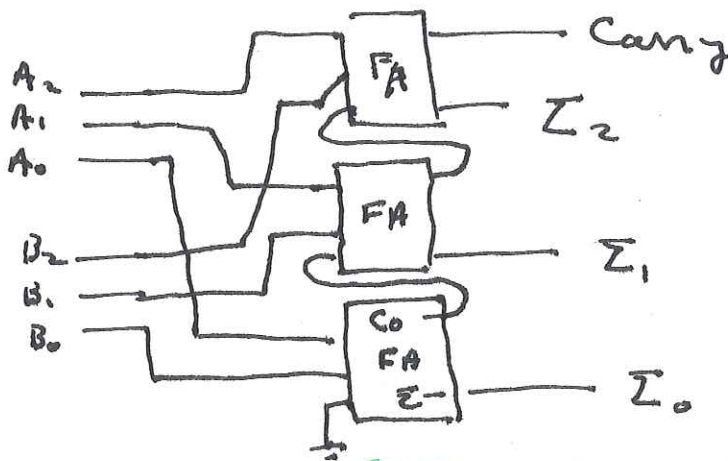Note: can strung together several full adders (FA) to add multi-bit parallel binary numbers



Again: building complex circuits using existing blocks is a good idea

∴ zero carry in for first bit

Karnaugh Maps: A 2d array of 0, 1, X (don't care)


Rows & Columns label via Gray code (change just one bit at a time: 00, 01, 11, 10)

Circle blocks of 2^N 1s & Xs until every 1 covered. The bigger the blocks the better.

Eg: A segment of seven segment display



A	B	C	D	a
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
above				X

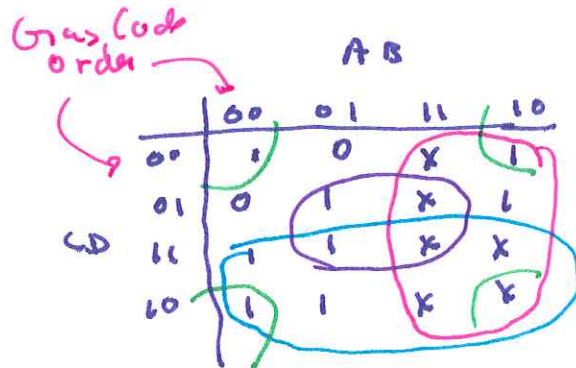

$$\overline{B}\overline{D} + A + C + DB$$

Remark: $\overline{B}\overline{D} + BD = \overline{B \oplus D}$
for which an IC exists

$$\overline{a} = \overline{A}\overline{B}\overline{C}D + \overline{A}\overline{B}C\overline{D}$$

$$a = (A+B+C+D)(A+B+\overline{C}+\overline{D}) \leftarrow \text{max term}$$

K-map For Full Adder Cout

		AB			
		00	01	11	10
Cin	0	0	0	1	0
	1	0	1	1	1

$$C_{in} A + A B + C_{in} B$$

Are the number of letters in the words 0-9 even?
 True for 0, 4, 5, 9; X for 11-15

		BA			
		00	01	11	10
DC	00	1	0	0	0
	01	1	1	0	0
	11	X	X	X	Y
	10	0	1	X	Y


$$D A + C \bar{B} + \bar{A} \bar{B} \bar{D}$$

Eg segment b of seven segment

ABCD

		AB			
		00	01	11	10
CD	00	1	1	X	1
	01	1	0	X	1
	11	1	1	X	X
	10	1	0	X	X

$$\bar{B} + CD + \bar{C} \bar{D}$$



 always ON except for 5 & 6