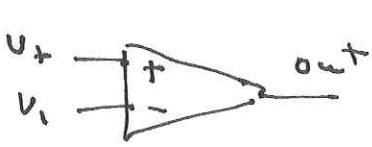



Digital meets Analog: Comparator (311)  
 $0 \leq 1$  voltages that are any real number.



if  $V_+ > V_-$  then out = High  
 if  $V_+ < V_-$  then out = Low

Note: like all the chips we've been using, comparator requires power connects (which we often don't bother to show in our diagrams) - often  $\pm 15V$

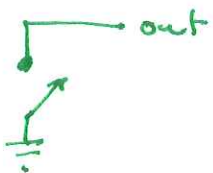
Note: the 311 (and many comparators) is an open collector device - meaning its "output" is effectively either a connection to ground or a disconnect



"High" state means a disconnect


"Low" means a closed switch to ground

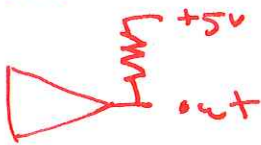In typical usage we would need a "pull up" resistor connected to the output




Often I will ignore this also in diagrams and pretend 311 output is +5V or 0V



### Basic Circuits

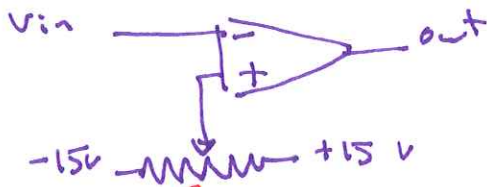

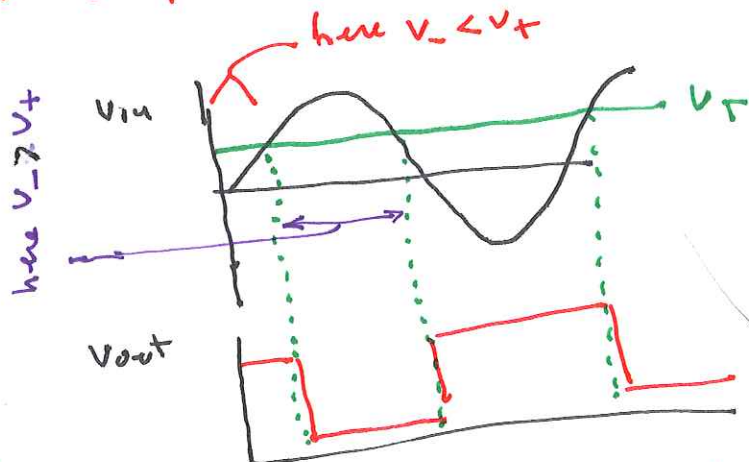
adjust pot for desired transition voltage =  $V_T$



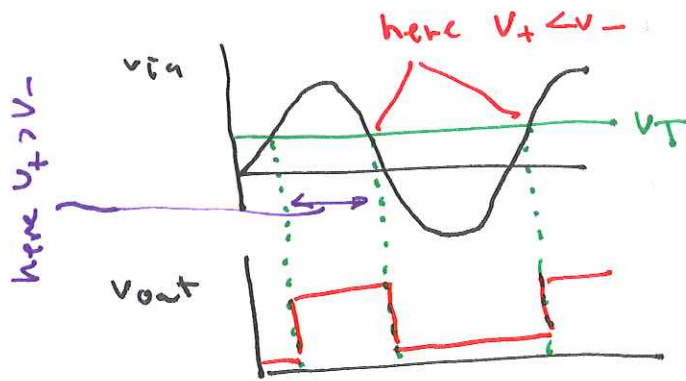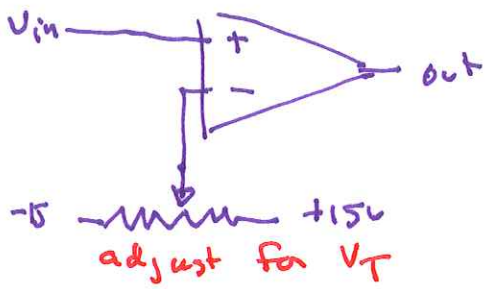note: inversion:  $v_{out}$  high where  $v_{in}$  below  $V_T$



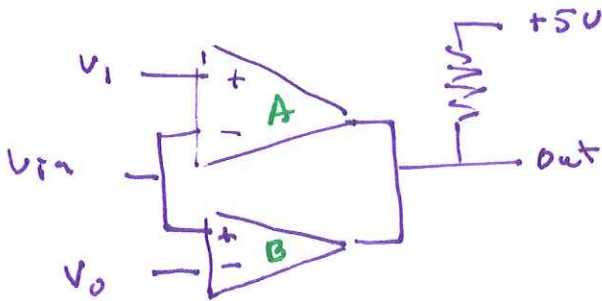"window" circuit: if  $V_0 < V_{in} < V_1$  then out = High  
 otherwise out = Low



if  $V_{in} > V_1$  then A out put to GND


if  $V_{in} < V_0$  then B out put to GND

Note: if either output connected to ground output IS GND

if  $V_0 < V_{in} < V_1$  then A output unconnected } result  
 B output unconnected } High


Note: "Multi Channel Analyzer" MCA: a stack of such window circuits such that exactly one window will be satisfied by any signal with outputs connected to counters — count the # pulses in each window display result as graphs

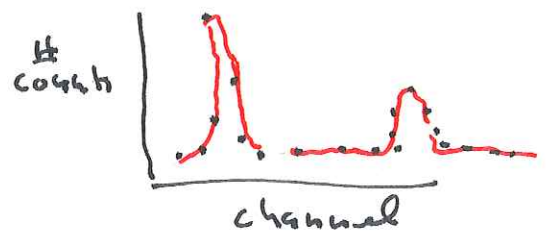often channel # relates to some physical quantity (like photon energy) and the result is called a spectrum.




connect the det

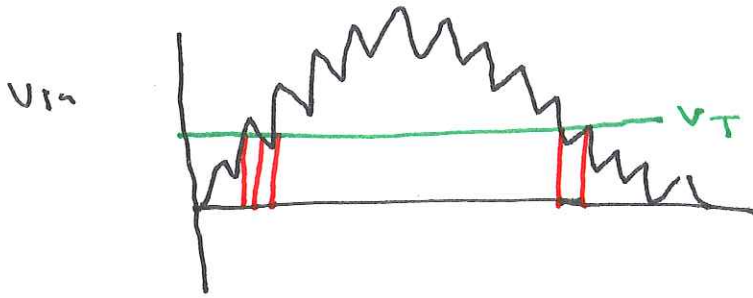Important Problem (and its solution) - analog signals usually come with "noise" - random variations




Noise results in multiple transitions whereas "real" signal has just one.

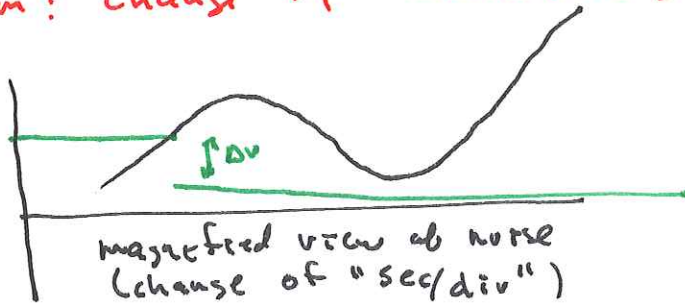
Solution: change  $V_T$  immediately following a transition



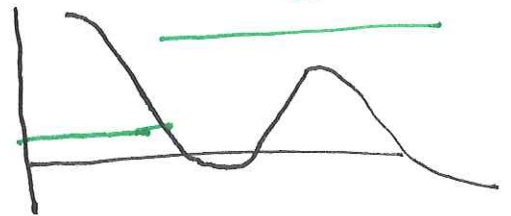
transition voltage level changes and changes back



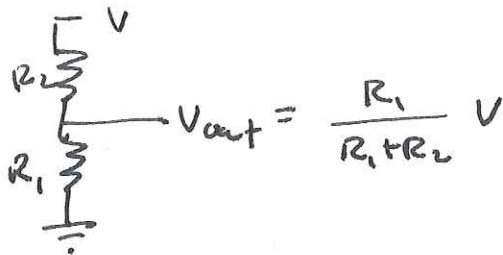
Circuit analysis based on basic voltage divider eg:



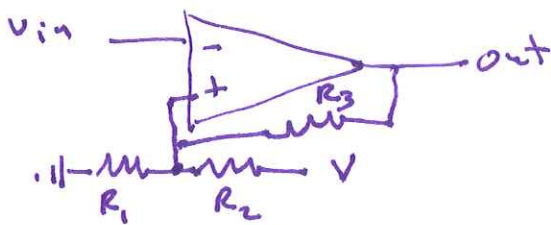Note: this very important equation assumes  $V_{out}$  draws a small fraction of the current flowing thru  $R_1$  &  $R_2$  - i.e. we assume  $R_1$  &  $R_2$  face exactly the same current




if  $V_{in} > V_T$  out is Low & circuit

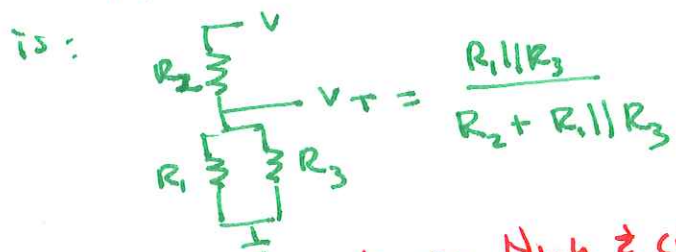

Notation:  $R_x \parallel R_y$  refers to parallel combo of  $R_x$  &  $R_y$  i.e.

$$R_x \parallel R_y = \frac{R_x R_y}{R_x + R_y}$$

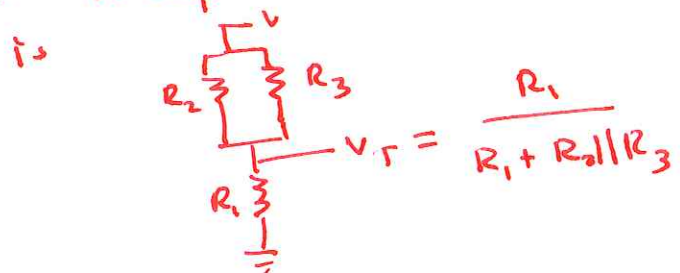if  $V_{in} < V_T$  out is High & circuit





Some algebra:

$$V_T = \frac{R_1 \parallel R_3}{R_2 + R_1 \parallel R_3} = \frac{\frac{R_1 R_3}{R_1 + R_3}}{R_2 + \frac{R_1 R_3}{R_1 + R_3}} = \frac{R_1 R_3}{R_2 R_1 + R_2 R_3 + R_1 R_3}$$

$$(-) \quad V_T = \frac{R_1}{R_1 + R_2 \parallel R_3} = \frac{R_1}{R_1 + \frac{R_2 R_3}{R_2 + R_3}} = \frac{R_1 (R_2 + R_3)}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

$$\Delta V = V_T - V_T = \frac{R_1 R_2}{R_1 R_2 + R_1 R_3 + R_2 R_3} = \frac{R_1 R_2 / (R_1 R_2)}{\frac{R_1 R_2}{R_1 + R_2} + R_3} = \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_3}$$

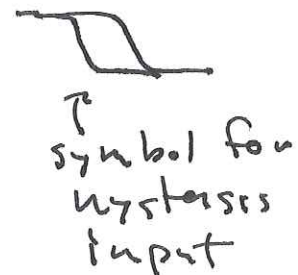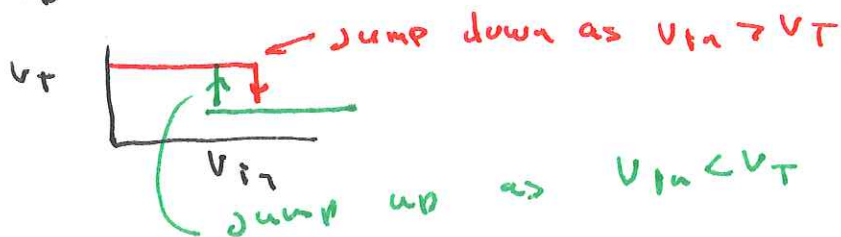Remark: the current value of  $V_T$  depends on the history of the circuit "hysteresis"  
graph of  $V_T$  vs  $V_{in}$ :



Design: the basic  $V_T$  is set by voltage divider

$$\frac{R_1}{R_2 + R_1} V = \frac{R_1 \parallel R_2}{R_2} V \quad \text{so} \quad R_2 + V_T \rightarrow R_1 \parallel R_2$$

$$\Delta V \propto R_1 \parallel R_2 \rightarrow R_3$$

$$R_2 \propto R_1 \parallel R_2 \rightarrow R_1$$