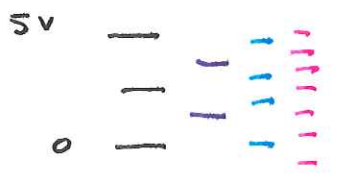



Successive Approximation ADC: Play 20 questions with  $V_{in}$  ... Is  $V_{in}$  more than  $\frac{5V}{2}$ ? if yes MSB is 1, otherwise 0.

is  $V_{in}$  more than  $\frac{3}{4}5V$ ? if yes next bit also 1 otherwise 0.   
 is  $V_{in}$  more than  $\frac{7}{8}5V$ ? if yes next bit is 1.   
 is  $V_{in}$  more than  $\frac{5}{8}5V$ ?



answer to each question gives next bit of approx digital value

Note: in below A is MSB; H to LSB

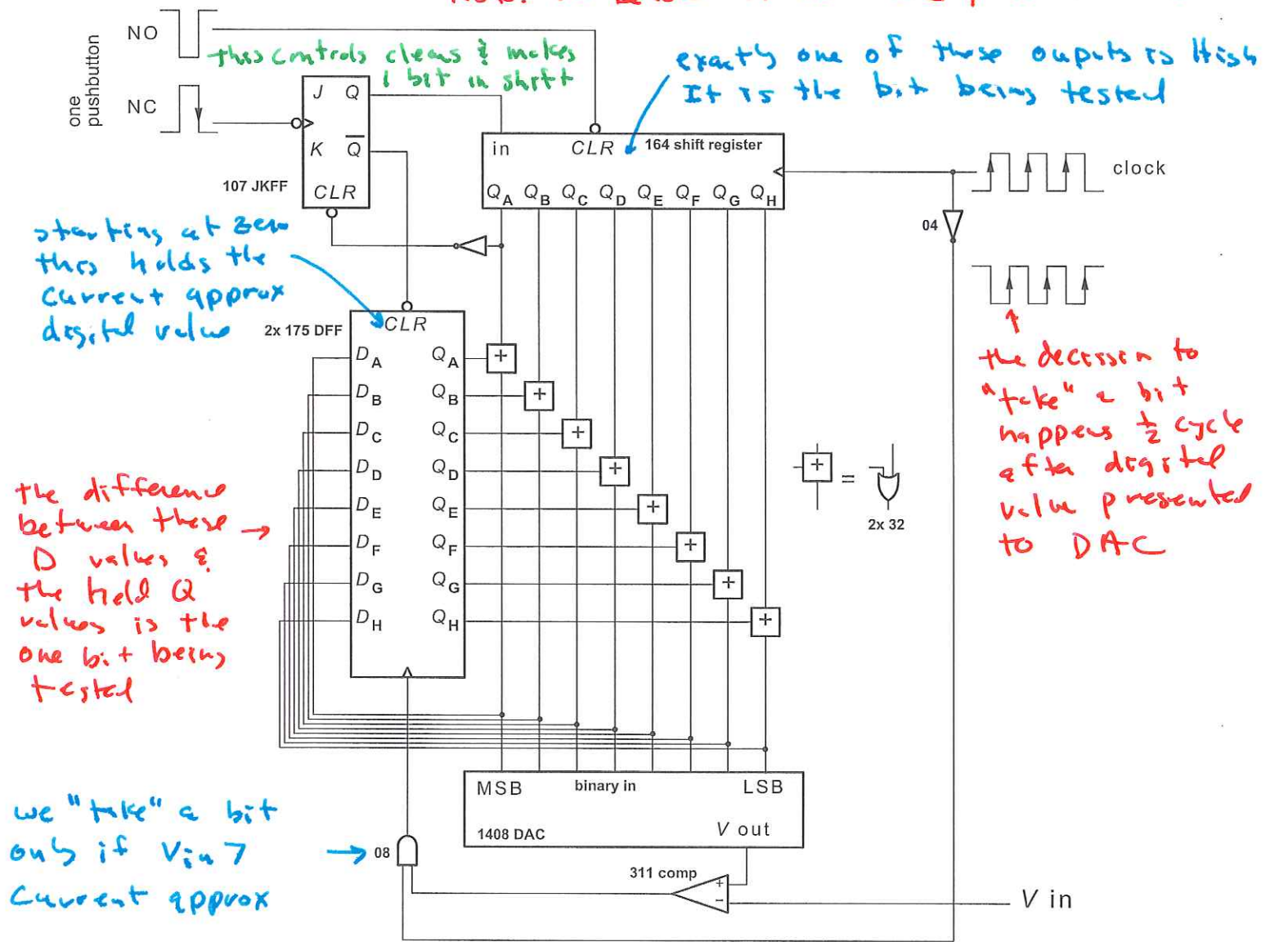

one pushbutton NO NC

this controls clears & makes 1 bit in shift

exactly one of these outputs is high. It is the bit being tested

starting at zero this holds the current approx digital value

the difference between these D values & the held Q values is the one bit being tested


we "take" a bit only if  $V_{in} >$  current approx

the decrease to "take" a bit happens  $\frac{1}{2}$  cycle after digital value presented to DAC

Note: in actual circuit 1408 DAC produces a negative voltage output. If thinking of positive DAC outputs reverse +- on comparator


Single slope APC:  $V_{in} \rightarrow$  time (measure with period meter)

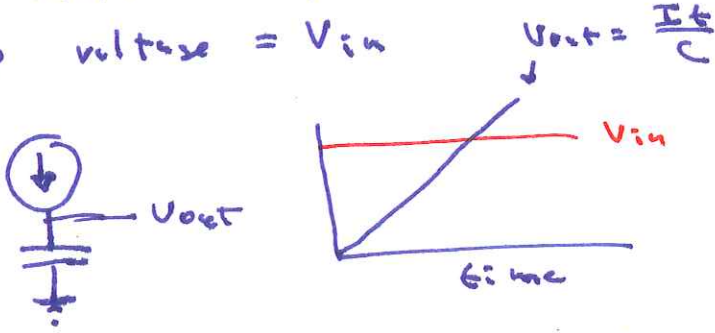plan: make a upward ramp voltage & time when ramp voltage =  $V_{in}$




time how long it takes  $V_{out} = V_{in}$  with capacitor & period meter

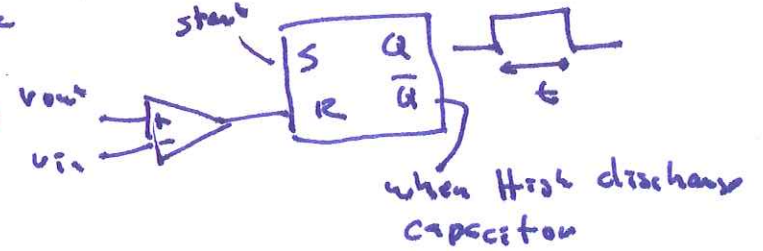
Note:  $V_{in}$  &  $t$  but proportionally constant depends on  $C$  [bad]



Dual Slope (common in DMM)

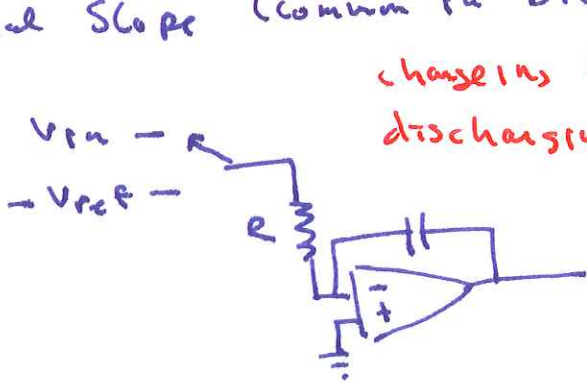

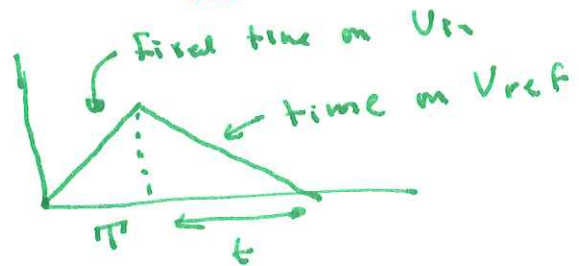charging current =  $\frac{V_{in}}{R}$   
 discharging current =  $\frac{V_{ref}}{R}$  } same total charge on/off



Remark: How do old needle meters work? The needle is attached to a coil of wire in a magnetic field Force (& hence torque) on coil proportional to current needle attached to torsional spring with torque & angle so  $I \propto$  torque  $\propto$  angle. Note: this is designed to work with small currents so most of current goes thru a lower resistance shunt

$$Q = \frac{V_{in}}{R} T = \frac{V_{ref}}{R} t$$

$$V_{in} = V_{ref} \frac{t}{T} \leftarrow \text{does not depend on } R \text{ or } C$$



To measure voltage:  $(V) =$   $\uparrow$  large R

current thru  $(A) = \frac{\Delta V}{R}$

Note: see that  $(V) =$  high resistance,  $(A) =$  low resistance.


New topic: Transducers

photo multiplier tube (single photon detection) "PM"

photoelectric effect: 1 photon  $\Rightarrow$  1  $e^-$ . Accelerate  $e^-$

so when slams into plate many electrons emitted

(electron "multiplication")

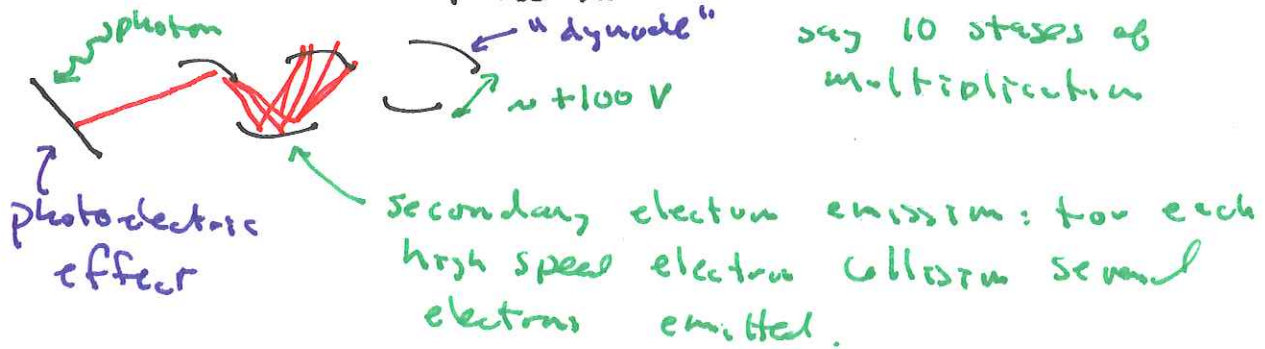

Net result: 1 photon in,  $10^8 - 10^9$  electrons out - enough to measure "pulse" out

Aim: Spend this week talking about how to convert physical quantities (light, pressure, temperature...) into electrical quantities (voltage, current, frequency...)