

Gates, algebra, truth table, TTL IC

AND




$$A \cdot B = \text{out}$$

| A | B | out |
|---|---|-----|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

quad AND = 7408

OR

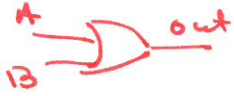

$$A + B = \text{out}$$

| A | B | out |
|---|---|-----|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

quad OR = 7432

INVERT



$$\bar{A} = \text{out}$$

| A | out |
|---|-----|
| 0 | 1 |
| 1 | 0 |

hex INVERT = 7404

BUFFER



$$A = \text{out}$$

| A | out |
|---|-----|
| 0 | 0 |
| 1 | 1 |

hex BUFFER = 74365

XOR



$$A \oplus B = \text{out}$$

| A | B | out |
|---|---|-----|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

quad XOR = 7486

NAND



$$\overline{A \cdot B}$$

| A | B | out |
|---|---|-----|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

quad NAND = 7400

NOR



$$\overline{A + B}$$

| A | B | out |
|---|---|-----|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

quad NOR = 7402

XNOR




$$\overline{A \oplus B}$$

| A | B | out |
|---|---|-----|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

quad XNOR = 74266

Note: combine: e.g.

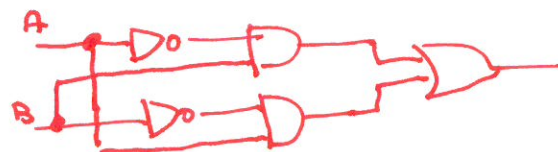

$$A \cdot \bar{B} + \bar{A} \cdot B = A \oplus B$$

