

We've been considering the case of Analog meets Digital: The universe is analog (pressure, temperature, voltage, mass etc are real numbers) but the sort of circuits we've been doing only know about 0 & 1. Certainly we can use 0s & 1s to represent real numbers ("floating point numbers") or use integers to approximate real numbers. How do we get those analog quantities into our digital circuits? How do we get our digital circuits to produce such numbers? So far we've looked at Comparators which make simple above/below cut on real number inputs, now lets make integer approximations of real numbers:

Analog to Digital Converter  
ADC

Voltage in  $\rightarrow$  Integer out  
Integer in  $\rightarrow$  Voltage out


Digital to Analog Converter  
DAC

### Digital to Analog Converters (DAC)


$\rightarrow$  Begin with an "Op Amp" (operational amplifier) which will be the star of analog electronics

#### Op Amp Rules:

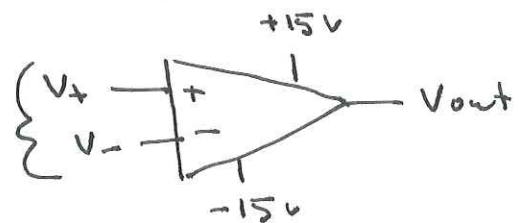- 1)  $V_+$  &  $V_-$  do not eat current
- 2)  $V_+ \approx V_-$  if operating correctly  
[  $V_{out} = 10^7 (V_+ - V_-)$  but with  $\pm 15V$  supplies  $V_+ - V_-$  is limited to  $\leq 1.5 \mu V$  ]




Basic Circuit:

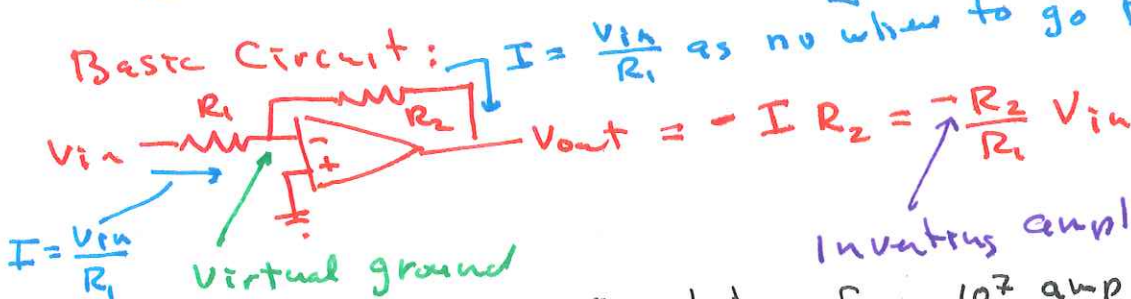

Inverting amplifier

Q: what go from  $10^7$  amp to  $\frac{R_2}{R_1}$ ?  
A: wait for analog course.

## Basic DAC circuit:

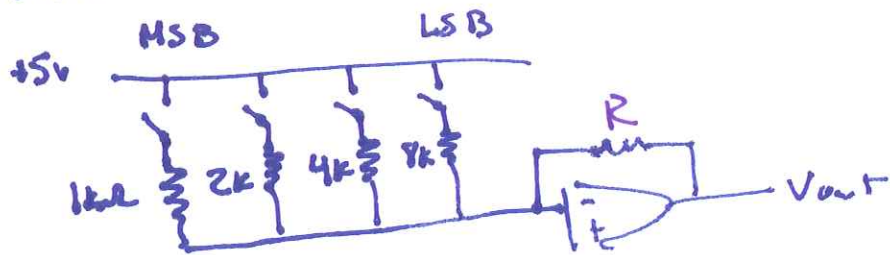

the (in this case) 4 bit binary number closes or opens switches to +5V. If closed the current  $\frac{5V}{R}$  flows towards virtual ground and then around thru R producing  $V_{out} = -R I_{total}$

$$I_{total} = \frac{5V}{1k\Omega} \left( D + \frac{1}{2} C + \frac{1}{4} B + \frac{1}{8} A \right)$$

CMOS

Note: TTL controlled "switches" = transmission gate aka analog switch

Note 2: Not perfect switch - few  $\Omega$  resistance; may not be bipolar


Note 3: This circuit has problems as precision resistors are expensive


Note: Example: CD audio is stereo (2 channels) of 16 bits @ 44.1 kHz

↳ ie 64K → 15 ppm accurate resistor required

Tricky solution - use lots of resistors that are identical but not of any precise value.


R-2R Ladder:

use:   
2 R resistors in series

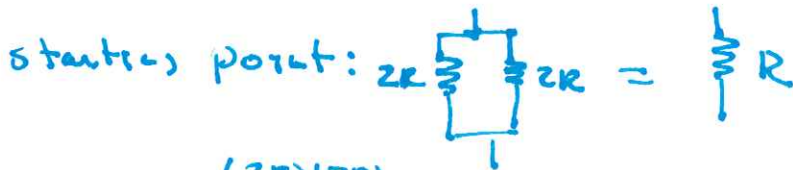
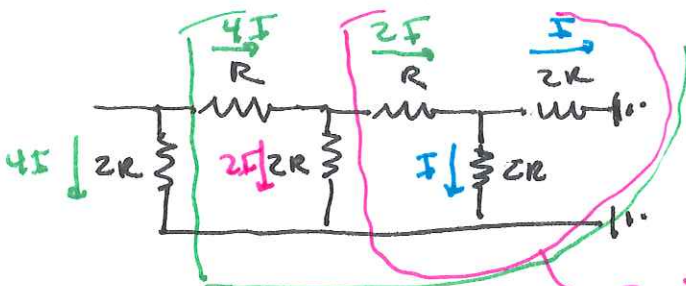
$$\text{as } \frac{(2R)(2R)}{(2R) + (2R)} = R$$






I: same volts same  $2R \Rightarrow$  same current

2I: current in = current out

is equivalent to  $2R$  so  $2I$  goes right must mean  $2I$  goes down

is equivalent to  $2R$  so  $4I$  goes right must mean  $4I$  goes down

Result: A system that produces currents exactly  $2^N I$  from identical but not precise  $R$ s. (Note: exact value of  $I$  will dependant on  $R$ , thus the proportional constant between (digital in) & (voltage out) is not accurately known, but the proportionality between (digital in) & (voltage out) should be accurate — i.e. Fit between (voltage out) & (digital in) should be accurately linear but the slope is only approximately set.

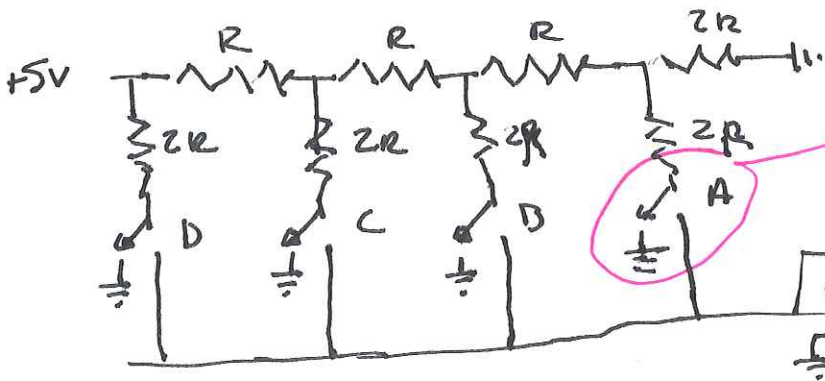


Analog switch direct current to ground on op amp according to value of digit


speed limited only by op amp

Note:  $R_0$  sets the overall scale of the output voltage and it is often an external component.

"Multiplying DAC" — 1408

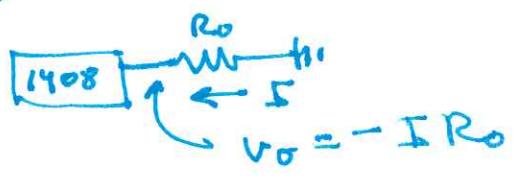

# Analogy to Digital Conversion (ADC)

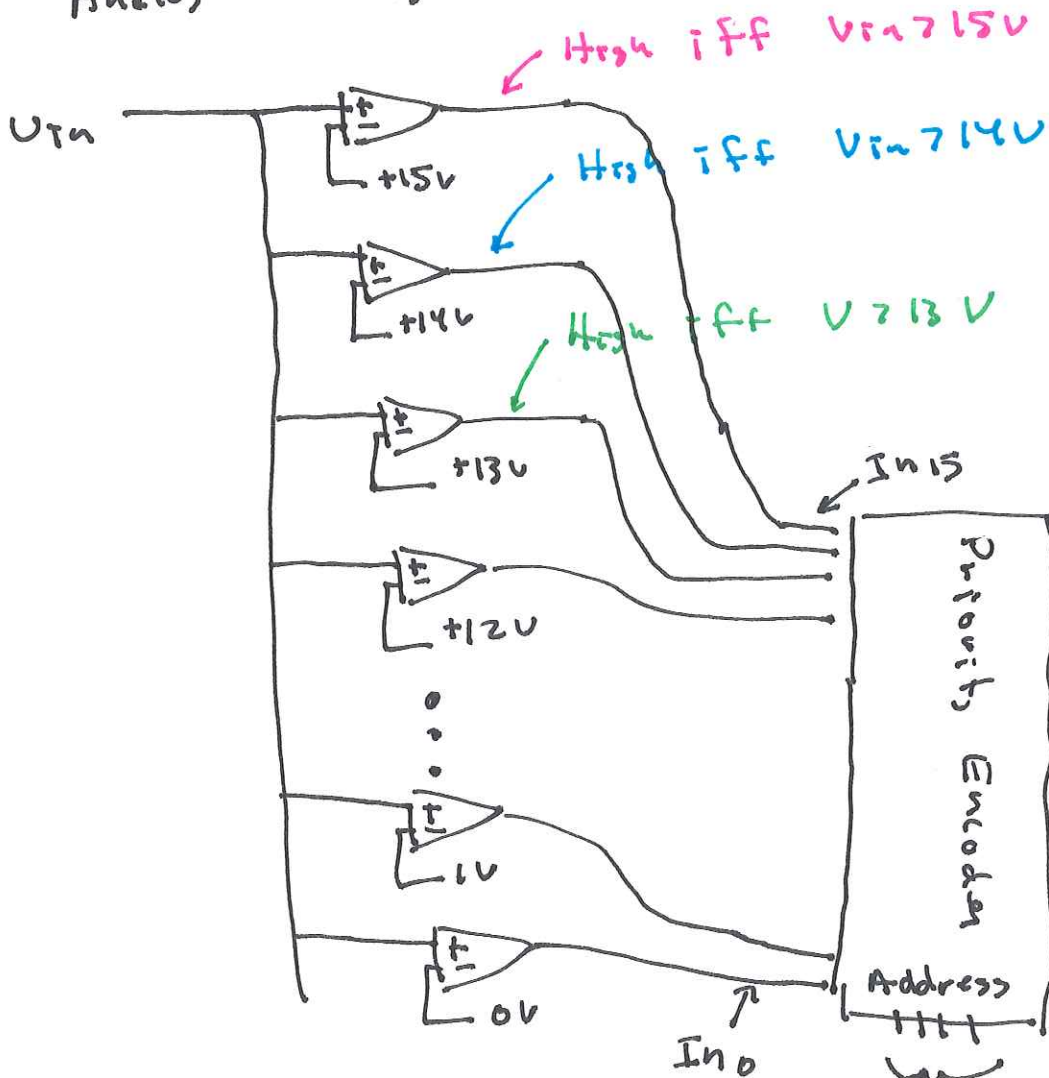


"Flash ADC"  
in Digital  
Scopes

→ another bit  
doubles the  
price.

output # of highest  
number  $I_n$  that is  
High

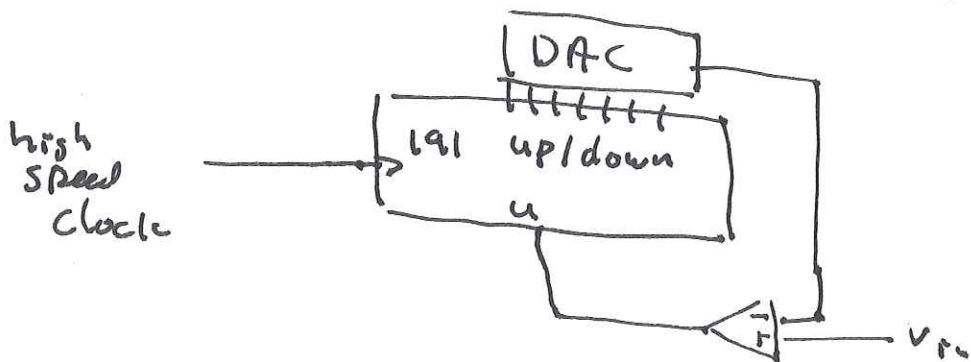slower but less expensive: use feedback & control



if the DAC's output is below  $V_{in}$ , count up  
if DAC's output above  $V_{in}$ ; count down  
The value in the counter is the binary value  
of  $V_{in}$

Successive Approximation ADC: Play 20 questions with  $V_{in}$  ... Is  $V_{in}$  more than  $\frac{5V}{2}$ ? if yes MSB is 1, otherwise 0.


is  $V_{in}$  more than  $\frac{3}{4}5V$ ?

if yes next bit also 1 otherwise 0

is  $V_{in}$  more than  $\frac{7}{8}5V$ ?


is  $V_{in}$  more than  $\frac{1}{4}5V$ ?  
if yes next bit is 1.

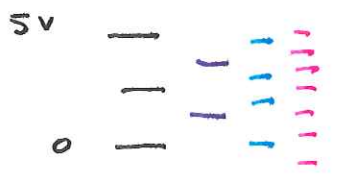is  $V_{in}$  more than  $\frac{5}{8}5V$ ?



answer to each question gives next bit of approx digital value

Note: in below A is MSB; H to LSB

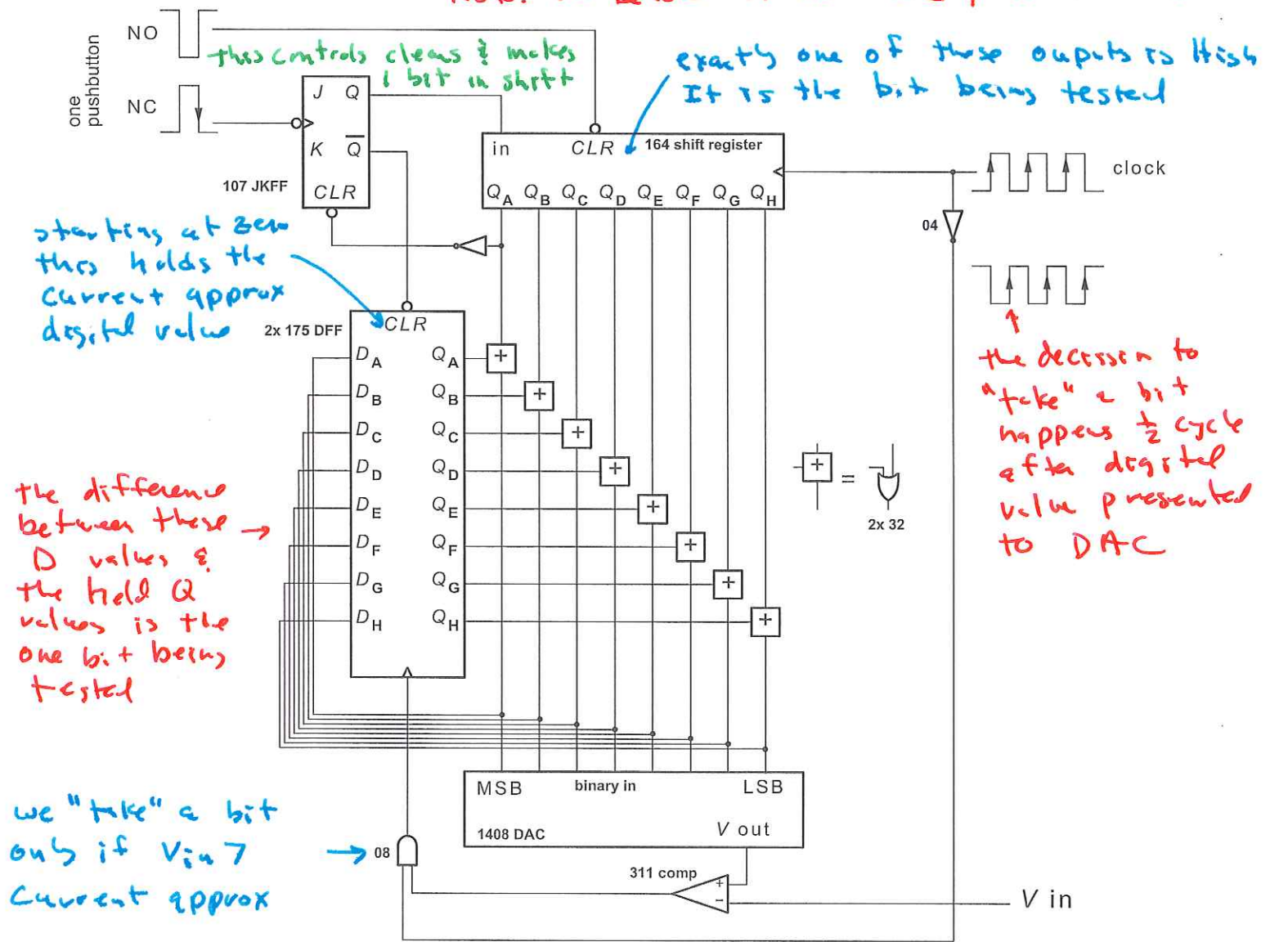

Note: in actual circuit 1408 DAC produces a negative voltage output. If thinking of positive DAC outputs reverse +- on comparator