
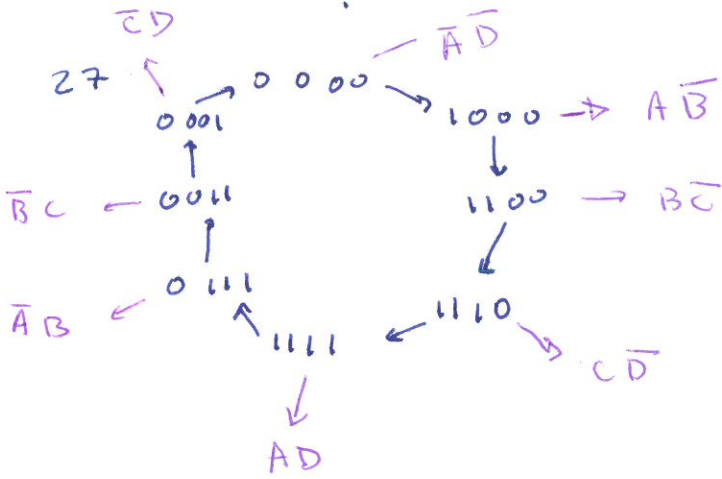


Problems. pdf : 21a, 27, 34, 31, 32, 36
 Computers. pdf: 1, 2

21a - use active low SK FF

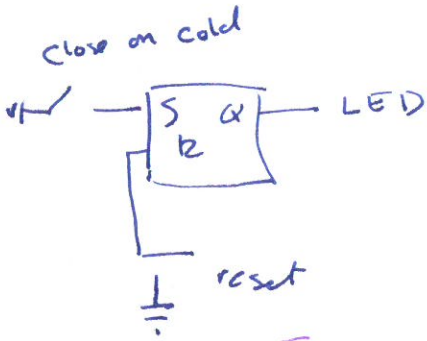

$$V_1 = V \frac{R_1}{R_1 + \frac{R_2 R_3}{R_2 + R_3}} = 5 \frac{15}{15 + 33.8} = 1.57V$$

$$V_0 = V \frac{R_1 R_2}{R_1 + R_2 + R_3} = 5 \cdot \frac{13}{51 + 13} = 1.02V$$

$$R_2 || R_3 = \frac{100 \cdot 51}{151} = 33.8$$

$$R_1 || R_3 = \frac{100 \cdot 15}{115} = 13.0$$

34 a) Math: $r_1 = \frac{1}{7} r_3$
 $r_2 = \frac{1}{2} r_3$

i say $r_3 = 100k$
 $r_1 = 14.3k$
 $r_2 = 50k$

b) Take $V_T = 1.25V \rightarrow \frac{1.25}{5} = \frac{r_1 || r_2}{r_2}$
 $\frac{1.25}{5} r_2 = r_1 || r_2 = 12.5k$
 $\frac{\Delta V}{V_T} = \frac{.5}{5} = \frac{12.5k}{12.5k + R_3} \rightarrow .1(12.5 + R_3) = 12.5k$
 $R_3 = 125 - 12.5 = 112.5k \rightarrow 110$
 $\frac{1}{r_1} + \frac{1}{r_2} = \frac{1}{12.5}$
 $r_1 = \frac{1}{\frac{1}{12.5} - \frac{1}{r_2}} = 16.7k \rightarrow 16$

$$R_2 || R_3 = \frac{51 \cdot 110}{161} = 34.85$$

$$R_1 || R_3 = \frac{16 \cdot 110}{126} = 13.97$$


$$V_1 = V \frac{16 || 110}{16 || 110 + 34.85} = 1.57V$$

$$V_0 = V \frac{16 || 110}{51 + 16 || 110} = 1.08V$$


31 - The spec sheet is a bit obscure on exactly how to connect the cap/resistor. Hit Frys 7.59 (p 462) is accurate (even though it does not exactly apply to 121)

Figure 2 in [sn74121B.pdf](#) or in [sn74121.pdf](#) in the notes: "1. an external capacitor may be connected between C_{ext} (positive) and R_{ext}/C_{ext} . 2. To use the internal resistor connect R_{int} to V_{CC} "

So: with external R:

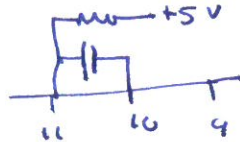

with internal 2k:

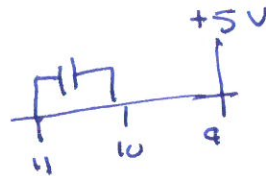

The formula for pulse length is also not easy to find:

$$\tau = .7 RC$$

I'm using internal 2k so $20 \mu s = .7 \cdot 2k \cdot C$

$$.014 \mu F = C$$

Note: not in Hit alloy "5%" list so hard to purchase - use $.015 \mu F$

For $10 \mu s$ pulse needed for

50 kHz square wave need $\frac{1}{2}$ above ... $6.8 nF$ or $6800 pF$

For 1ms delay


$$1 \times 10^{-3} = .7 \cdot 2k \cdot C$$

a) B is good for positive edge


$$.71 \mu F = C$$

A1 & A2 = Low / pull down / GND at corners

use $.68 \mu F$


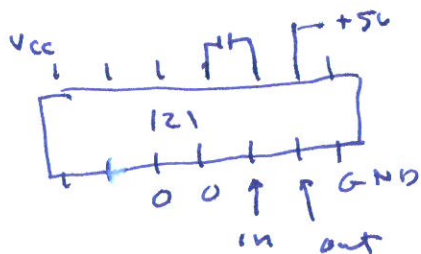


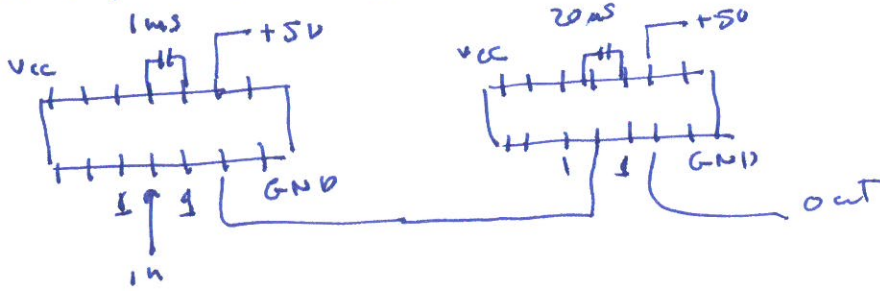b) A inputs for negative edge: $A1 = \text{High}$ $A2 = \text{Input}$ $B = \text{High}$



c) $f_n = 50 \text{ kHz}$, $\text{Period} = 20 \mu\text{s}$ so $H \& L$ are $10 \mu\text{s}$ each

As above

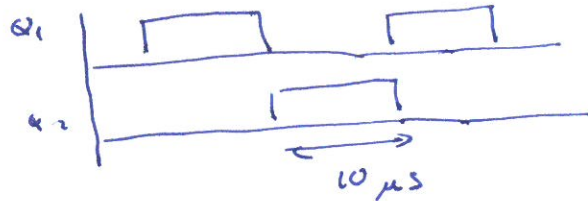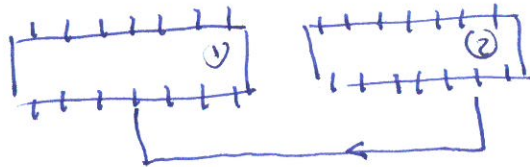

32) a) B b) C c) C d) A

36 see lecture 11-timers.pdf for words

mono
monoshot C: between (7) = discharge to gnd) trissen goes low \rightarrow
R1: between (7) to V_{CC} pulse $1.1RC$

oscillator: C: between (7) to gnd $\leftarrow \text{trissen}$
R_A: between (7) = discharge to V_{CC}
R_B: between (7) to (2)
connect (6) = threshold to (2) = trissen

format for :
 64 bit ("double") float:
 (sign)(11 bit exponent)(52 bit mantissa)
 1.0= 0x3FF0000000000000 = 00 ten 1 rest 0
 2.0= 0x4000000000000000 = 0 one 1 rest 0
 0.5= 0x3FE0000000000000 = 00 nine 1 rest 0

$$x_{n+1} = \frac{1}{2} (x_n + S/x_n)$$

(3)
(2)
(1)

$$x_0 = (1 - 2^{52})/2 + 2^{61}$$

find sqrt of a number stored in RAM
 find 3 mistakes!

```

load r0 r1      1101x01 load opcode #r1 holds S
address that holds number
mov r1,r2      0011x12 mov opcode
sub r2,r0,r2   0111202 sub opcode
2^52
clr r3        0001xx3 clr opcode
inc r3 r3     0011x33 inc opcode
asr r2 r3 r2  0111232 asr opcode
add r2 r0 r2  1111202 add opcode #r2 holds the first approx: x
2^61
mov r0 r5     1011x05 mov opcode
2.0
mov r0 r6     1011x06 mov opcode
small
mov r0 r9     1011x09 mov opcode
2
mov rF rE    0011xFE mov opcode #current PC=rF saved to rE
add r9 rE rE  01119EE add opcode #note (rE) is address of following instruction
mov r2 r4     0011x24 mov opcode #r4 is the starting x
fdiv r1 r2 r3 0111123 fdiv opcode (1)
fadd r2 r3 r2 0111232 fadd opcode (2)
fdiv r2 r5 r2 0111252 fdiv opcode #r2 is the updated x (3)
fsub r2 r4 r4 0111232 fsub opcode
fdiv r4 r2 r4 0111123 fdiv opcode
fabs r4 r4    0011044 fabs opcode
fcmp r4 r6    011046x 2 fcmp opcode = fsub opcode
bpl rE       0011xEF conditional version of mov rE rF opcode
mov r0 rE    1011x0E mov opcode
address to output x
store r2 rE  0110CEx store opcode
halt
    
```

B bus holds address to load

Following not instructions

wrong reg

example: (all iterations shown)
 take sqrt of 2.
 bit pattern of 2.=4000000000000000 (hex)
 bit pattern of x0=3FF8000000000000 (hex)

```

1.5000000000000000
1.4166666666666665
1.4142156862745097
1.4142135623746899
1.4142135623730949
    
```

bit pattern of xN=3FF6A09E667F3BCC (hex)

1.4142135623730951 (actual)

take sqrt of pi
 3.14159265358979323d0