

V - potential difference "across or between" Volt = $\frac{I}{C} = \frac{PE}{charge}$

- in some sense we should be writing things like $\Delta V = IR$ but since every voltage is a ΔV , why bother with Δ ?
- when we talk about "the voltage" at a point, that voltage is a ΔV to "ground"
- "ground" can be any point we select - it need not follow the technical definition of connected to a metal stake driven into the ground water.
- scopes measure voltages relative to ground - cannot easily be used for voltage across

I - current "through" Amps = $\frac{C}{S}$ [typical: mA]

Note: "charge" is absolutely conserved

- current density $J = I/\text{Area}$ - intensive

Kirchhoff's Laws: ① Current in = current out
② Voltage around loop = 0

R - resistance - ohm's law: $V = I R$ $R = \frac{V}{I}$ [typical Ω]




- Note: Ohm's Law is an approximation of nature
- R depends on the material & its geometry
"resistivity" is the intensive quantity
- in this class wires are assumed to have $R=0$
therefore every piece of a wire is at the same voltage.

C - capacitance aka condensers $\frac{1}{T} \left. \begin{array}{l} Q \\ -Q \end{array} \right\} V \quad Q = CV \quad F = \frac{C}{V} \quad [\mu F]$


- note: we can have a current "through" a capacitor with current in = current out? Q increases but no electron is going thru the gap

L - inductors - aka coils, chokes $H = \frac{V}{A/I}$ [nH]
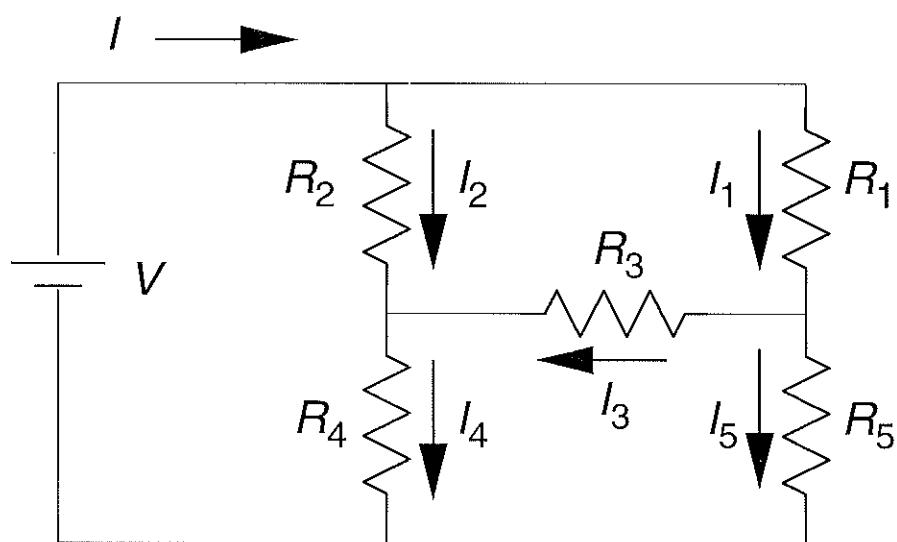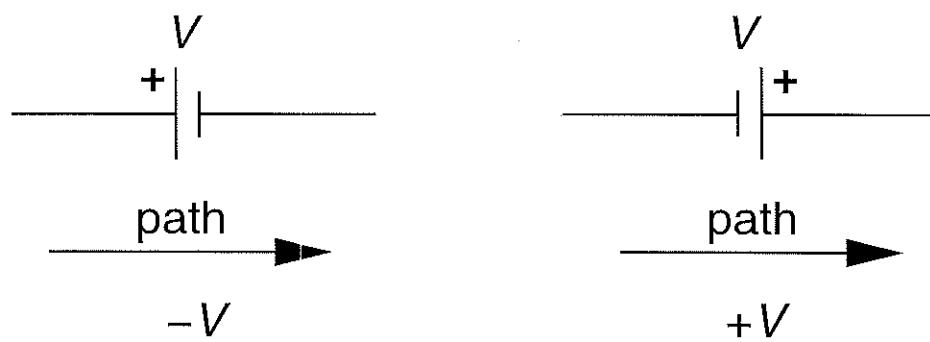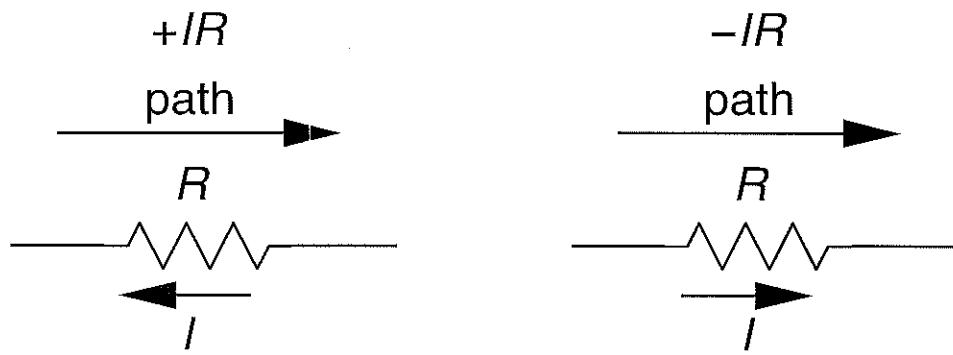
$$\left. \begin{array}{l} V \\ - \end{array} \right\} L \frac{dI}{dt}$$



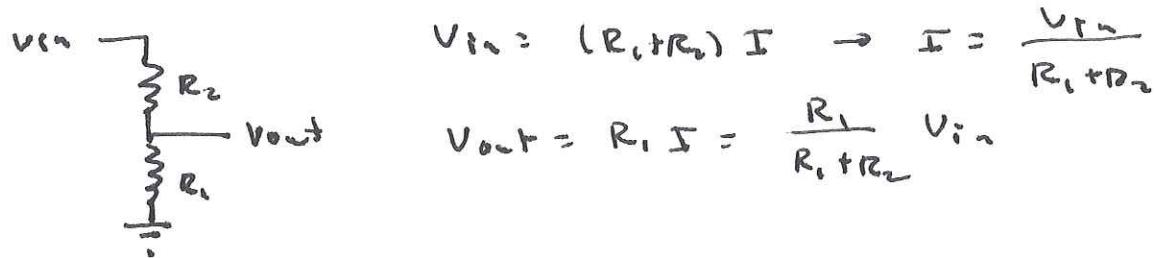The most important example: voltage divider



Q: the above assumed current thru R_2 = current thru R_1 , what if some current is drawn out -

$$V_{in} = (\tilde{I} + I) R_2 + \tilde{I} R_1$$

$$\frac{V_{in} - I R_2}{R_1 + R_2} = \tilde{I}$$

$$V_{out} = \tilde{I} R_1 = \frac{R_1}{R_1 + R_2} V_{in} \rightarrow \frac{R_2 R_1}{R_1 + R_2} I$$

Voltage divider
 $R_1 \parallel R_2$

This is a general result \rightarrow Thevenin's Thm

Case of sinusoidal "AC" sources

$$\text{+ } \left\{ V = V_0 \cos(\omega t) \right. \quad V_{rms} = \frac{V_0}{\sqrt{2}}$$

$$Q = CV = C V_0 \cos(\omega t)$$

$$I = \dot{Q} = -C\omega V_0 \sin(\omega t)$$

amplitude = $C\omega V_0$


$$\rightarrow I_0 \left(\frac{1}{C\omega} \right) = V_0 \quad X_C$$

$$\left\{ \begin{array}{l} I = I_0 \cos(\omega t) \\ V = L \frac{dI}{dt} = -L I_0 \omega \sin(\omega t) \end{array} \right.$$

amplitude = $L I_0 \omega$

$$V_0 = \left(L \omega \right) I_0 \quad X_L$$

Switched DC Sources -

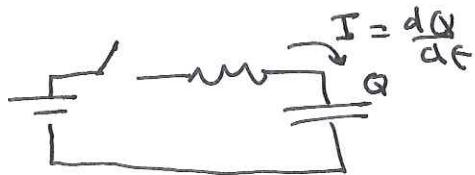

$$I = \frac{dQ}{dt} \quad V = RI + \frac{Q}{C} = R \frac{dQ}{dt} + \frac{Q}{C}$$

1st order, linear, inhomogeneous
Seek homogeneous solution + particular solution

homogeneous: $0 = R \frac{dQ}{dt} + \frac{Q}{C}$

$$\frac{dQ}{dt} = -\frac{1}{RC} Q \leftarrow \text{this is a separable Diffeq but it should be obvious solution is}$$

exp: $Q = A e^{-t/RC}$

Particular: $I=0; Q=CV$

any constant \rightarrow "time constant" $\tau = RC$

General: $Q = CV + A e^{-t/\tau}$


BC: $Q(t=0) = 0 \rightarrow Q = CV(1 - e^{-t/\tau})$



$$I = \frac{dQ}{dt} = \frac{V}{R} e^{-t/\tau}$$

$$V = IR + L \frac{dI}{dt}$$

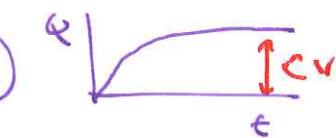homogeneous: $\frac{dI}{dt} = -\frac{R}{L} I; I = A e^{-\frac{R}{L} t}$



time constant $\tau = L/R$

Particular: $\frac{dI}{dt} = 0 \Rightarrow I = \frac{V}{R}$

General: $I = \frac{V}{R} + A e^{-\frac{R}{L} t}$

BC: $I(t=0) = 0 \Rightarrow I = \frac{V}{R}(1 - e^{-t/\tau})$