

The phase difference between $V \& I$ in L/C makes Kirchhoff's Laws difficult to apply eg

$$V = RI + L \frac{dI}{dt} \rightarrow V_0 \cos(\omega t) = RI_0 \cos(\omega t) - L \omega I_0 \sin(\omega t)$$

must now add $\cos \& \sin$

If we go to complex numbers phase difference becomes just multiplication & allows us to factor out time.

$$V = RI + L \frac{dI}{dt} \rightarrow V_0 e^{i\omega t} = RI_0 e^{i\omega t} + i\omega L I_0 e^{i\omega t}$$

$$V_0 = R I_0 + i\omega L I_0$$

\sum exactly like $R = \omega L$

Result: treat C as if " $R = \frac{1}{i\omega C}$ " (because $V = \frac{Q}{C}$)

$$\therefore Q = \int I dt \rightarrow I_0 \int e^{i\omega t} dt = \frac{I_0}{i\omega} e^{i\omega t}$$

And L as if " $R = i\omega L$ "

Note: EE's used symbol "i" for current hence they & HH use $\sqrt{-1} = j$


Note: $I = I_0 e^{i\omega t}$ is the rotating phasor at 200°



Then $V_L = i\omega L I$ is 90° ahead as $i = e^{i\pi/2}$ and $V_C = \frac{-i}{\omega C} I$

is 90° behind as $-i = e^{-i\pi/2}$


V_R is in phase with I

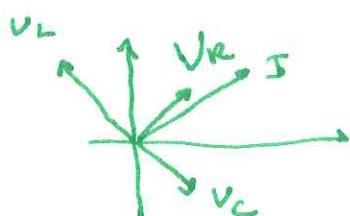

Note: All the rules from 200 which were derived via Kirchhoff's Laws now apply with these complex "resistors" eg $Z_1 || Z_2 = \frac{Z_1 Z_2}{Z_1 + Z_2}$

$$Z_1 || Z_2 = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

$$f = 5000 \text{ Hz}$$

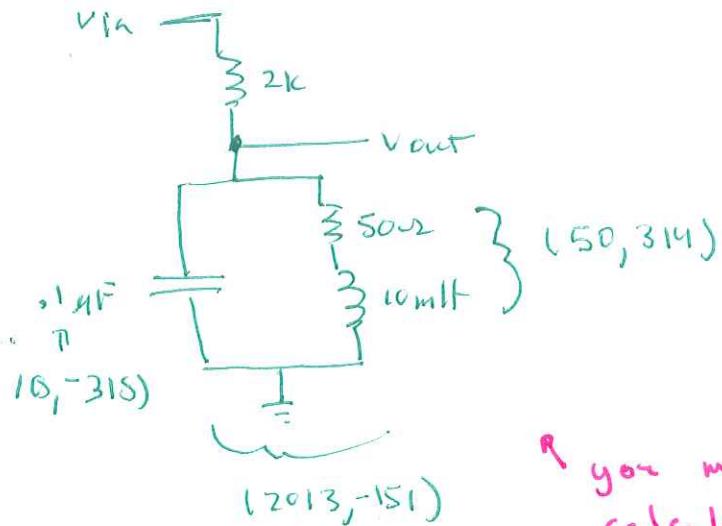



$$\frac{V_{out}}{V_{in}} = \frac{(2013, -151)}{2000 + (2013, -151)}$$

$$= (.5, -1.88 \times 10^{-2})$$

$$= .5 L^{-2.1} \text{ phase}$$

magnitude

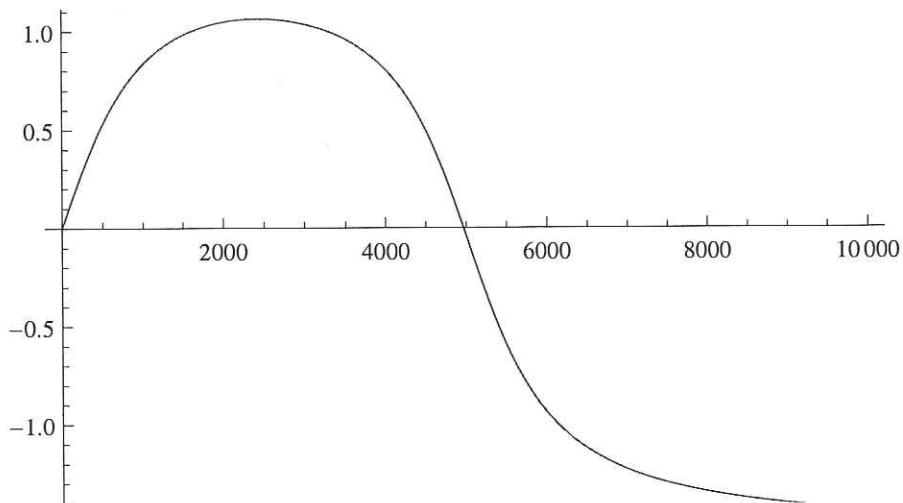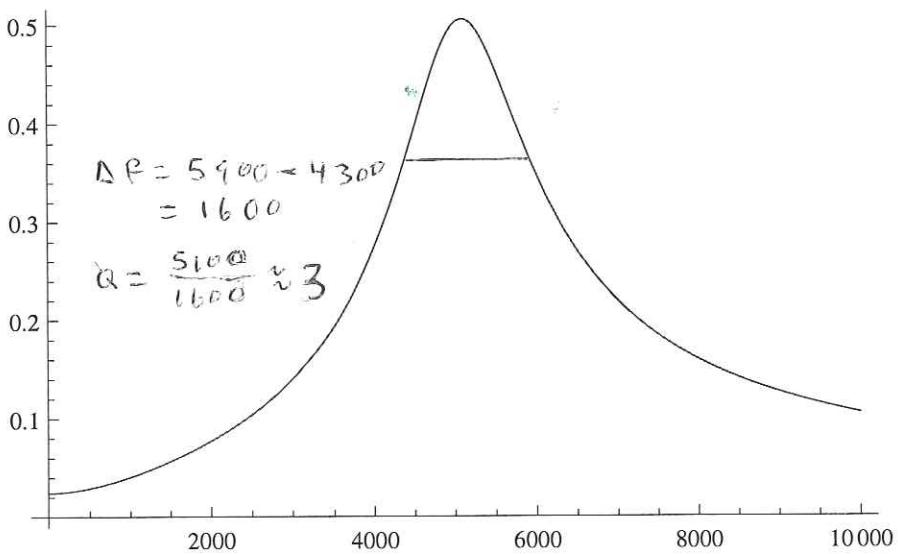You must be able to do complex calculations like this using your calculator!



03/18/14

```

1 L=.01
2 c=10^(-7)
3 r=2000
4 f=5000
5 zC=1/(I^2 Pi f c)
6 zL=I^2 Pi f L + 50
7 z=zC zL/(zC+zL)
8 Out[7]= 2012.56 - 151.243 I
9
10 z/(2000+z)
11 Out[8]= 0.502272 - 0.0187606 I
12
13 {Abs[%],Arg[%]*180/Pi}
14 Out[9]= {0.502622, -2.13909}
15
16 ClearAll[f]
17 zC=1/(I^2 Pi f c)
18 zL=I^2 Pi f L + 50
19 z=zC zL/(zC+zL)
20 z/(2000+z)
21 Plot[Abs[%],{f,1,10000}]
22 Plot[Arg[%],{f,1,10000}]
23 GraphicsGrid[{{%15},{%16}}]
24 Export["tank.eps",%]
25

```

$$v_{out} = \frac{\frac{1}{i\omega_c} || i\omega L}{\frac{1}{i\omega_c} || i\omega L + R} v_{in} = \frac{\frac{1}{i\omega_c} || i\omega L}{i(\omega L - \frac{1}{\omega_c})}$$

$$= \frac{A}{A + i\Delta} v_{in} \quad \rightarrow 0 \quad \omega \rightarrow \infty$$

$$| \frac{v_{out}}{v_{in}} | = \frac{A}{\sqrt{A^2 + \Delta^2}} \quad \begin{matrix} \rightarrow 0 & @ \omega_0 \\ \rightarrow 0 & \omega \rightarrow 0 \end{matrix}$$

Taylor Δ near ω_0 :

$$\Delta \approx 0 + \Delta' \left(\frac{\Delta \omega}{\omega_0} \right)$$

$$\frac{L}{R} + \frac{1}{\omega_0} \frac{1}{RC} = 2 \frac{L}{R}$$

$$| \frac{v_{out}}{v_{in}} | = \frac{A}{\sqrt{A^2 + \left(\frac{2L}{R} \Delta \omega \right)^2}}$$



Find $\Delta \omega$ for $\frac{1}{2}$ $A = \frac{\omega_0}{R} \Delta \omega = \frac{L}{RC}$

$$\Delta \omega = \frac{1}{2} \frac{1}{RC}$$

full width = $\frac{1}{RC}$

$$Q = \frac{\omega_0}{\text{full}} = \frac{\frac{1}{RC}}{\frac{1}{RC}} = \sqrt{\frac{RC}{L}} \quad (\frac{1}{a} \text{ auf Seite})$$

\rightarrow LRC series: $Z = R + i(\omega L - \frac{1}{\omega C})$


$$I_o = \frac{V_o}{Z} ; \quad |I_o| = \frac{V_o}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$

peak at
 $\omega L = \frac{1}{\omega C}$
 $\omega = \frac{1}{\sqrt{LC}}$

\hookrightarrow Taylor expand $\Delta @ \omega = \frac{1}{\sqrt{LC}}$: $\Delta \approx 0 + \left(L + \frac{1}{\omega^2 C} \right) \Delta \omega$

half-width $\Delta \omega$ for $\frac{1}{2}$ $\rightarrow 2L \Delta \omega = R \rightarrow \Delta \omega = \frac{R}{2L}$

$$Q = \frac{\pi Q_o}{\sqrt{6}} \approx \frac{1}{2} \frac{\omega_0}{\Delta \omega} = \sqrt{\frac{L}{RC}}$$

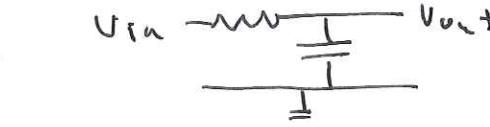Low Pass RC circuit: 



$$\frac{V_{out}}{V_{in}} = \frac{-i/wC}{R + i/wC} = \frac{1}{\omega RC + 1}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{(\omega RC)^2 + 1}} = \begin{cases} \omega \ll \frac{1}{RC} & \rightarrow 1 \\ \omega \gg \frac{1}{RC} & \rightarrow \frac{1}{\omega RC} \end{cases}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{2}} \quad @ \quad \omega = \frac{1}{RC} \quad \leftarrow \text{"-3dB freq"}$$

phase $\frac{V_{out}}{V_{in}}$ = $\begin{cases} \omega \ll \frac{1}{RC} & \rightarrow 0 \\ \omega = \frac{1}{RC} & \rightarrow -\pi/4 \\ \omega \gg \frac{1}{RC} & \rightarrow -\pi/2 \end{cases}$

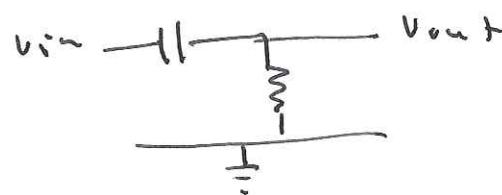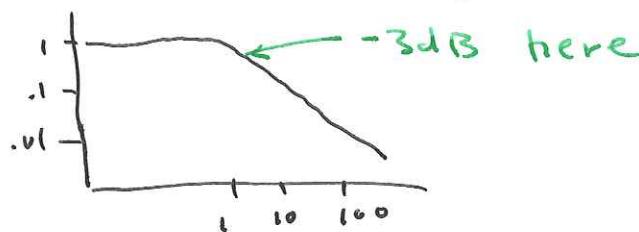Bode Plot: $\log\left(\frac{V_{out}}{V_{in}}\right)$ vs $\log(\text{freq})$



High Pass RC circuit:

$$\frac{V_{out}}{V_{in}} = \frac{R}{R - i/wC} = \frac{1}{1 - \frac{i}{\omega RC}}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{1 + (\frac{1}{\omega RC})^2}} = \begin{cases} \omega \gg \frac{1}{RC} & \rightarrow 1 \\ \omega = \frac{1}{RC} & \rightarrow \frac{1}{R_2} \\ \omega \ll \frac{1}{RC} & \rightarrow \omega RC \end{cases}$$

Phase

| | | |
|---|------|------|
| 0 | +π/4 | +π/2 |
|---|------|------|

Bode Plot

