

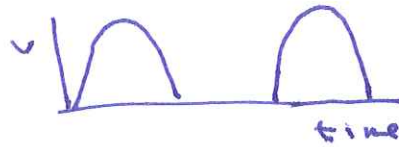



Rectification

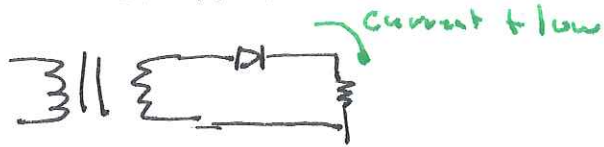

"half wave"

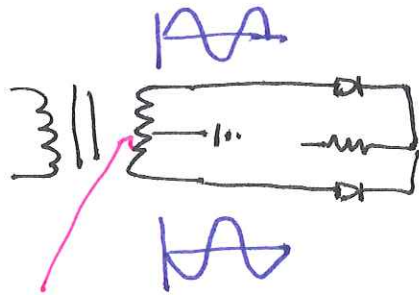


"center tapped"

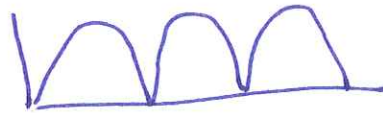

"full wave"

$$f = 120 \text{ Hz}$$


Full wave bridge with 2 diode drop.

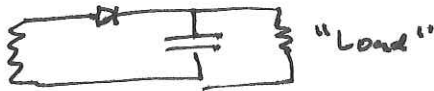

$R_{TH}?$

$$V_{DC} = V_0 - \frac{1}{2} \frac{I_T}{C}$$

What is V_{rms} of sawtooth?

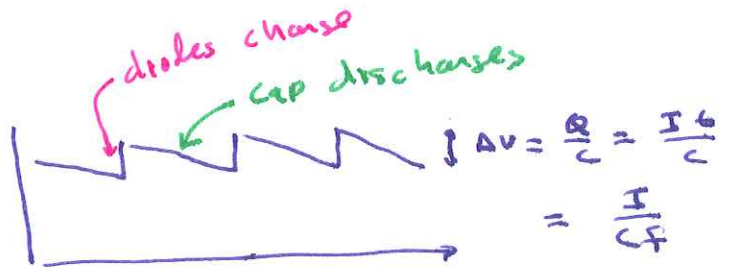


$$V = -A \frac{t}{\pi/2}$$

$$\langle V^2 \rangle = \frac{1}{T} \int_{-T/2}^{T/2} \left(-A \frac{t}{\pi/2}\right)^2 dt = \frac{4A^2}{\pi^3} \int_0^{T/2} t^2 dt$$

$$= \frac{A^2}{3} \rightarrow V_{rms} = \frac{A}{\sqrt{3}}$$


$$V_{rms} = \frac{1}{\sqrt{3}} \frac{I_T \pi/2}{C}$$

3 terminal regulator

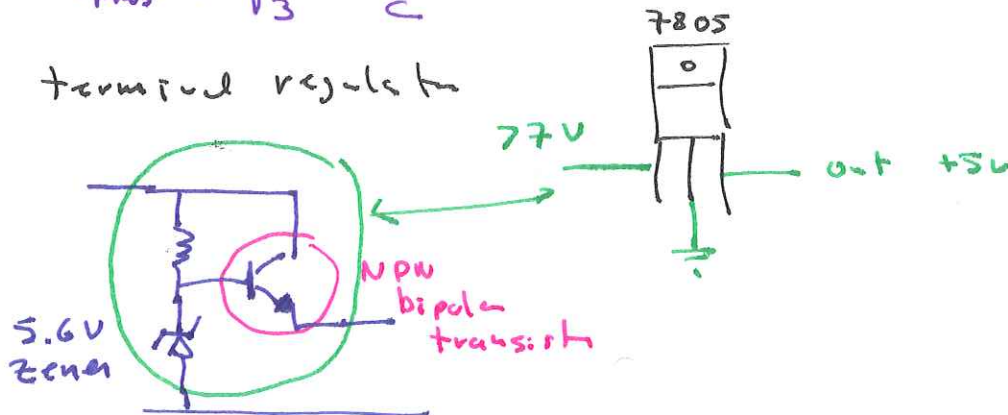

Select six (6) (out of seven) problems for grading.

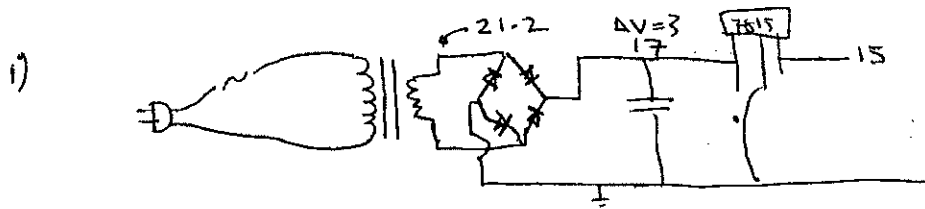1. Design and provide the schematic diagram for a +15 volt regulated power supply that will supply .75 A of current. Use a 7815 IC regulator, which is similar to the 7805 used in lab (e.g., it requires a 2 V "headroom"), but is designed for 15 volts. The full-current peak-to-peak ripple before the regulator should be 3 V. Record on your drawing the ratings for all components (e.g., transformer rms secondary voltage, C of capacitor, power dissipated in regulator at full current, rating for fuse on 120 V line cord, etc.)



$$V_{\text{rms}} = \frac{21:2}{\sqrt{2}} = 15.0 \text{ V}$$

$$C = \frac{IT}{\Delta V} = \frac{(.75)(\frac{1}{120})}{3} = 2080 \mu\text{F}$$

$$7815 \text{ power} = (2 + 1.5)(.75) = 2.63 \text{ W}$$

$$\text{fuse} = \frac{(21:2)(.75)}{120} = .133 \text{ A use } \frac{1}{4} \text{ A}$$