
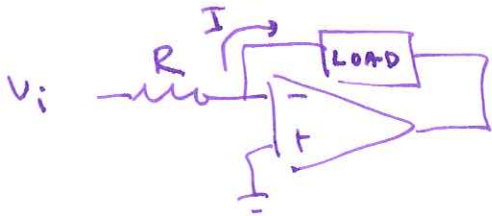


Current sources — supplies a fixed current — if R is big
 a big voltage results; if R small \rightarrow small voltage.
 Every current source has its limits — if R is too big
 will not be able to produce required voltage.

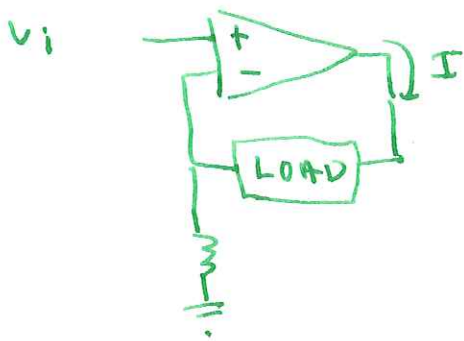[contrast: voltage sources supply fixed voltage — if R is
 big a small current results; if R small \rightarrow large current.
 Every voltage source has its limits — if R is too small
 will not be able to produce required current]




$$I = \frac{V_i}{R}$$



$$I = \frac{V_i}{R}$$

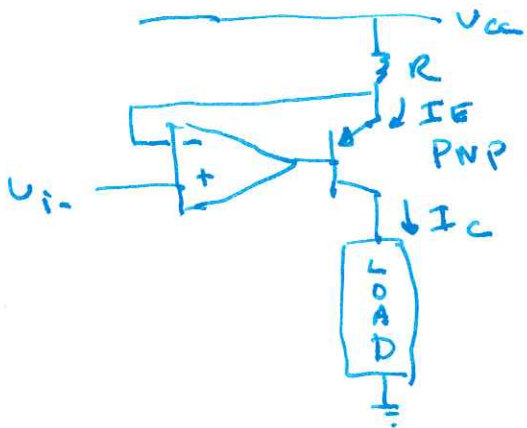Always require a "floating" load — often want load
 connected to ground. Also always limited by current
 output of op-amp \rightarrow a few mA



Since $I_E \approx I_C$

$$I_C \approx \frac{V_i}{R}$$

Vocabulary

AC or DC amp

bandwidth (f-3dB) ; "mid band" gain

inverting / non inverting

clipping

differential amp (out = $A_d(V_+ - V_-)$)

- common mode gain (where $V_+ = V_- = V_{cm}$) A_c

- differential gain (where $V_+ - V_- = V_{dm}$) A_d

- common mode rejection ratio = $\frac{A_d}{A_c}$ (often in dB)

noise - note odd unit $\mu V / \sqrt{Hz}$ or PA / \sqrt{Hz}

For op-Amps

Gain - Bandwidth product [note compensated op-Amps]


slew rate

"rail-to-rail" or limited out put voltage swing



input offset voltage - "as if"

input bias current

open loop gain

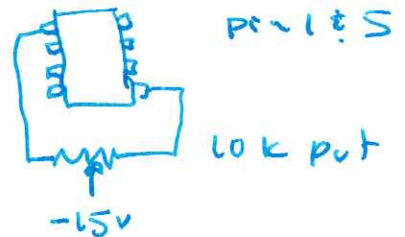

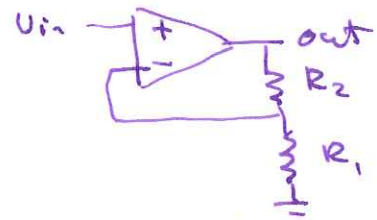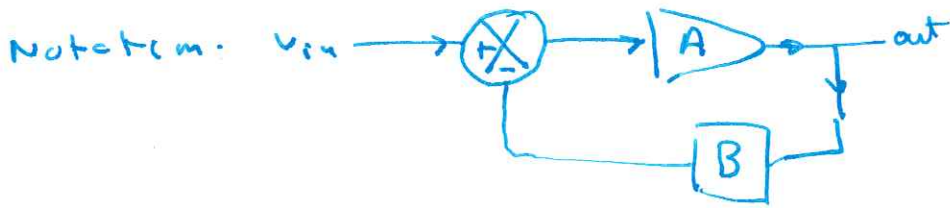Feedback - some notation & algebra to show that "things get better if you 'throw away' gain"



$$A(V_{in} - BV_{out}) = V_{out}$$

$$V_{in} = \left(B + \frac{1}{A}\right) V_{out}$$

$$\frac{1}{\left(B + \frac{1}{A}\right)} = \frac{V_{out}}{V_{in}} \leftarrow \text{circuit gain}$$


Remark: not related to transistor β

in contrast to op amps gain

$$\frac{1}{\left(1 + \frac{1}{AB}\right)} \leftarrow \frac{R_1 + R_2}{R_1} = 1 + R_2/R_1$$

sometimes called the "loop gain" AB

alternative form

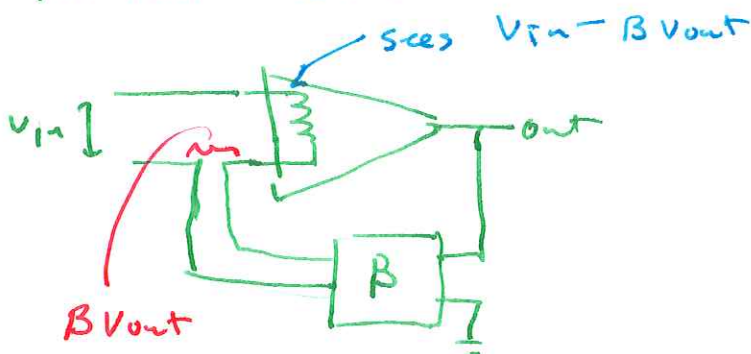


Note: the above is negative feedback; positive

feedback \rightarrow expo growth and is generally a bad idea.

The invention of negative feedback amps is attributed to Harold Black - EE works at Bell Labs - 1927

Output Impedance - a trick to mathematically calculate a circuit output impedance. Consider $V_{in} = 0$ ("ground the input") thro (in theory) would produce $V_{out} = 0$ but we (mathematically) apply an external voltage V to the output & calculate the resulting current, I . The circuit's output impedance is the V/I .

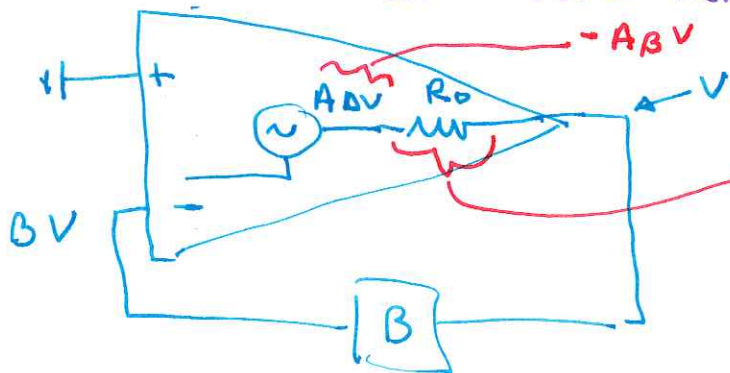(In an experimental situation we'd more like remove current from amp - by applying a load - and measure the resulting voltage drop - the circuit's ~~Z_{out}~~ Z_{out} would then be $\frac{\Delta V}{I}$)




voltage drop = $V - -ABV$
 $= (1 + AB)V$

current = $\frac{\text{voltage drop}}{R_0}$

$Z_o = \frac{V}{I} = \frac{R_0}{(1 + AB)}$ ← note reduced from what was probably a small R_0 to begin with. $I = \frac{(1 + AB)V}{R_0}$

Slight practical consideration - in real circuit feedback network B it self would draw some current

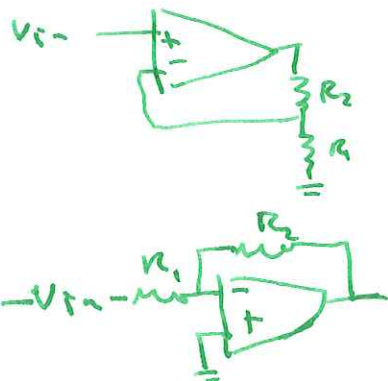
in both cases an addition current flow of $\frac{V}{R_1 + R_2}$ happens - i.e. must add this current to above



result: $Z_{out} = \frac{R_0}{(1 + AB)} \parallel R_1 + R_2$

this should be much smaller than $R_1 + R_2$ so $Z_o \approx \frac{R_0}{(1 + AB)}$

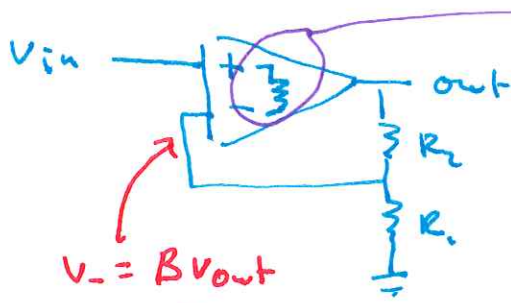Input Impedance (Note: for inverting amp circuit this will be R which is not huge — say 10Ω)



$$V_- = BV_{out}$$

$$B = \frac{R_1}{R_1 + R_2}$$

$$I = \frac{V_{in} - BV_{out}}{R_{in}} = \frac{V_{in}}{R_{in}} (1 - BG)$$

$$G = \frac{V_{out}}{V_{in}} = \frac{A}{1 + BA}$$

$$\frac{V_{in}}{I} = \frac{R_{in}}{(1 - BG)} = \frac{R_{in}}{(1 - \frac{AB}{1 + BA})}$$

$$= \underline{R_{in}(1 + BA)}$$

an intrinsically large value increased even more.