

 
 
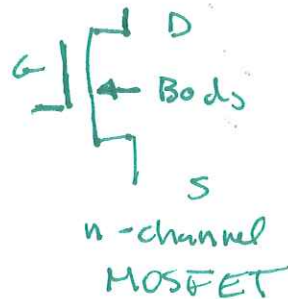


 3 terminal devices - we start with the ancient triode  
 [usually attributed to Lee de Forest (1906) [PhD under Gibbs at Yale] but not much used until 1912]




The flow of electrons cathode  $\rightarrow$  anode can be affected (reduced) by putting a negative voltage on Grid. Note that Grid sits in vacuum - essentially disconnected - so basically zero current & hence zero power in. The mA scale cathode-anode current @ 100V represents  $\approx$  1W power so we have potential for power gain.

 The physics of Field Effect Transistors (FET) is not much like a triode but the basic idea is the same - a voltage (at zero current) controls a larger current flowing between two other terminals



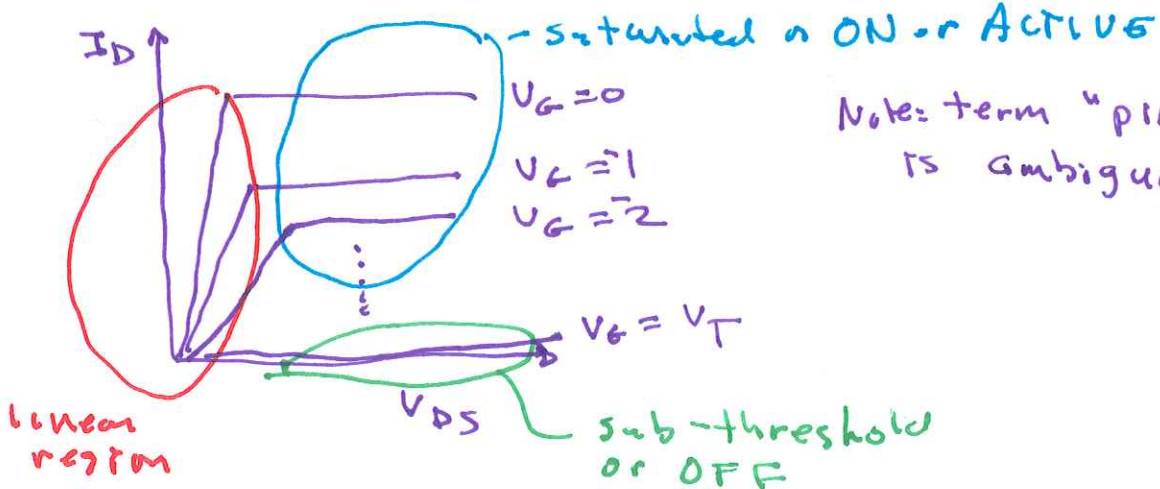We display the behavior of these 3-terminal devices with characteristic curves - plots of  $I_D$  thru vs  $V_{D/S}$  for various control voltages



Note: term "pinched-off" is ambiguous - avoid

currently we restrict consideration to the saturated regime where  $I_D$  plateaus (ie  $I_D$  is constant as  $V_{DS}$  increases — not like a resistor). Then

$$I_D = k (V_G - V_T)^2$$


$V_G - V_T \equiv$  gate drive — larger means more current

For n-channel JFET this is negative &  $V_G$  would also be negative, but  $V_G - V_T > 0$

As shown below we will be interested in


$$\frac{dI_D}{dV_G} = 2k(V_G - V_T) = g = g_{fs}$$

 ← forward admittance  
← transconductance



often we will be interested in  $g$  at a particular voltage — the operating point

Simple circuit — Common Source Amp

 


$V_G$  is used to set a particular  $V_G$ .  $V_{in}$  will slightly modify that  $V_G$  [The capacitor is a bypass cap —  $V_{in}$  will appear with a DC offset]

$$V_{out} = V_{DD} - R_D I_D$$

$$\frac{dV_{out}}{dV_{in}} = -R_D \frac{dI_D}{dV_{in}} = -R_D g$$

← inverting amp with a DC offset.

 Load Line Analysis - plot the equation for  $R_D$  on top of the characteristic curves of FET.



$$V_{DS} + I_D R_D = V_{DD}$$


$$I_D = -\frac{1}{R_D} V_{DS} + \frac{V_{DD}}{R_D}$$

←  $y$  intercept

$x$  intercept: if  $I_D = 0 \rightarrow V_{DS} = V_{DD}$

current that would flow if FET shorted out

 Assume  $V_G$  set =  $-1V$   
by battery. Quiescent point  $Q$ . As  $V_{in}$  swings  $V_G \pm 1V$  (to  $0 \rightarrow 2$ )  
 $V_{DS}$  also changes (inverted)



$$\Delta I_D = \frac{dI_D}{dV_G} \Delta V_G = \left(-\frac{1}{R_D}\right) \Delta V_{DS} \rightarrow -g R_D = \frac{\Delta V_{DS}}{\Delta V_G}$$

In the above I've shown the characteristic curves as exactly flat - no change in  $I_D$  as increase  $V_{DS}$  -


In fact some slope  $\frac{\Delta I_D}{\Delta V_{DS}} = y_{os}$  "output admittance"

Output Impedance - "ground input" & apply extra voltage  $V$  to output. Reduces current thru  $R_D$  increases

current thru FET: Must add current:  $\frac{\Delta V}{R_D} + y_{os} \Delta V$

$$\frac{\Delta V}{I} = \frac{1}{\frac{1}{R_D} + y_{os}} \rightarrow R_D \parallel \frac{1}{y_{os}}$$

# Source Follower

 

$$\Delta V_s = \Delta I_D R_L$$

$$= g_m \Delta (V_{in} - V_s) R_L$$

$$(1 + g_m R_L) \Delta V_s = g_m R_L \Delta V_{in}$$

$$\frac{\Delta V_s}{\Delta V_{in}} = \frac{g_m R_L}{1 + g_m R_L} \approx 1$$

Output Impedance: Force  $V_{out}$  up by  $V$

increase in current thru  $R_L = \frac{V}{R_L}$

decrease in current thru FET =  $-g_m V$

$$I = \text{total added current} = (g_m + \frac{1}{R_L}) V$$

$$\frac{1}{g_m + \frac{1}{R_L}} = \frac{V}{I} = R_{out} \rightarrow \frac{1}{g_m} \parallel R_L$$

300Ω