 


Small Signal Model — the superposition theorem allows us to totally separate signals at different frequencies. In particular we separate the DC signals (volt / amps) — which we call the 'bias' — from AC signals. We must assume the AC signals are 'small' so we can approximate non linear response with just the linear term of Taylor's approx. [Superposition requires linear circuit elements]

Thus we consider a generic 3-terminal device



We assume currents are known functions of voltages. [There is nothing special about this — in future we'll consider cases where Voltage is a function of current. On the other hand the range of validity of Taylor Approx may depend on what we take as dependent / independent variables — i.e. some models rank one better than others]

$$I_2(V_1, V_2) \Rightarrow dI_2 = \frac{\partial I_2}{\partial V_1} dV_1 + \frac{\partial I_2}{\partial V_2} dV_2$$

transconductance g_m
forward admittance y_{fs}

output admittance y_{os}
 $= \frac{1}{R_o}$


$$I_1(V_1, V_2) \Rightarrow dI_1 = \frac{\partial I_1}{\partial V_1} dV_1 + \frac{\partial I_1}{\partial V_2} dV_2$$

input admittance y_{is}
 $= \frac{1}{R_i}$


so small I've never seen a value for this

For FETs this term is truly small, bias dependent and hence not in spec sheet
Note: input capacitance is in spec sheet $\rightarrow y_{os} = i_w C$

Resulting model for FET:

 

AC model for common source amp:

 

so gain is now $g(R_o \parallel R_d)$

EE notation (which I will probably violate sometimes)

I_D - DC current into drain - cap symbol & subscript

i_d - AC current into drain - lowercase " "


i_D - AC+DC current into drain - lowercase symbol
uppercase subscript

e.g. (future) h_{FE} - ratio of 2 total currents
 h_{fe} - ratio of just AC parts

Remark: Common Source Amp - rid $\frac{1}{g_v} V_s \approx \frac{1}{R_o}$ (maybe)

plan: have $V_G = 0V$ but $V_S = +1V$ (eg) so

 
$V_{GS} = -1V$, Let V_S be steady even as I_S (i_s) varies.




Select $R_s \Rightarrow I_D R_s = \text{desired } |V_{GS}|$

Select $C_s \Rightarrow \frac{1}{\omega_c} \ll R_s$ for lowest desired freq.

Design

 

high pass filter
blocking cap

 

Select Quiescent Point
(aka. Operating Point)
 $\rightarrow V_{DS} \approx \frac{V_{DD}}{2}$
 \rightarrow smaller $I_D \rightarrow$ bigger R_D
 \Rightarrow bigger gain
 but bigger output impedance

Given an operating point - Find R_S/C_S to supply the required bias

C_D : this cap will probably be connected to something with an R_{in} . Good practice requires that R_{in} to be bigg compared to circuit's output impedance ($= R_D \parallel \frac{1}{y_{os}}$) $\&$ generally $R_D \ll \frac{1}{y_{os}}$. Thus we should be ok with $X_C = R_D$
 [Solve for C using lowest interesting freq]