
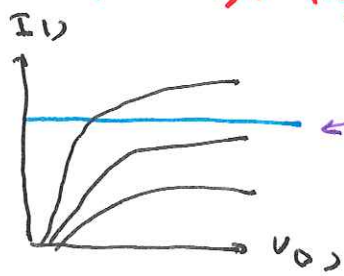


Additional FET circuits.

Note that for common source amp, if we went for higher gain by increasing R_D the operating point was pushed to closer to V_T with resulting reduction in g .

[increasing R_D does result in higher gain - just not as much gain increase as might expect]

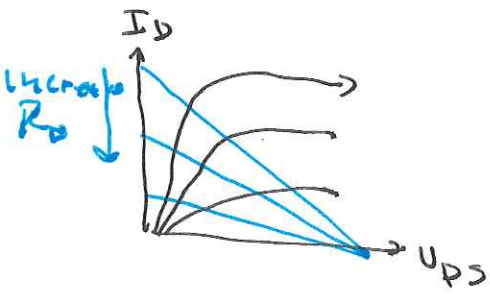Warning: this idea of going for increased gain is almost always the wrong approach - eg it increases Z_{out} which is generally bad. We introduce it here mostly as a way of introducing the idea of an "active load" - not because its anything to actually do.






if we had a load like this very small changes in V_G → big V_{DS} swings i.e. big gain

a device like this would be called a constant current source.

Remark 1: since the slope on I_D vs V is $\frac{1}{R}$, constant current sources correspond to $R = \infty$ [Note $R_D \rightarrow \infty$ should give use big gain as $A \approx -g R_D$]

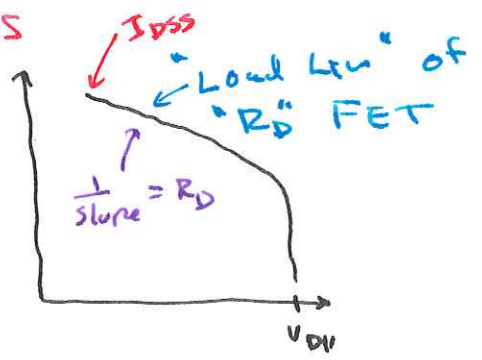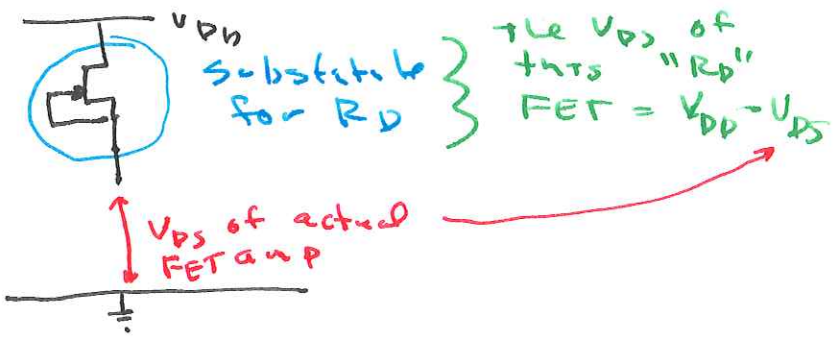Remark 2: (Important) A FET acts a bit like a constant current source - i.e. those plateaus





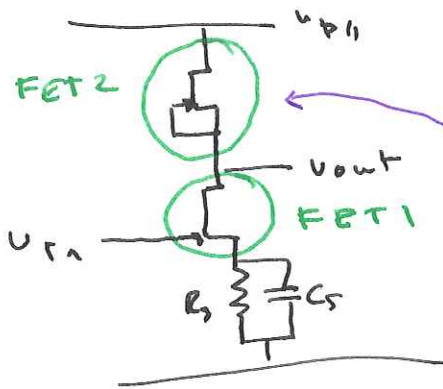


Repeat warnings: $R_D \rightarrow \infty$ is a bad idea

"Active Load" - HH talks about improving followers with active load that is a good & useful idea.

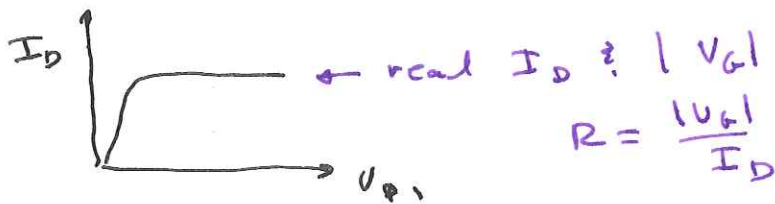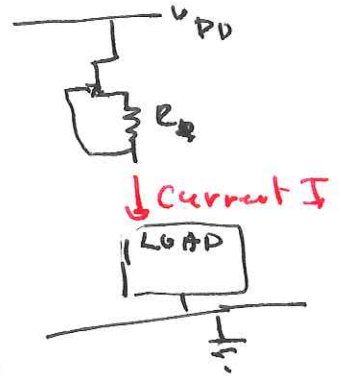Good Idea: FET as a current source - set I via R . [Note: $R \rightarrow \infty \Rightarrow I_{DSS}$]



alt: load line analysis:

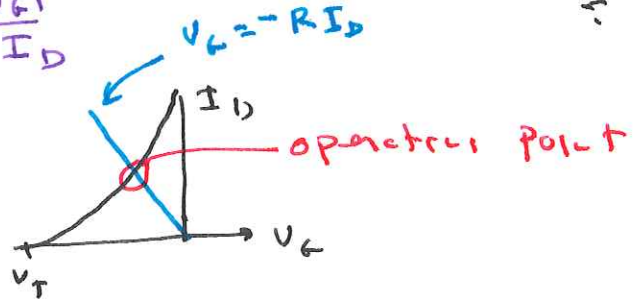

Remark: HH talks about "current limited diodes" - pre built FETs with correct R to produce a specified current.

These always sound like a great idea to me, but any time I've thought to use them I've found them ① hard to find (buy eg. from Digi-Key) ② pricy - much more than a FET.

Good Idea - FET (in its linear region) is a voltage controlled resistor. The "linear region" is not super linear but HH describe how to improve it.

$$\frac{1}{R_{ps}} = \underbrace{2k}_{g} \left[(v_G - v_T) - \frac{v_{DS}}{2} \right]$$

Good Idea - use a ON/OFF FET (particularly a MOSFET) as a switch.


On resistance $\text{few } \Omega$; OFF: expo small leakage currents.

MOSFETS can control multiple As! - Power MOSFETS

packaged "analog switches"

enhancement mode MOSFET

2N7000: TTL signals control 100mA

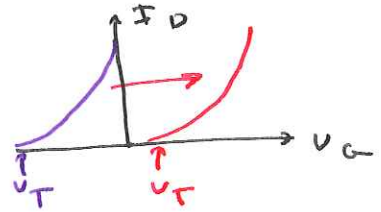

Why use a discrete FET instead of a 411?

→ high input impedance → for followers

(FET amps don't have much gain; are subject to parameter variations)

→ current source

→ sometimes a single FET exactly matches need

→ MOSFET current switches / power control

↪ recall switching power supplies