

The phase difference between V & I in L/C makes Kirchhoff's Laws difficult to apply e.g.

$$V = RI + L \frac{dI}{dt} \rightarrow V_0 \cos(\omega t) = RI_0 \cos(\omega t) - L\omega I_0 \sin(\omega t)$$

must now add \cos & \sin

If we go to complex numbers phase difference becomes just multiplication & allows us to factor out time.

$$V = RI + L \frac{dI}{dt} \rightarrow V_0 e^{i\omega t} = RI_0 e^{i\omega t} + i\omega LI_0 e^{i\omega t}$$

$$V_0 = RI_0 + i\omega LI_0$$

↳ exactly like $R = i\omega L$

Result: treat C as if " R " = $\frac{1}{i\omega C}$ (because $V = \frac{Q}{C}$)

$$\therefore Q = \int I dt = I_0 \int e^{i\omega t} dt = \frac{I_0}{i\omega} e^{i\omega t}$$

And L as if " R " = $i\omega L$

Note: EE's real symbol " i " for current hence they & HH use $\sqrt{-1} = j$


Note: $I = I_0 e^{i\omega t}$ is the rotating phasor at 200



Then $V_L = i\omega LI$ is 90° ahead as $i = e^{i\pi/2}$ and $V_C = \frac{-i}{\omega C} I$

is 90° behind as $-i = e^{-i\pi/2}$


V_R is in phase with I

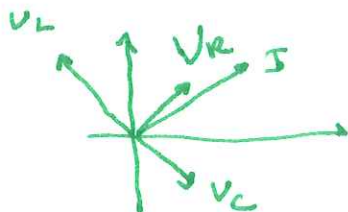

Note: All the rules from 200 which were derived via Kirchhoff's Laws now apply with these complex

"resistors" e.g. $Z_1 || Z_2 = \frac{Z_1 Z_2}{Z_1 + Z_2}$

$$f = 5000 \text{ Hz}$$

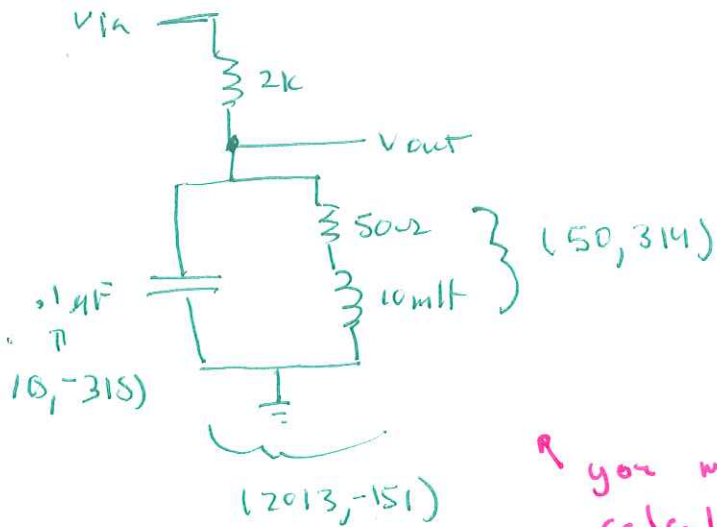



$$\frac{V_{out}}{V_{in}} = \frac{(2013, -151)}{2000 + (2013, -151)}$$

$$= (.5, -1.68E-2)$$

$$= .5 \angle -2.1^\circ$$

↑ magnitude ↑ phase

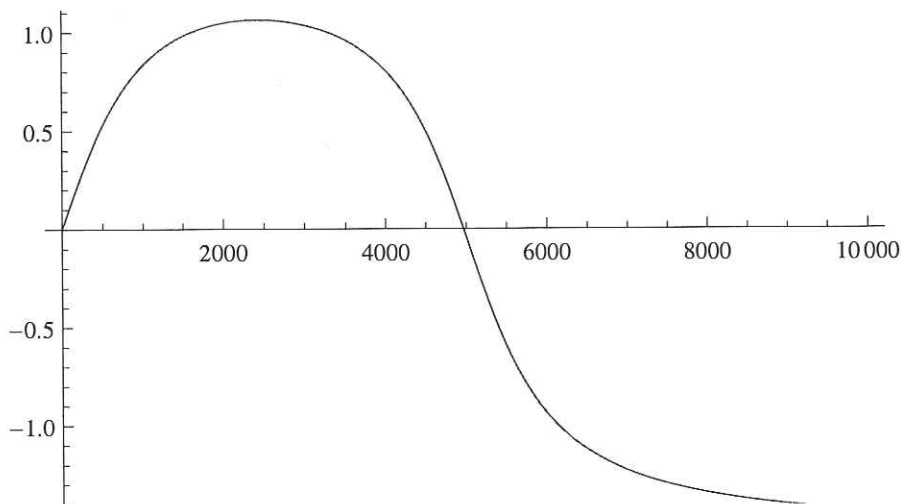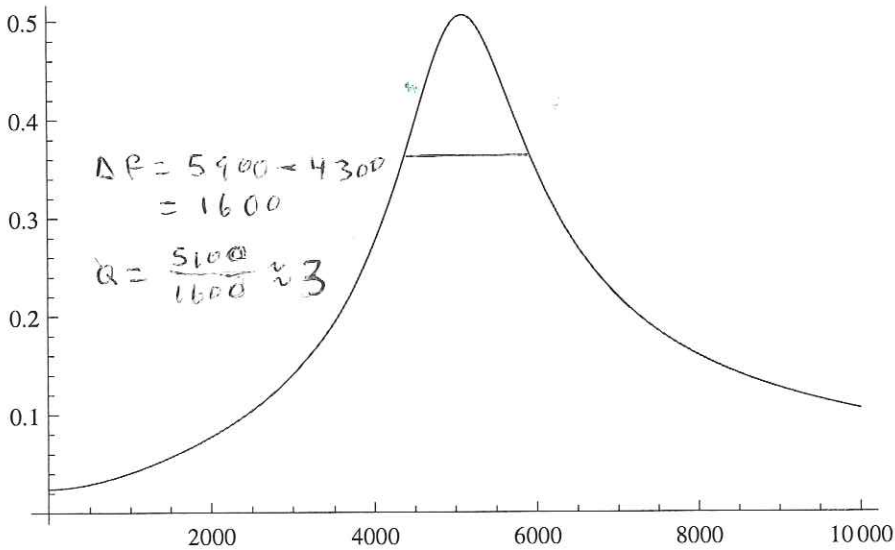↑ you must be able to do complex calculations like this using your calculator!




03/18/14

```

1 L=.01
2 c=10^(-7)
3 r=2000
4 f=5000
5 zC=1/(I 2 Pi f c)
6 zL=I 2 Pi f L + 50
7 z=zC zL/(zC+zL)
8 Out[7]= 2012.56 - 151.243 I
9
10 z/(2000+z)
11 Out[8]= 0.502272 - 0.0187606 I
12
13 {Abs[%],Arg[%]*180/Pi}
14 Out[9]= {0.502622, -2.13909}
15
16 ClearAll[f]
17 zC=1/(I 2 Pi f c)
18 zL=I 2 Pi f L + 50
19 z=zC zL/(zC+zL)
20 z/(2000+z)
21 Plot[Abs[%],{f,1,10000}]
22 Plot[Arg[%],{f,1,10000}]
23 GraphicsGrid[{{%15},{%16}}]
24 Export["tank.eps",%]
25

```

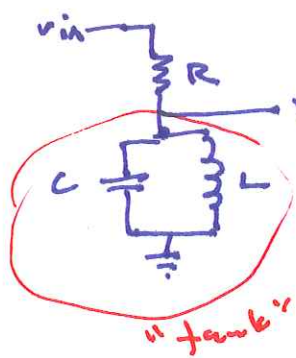

$$V_{out} = \frac{\frac{1}{i\omega C} \parallel i\omega L}{\frac{1}{i\omega C} \parallel i\omega L + R} V_{in} = \frac{\frac{L}{CR^2}}{\frac{L}{CR^2} + i\left(\omega \frac{L}{R} - \frac{1}{\omega RC}\right)} V_{in}$$

$\omega \rightarrow \infty \rightarrow +i\infty$
 $\omega \rightarrow 0 \rightarrow -i\infty$
 $\omega = \frac{1}{\sqrt{LC}} \rightarrow 0$

$$= \frac{A}{A + i\Delta} v_{in} \rightarrow 0 \quad \omega \rightarrow \infty$$

$$\rightarrow A \quad @ \omega_0$$

$$\rightarrow 0 \quad \omega \rightarrow 0$$

$$\left| \frac{V_{out}}{v_{in}} \right| = \frac{A}{\sqrt{A^2 + \Delta^2}}$$

Taylor Δ near ω_0 : $\Delta \approx 0 + \Delta' \Big|_{\omega_0} \Delta \omega$

$$\frac{L}{R} + \frac{1}{\omega^2 RC} = 2 \frac{L}{R}$$

$$\left| \frac{V_{out}}{v_{in}} \right| = \frac{A}{\sqrt{A^2 + \left(\frac{2L}{R} \Delta \omega\right)^2}}$$

find $\Delta \omega$ for $\frac{1}{2}$ $A = \frac{2L}{R} \Delta \omega = \frac{L}{RC}$

$$\Delta \omega = \frac{1}{2} \frac{1}{RC}$$

full width = $\frac{1}{RC}$

$$Q = \frac{\omega_0}{\text{full}} = \frac{1/\sqrt{LC}}{1/RC} = \sqrt{\frac{RC}{L}}$$

($\frac{1}{a}$ of series)

LRC series: $Z = R + i(\omega L - \frac{1}{\omega C})$

$$I_0 = \frac{V_0}{Z}; \quad |I_0| = \frac{V_0}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$

peak at $\omega L = \frac{1}{\omega C}$
 $\omega = \frac{1}{\sqrt{LC}}$


Taylor expand Δ @ $\omega = \frac{1}{\sqrt{LC}}$: $\Delta \approx 0 + \left(L + \frac{1}{\omega^2 C}\right) \Delta \omega$

$$= 2L \Delta \omega$$

half-width $\Delta \omega$ for $\frac{1}{\sqrt{2}}$ $\rightarrow 2L \Delta \omega = R \rightarrow \Delta \omega = \frac{R}{2L}$

$$Q = \frac{\omega_0}{\Delta \omega} = \frac{\frac{1}{\sqrt{LC}}}{\frac{R}{2L}} = \sqrt{\frac{L}{RC}}$$

Low Pass RC circuit:

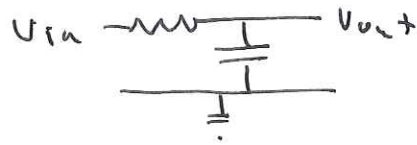



$$\frac{V_{out}}{V_{in}} = \frac{-j/\omega C}{R + \frac{-j}{\omega C}} = \frac{1}{\omega RC + 1}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{(\omega RC)^2 + 1}} = \begin{cases} \omega \ll \frac{1}{RC} \rightarrow 1 \\ \omega \gg \frac{1}{RC} \rightarrow \frac{1}{\omega RC} \end{cases}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{2}} \quad @ \quad \omega = \frac{1}{RC} \quad \leftarrow \text{"-3dB freq"}$$

$$\text{phase } \frac{V_{out}}{V_{in}} = \begin{cases} \omega \ll \frac{1}{RC} \rightarrow 0 \\ \omega = \frac{1}{RC} \rightarrow -\pi/4 \\ \omega \gg \frac{1}{RC} \rightarrow -\pi/2 \end{cases}$$

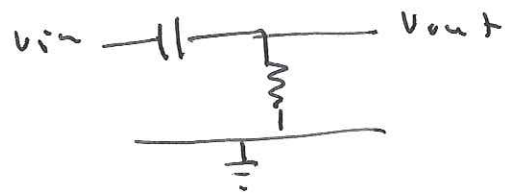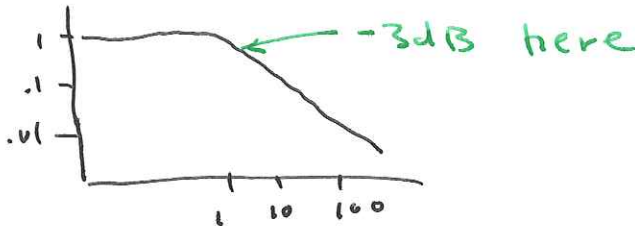Bode Plot: $\log\left(\frac{V_{out}}{V_{in}}\right)$ vs $\log(\text{freq})$



High Pass RC circuit:

$$\frac{V_{out}}{V_{in}} = \frac{R}{R - \frac{j}{\omega C}} = \frac{1}{1 - \frac{j}{\omega RC}}$$


$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{1 + \left(\frac{1}{\omega RC}\right)^2}} = \begin{cases} \omega \gg \frac{1}{RC} \rightarrow 1 \\ \omega = \frac{1}{RC} \rightarrow \frac{1}{\sqrt{2}} \\ \omega \ll \frac{1}{RC} \rightarrow \omega RC \end{cases}$$

Phase
0
+π/4
+π/2


Bode Plot



Low-pass

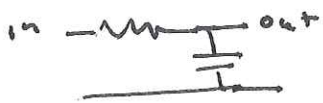
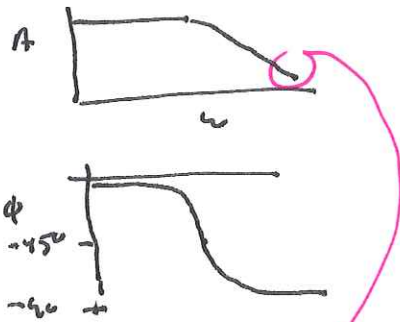
$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + i\omega RC}$$



$$V_{out} \approx 0$$

$$I = \frac{(V_{in} - V_{out})}{R}$$

$$= \frac{dQ}{dt} = C \frac{dV_{out}}{dt}$$


$$\Rightarrow \frac{dV_{out}}{dt} \approx \frac{1}{RC} V_{in}$$

$$\text{so } V_{out} \approx \frac{1}{RC} \int V_{in} dt$$


$$\frac{V_{out}}{V_{in}} \approx \frac{1}{i\omega RC}$$

$$V_{out} \approx \frac{1}{RC} \underbrace{\frac{1}{i\omega} V_{in}}_{\int V_{in} dt}$$

High-pass

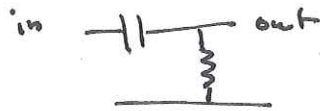
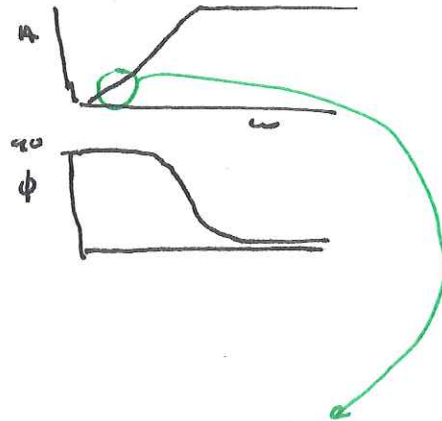
$$\frac{V_{out}}{V_{in}} = \frac{i\omega RC}{1 + i\omega RC}$$



$$V_{out} \approx 0$$

$$I = \frac{dQ}{dt} = C \frac{d}{dt} (V_{in} - V_{out})$$

$$V_{out} = IR \approx RC \frac{d}{dt} V_{in}$$

$$\frac{V_{out}}{V_{in}} \approx i\omega RC$$

$$V_{out} \approx RC \underbrace{i\omega V_{in}}_{\frac{d}{dt} V_{in}}$$