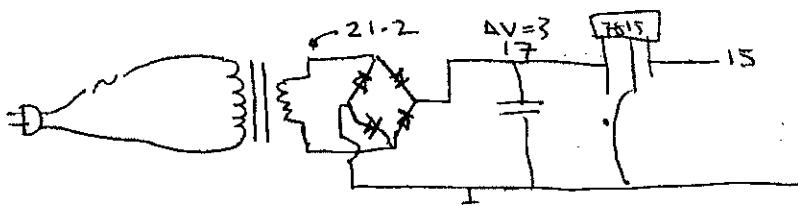


Select six (6) (out of seven) problems for grading.

1. Design and provide the schematic diagram for a +15 volt regulated power supply that will supply .75 A of current. Use a 7815 IC regulator, which is similar to the 7805 used in lab (e.g., it requires a 2 V "headroom"), but is designed for 15 volts. The full-current peak-to-peak ripple before the regulator should be 3 V. Record on your drawing the ratings for all components (e.g., transformer rms secondary voltage, C of capacitor, power dissipated in regulator at full current, rating for fuse on 120 V line cord, etc.)

i)



$$V_{rms} = \frac{21.2}{\sqrt{2}} = 15.0 \text{ V}$$

$$C = \frac{IT}{AV} = \frac{(75)(\frac{1}{120})}{3} = 2080 \mu\text{F}$$

$$7815 \text{ power} = (2 + 1.5)(.75) = 2.63 \text{ W}$$


$$\text{fuse} = \frac{(21.2)(.75)}{120}$$

$$= .133 \text{ A} \quad \text{use } \frac{1}{4} \text{ A}$$

switching Power Supplies → use "conductive" behavior of switched inductor to control output voltage
 → High Efficiency; high freq "noise"
 while not as simple as 7805 there are chips to make switches


→ single block DC → DC [even DC+ → DC-] converters

Boost (buck + switch)

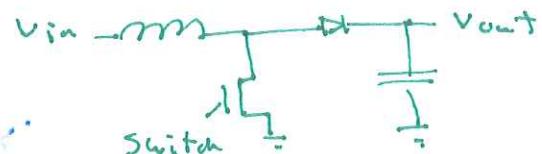

get a current goes to GND then switch it to Vout



Buck

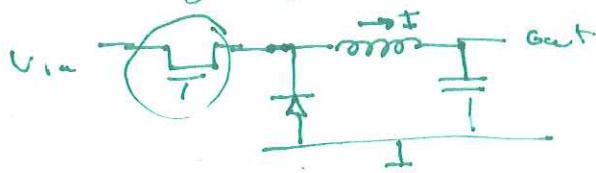

switch closed
 switch open
 diode conducts
 time.


Other diode circuits

Clamp

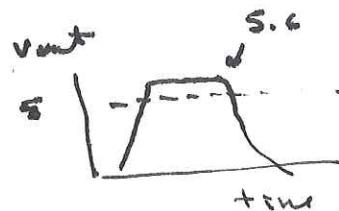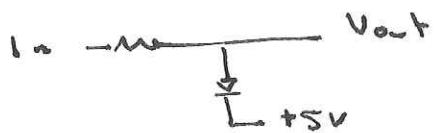


small signal limit $V_{in} - \frac{1}{L} \frac{dI}{dt}$ V_{out}
 $\pm .6V$


Voltage Multiplier (Cockcroft-Walton)

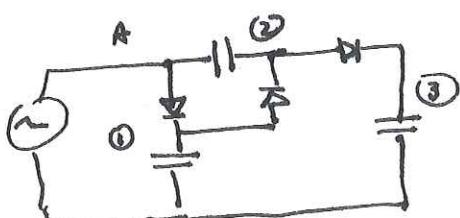

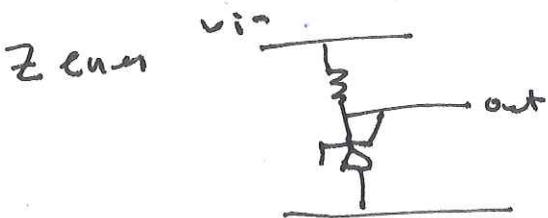- ① charges to V_0
- ② when A at $-V_0$ charges to $+V_0$
- ③ when A at $+V_0$ charges to $+3V_0$




Gate

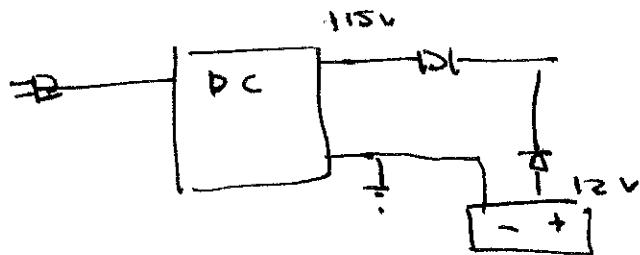

inductor



Transformers -

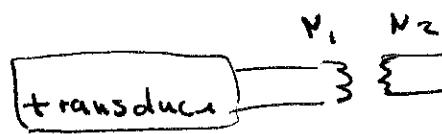

- power
- impedance match "amplify"
↳ $\text{eff. induct} = \left(\frac{N_2}{N_1}\right)^2 R_T$
- free up ground
- insert a signal at a "floater" potential