

Amplifiers: Two frequent examples

transducer  $\rightarrow$  amp  $\rightarrow$  measur

function generator  $\rightarrow$  amp  $\rightarrow$  power output

Typical Public Address System

Combines two: microphone  $\rightarrow$  amp  $\rightarrow$  speaker.

Claim: the important characteristics of amp are:

- ① input impedance, ② output impedance, ③ gain

Note: thevenin says the input terminals =  and we expect the voltage on inputs (with nothing connected) should be negligible. On output thevenin says same:  but here we expect big output voltages — typically the output (open circuit gain) will be a multiple of what is on the input terminals:  $V_{out} = A V_{in}$  "gain" perhaps in dB

Eg "glass electrode" transducer used to measure pH:




If this is attached to a typical DMU with input impedance  $\sim 1\text{M}\Omega$

the measured voltage will be  $\frac{1}{101} \cdot 5 = .005$



is a huge error!

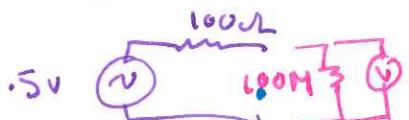
Eg — on the other hand in Zoo you measured (in the Helmholtz lab) AC magnetic fields with a little "pickup" coil whose impedance  $< 100\Omega$



$$\text{measure: } \frac{100 \times 10^6}{100 + 100} \cdot 5V = .5V$$


Remarks: A low impedance transducer like this is a good candidate for an "impedance matching" transformer — using a transformer we could boost the voltage 10X and change the impedance  $100\Omega \rightarrow 10\text{k}\Omega$ .  $10\text{k}\Omega$  is still negligible compared to  $1\text{M}\Omega$  so we would still get essentially 100% voltage transfer. However in the Zoo lab there was no reason to boost voltage as they were already large enough to easily measure.

Generic Amp:

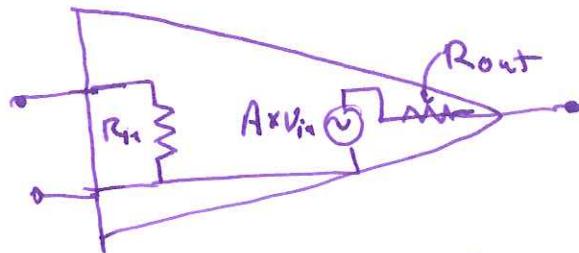


Remarks: it turns out that  $R_{in} \rightarrow \infty$  &  $R_{out} \rightarrow 0$  are good characteristics of amp.

Eg:

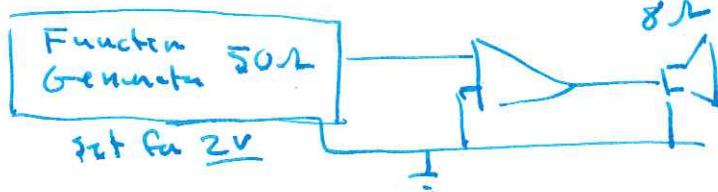

$$\begin{aligned} \text{say: } R_{in} &= 150\Omega \\ R_{out} &= 16\Omega \\ A &= 30 \text{ dB} \\ &= 10^{\frac{30}{20}} \\ &= 31.6 \end{aligned}$$
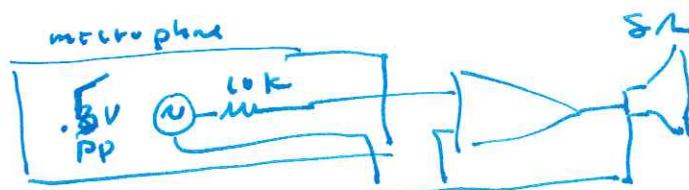
$$V_{out} = \left( \frac{150}{200} \cdot 2V \right) \times 31.6 \times \left( \frac{8}{16} \right) = 15.8$$



$$\begin{aligned} R_{in} &= 1M\Omega \\ R_{out} &= 1\Omega \\ A &= 30 \text{ dB} \end{aligned}$$

$$V_{out} = \left( \frac{10^6}{10^6 + 10^4} \cdot \frac{0.5}{2f_z} \right) \times 31.6 \cdot \left( \frac{8}{1} \right) = 4.9V$$


In lab we will commonly measure  $R_{in}$ ,  $R_{out}$  &  $A$ .

Can measure  $R_{out}$  as was discussed RE Thevenin

$$R_{out} = \frac{R}{\frac{V}{\Delta V} - 1} \quad \text{where } \Delta V \text{ is the "drop" from}$$

usraj  $\rightarrow$  load R.

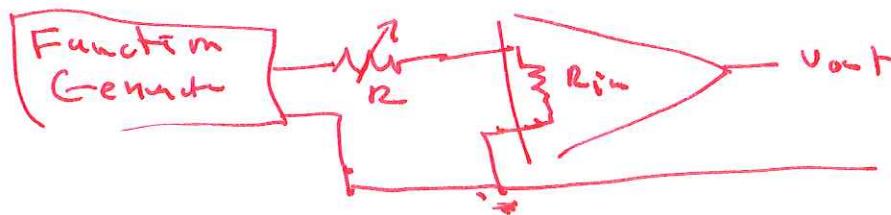IF  $R_{in} \gg$  Function generator 50Ω output impedance.




$V_{out}$  will be  $\pm \frac{1}{2}$  normal if  $R = R_{in}$

$$\text{In general: } R_{in} = R \left( \frac{V}{\Delta V} - 1 \right)$$

An ideal op-amp:  $R_{in} = \infty$ ,  $R_{out} = 0$ ,  $A = \infty$

Eg

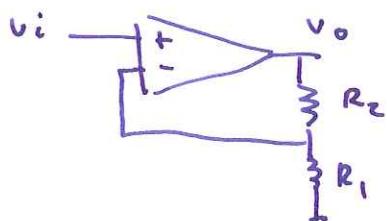

$$V_- = \frac{R_1}{R_1 + R_2} V_o$$

$$A(V_+ - V_-) = V_o$$

$$A\left(V_+ - \frac{R_1}{R_1 + R_2} V_o\right) = V_o$$


$$gain = \frac{1}{\left(\frac{1}{A} + \frac{1}{1 + R_2/R_1}\right)}$$

$$\xrightarrow{A \rightarrow \infty} 1 + \frac{R_2}{R_1}$$

$$Vi = V_+ = \left(\frac{1}{A} + \frac{R_1}{R_1 + R_2}\right) V_o$$

$$\frac{Vi = V_o}{\left(\frac{1}{A} + \frac{1}{1 + R_2/R_1}\right)}$$

Eg

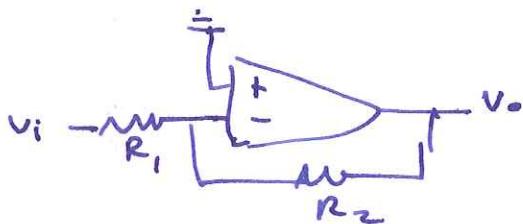

$$\frac{V_+ - V_-}{R_1} = \frac{V_- - V_o}{R_2}$$

$$V_o = -AV_-$$

$$\begin{aligned} \frac{Vi}{R_1} &= \left(\frac{1}{R_1} + \frac{1}{R_2}\right) V_- - \frac{V_o}{R_2} = -\frac{1}{R_2} \left[ -\left(1 + \frac{R_2}{R_1}\right) V_- + V_o \right] \\ &= -\frac{1}{R_2} \left[ \left(1 + \frac{R_2}{R_1}\right) \frac{1}{A} + 1 \right] V_o \end{aligned}$$

$$\frac{-\frac{R_2}{R_1} Vi}{\left(1 + \frac{1}{A} \left(1 + \frac{R_2}{R_1}\right)\right)} = V_o$$

$$gain = \frac{-R_2/R_1}{\left(1 + \frac{1}{A} \left(1 + \frac{R_2}{R_1}\right)\right)} \rightarrow -\frac{R_2}{R_1}$$

Easy to remember Golden Rules

- ① No input currents
- ②  $V_+ = V_-$  "Virtual ground"