
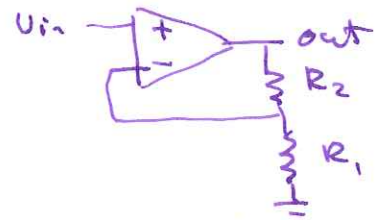


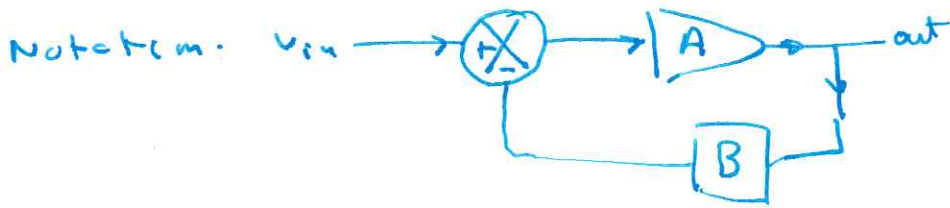Feedback - some notation & algebra to show that "things get better if you 'throw away' gain"



$$A(V_{in} - B V_{out}) = V_{out}$$

$$V_{in} = (B + \frac{1}{A}) V_{out}$$

$$\frac{1}{(B + \frac{1}{A})} = \frac{V_{out}}{V_{in}} \leftarrow \text{circuit gain}$$


Remark: not related to transistor  $\beta$

in contrast to op amps gain

$$\frac{1}{1 + \frac{1}{AB}} \leftarrow \frac{R_1 + R_2}{R_1} = 1 + R_2/R_1$$

sometimes called the "loop gain"  $A_L$

alternative form

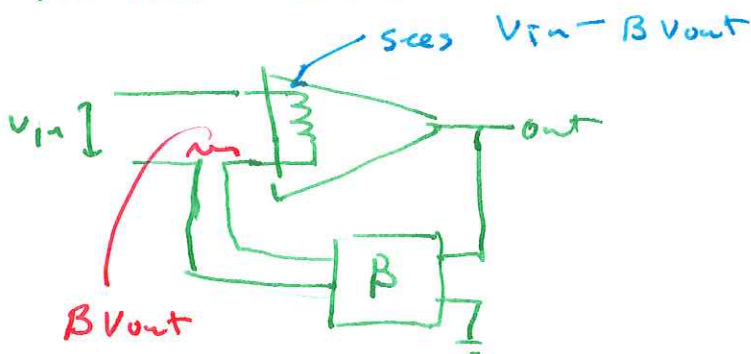


Note: the above is negative feedback; positive

feedback  $\rightarrow$  expo growth and is generally a bad idea.

The invention of negative feedback amps is attributed to Harold Black - EE works at Bell Labs - 1927

Output Impedance - a trick to mathematically calculate a circuit output impedance. Consider  $V_{in} = 0$  ("ground the input") thro (in theory) would produce  $V_{out} = 0$  but we (mathematically) apply an external voltage  $V$  to the output & calculate the resulting current,  $I$ . The circuit's output impedance is the  $V/I$ .

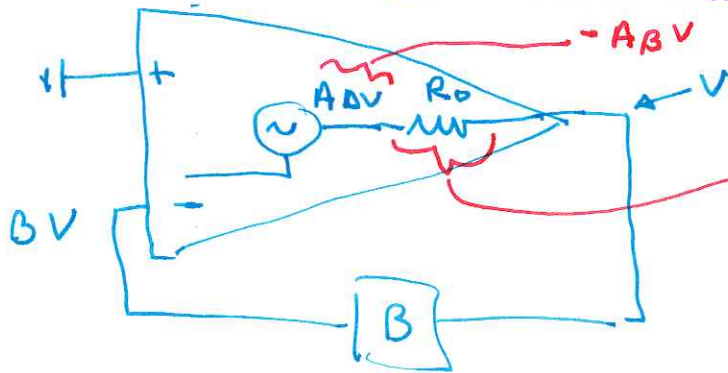(In an experimental situation we'd more like remove current from amp - by applying a load - and measure the resulting voltage drop - the circuit's  ~~$Z_{out}$~~   $Z_{out}$  would then be  $\frac{\Delta V}{I}$ )





$$\text{voltage drop} = V - -ABV = (1 + AB)V$$

$$\text{current} = \frac{\text{voltage drop}}{R_o}$$

$$Z_o = \frac{V}{I} = \frac{R_o}{(1 + AB)} \leftarrow \text{note reduced from what was probably a small } R_o \text{ to begin with.}$$

$$I = \frac{(1 + AB)V}{R_o}$$

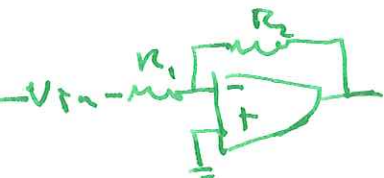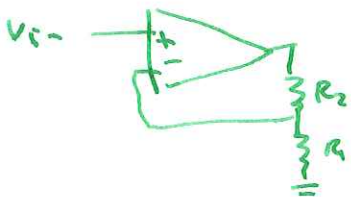Slight practical consideration - in real circuit feedback network  $B$  it self would draw some current




in both cases an addition current flow of  $\frac{V}{R_1 + R_2}$  happens - i.e. must add this current to above

$$\text{result: } Z_{out} = \frac{R_o}{(1 + AB)} \parallel R_1 + R_2$$

this should be much smaller than  $R_1 + R_2$  so

$$Z_o \approx \frac{R_o}{(1 + AB)}$$

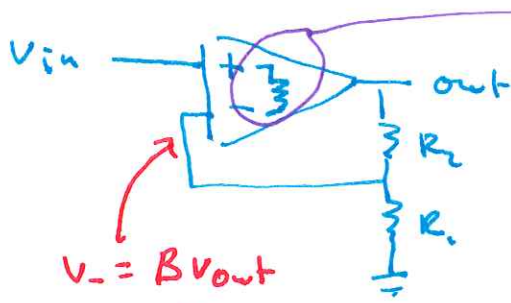Input Impedance (Note: for inverting amp circuit this will be  $R$  which is not huge — say  $10\Omega$ )



$$V_- = BV_{out}$$

$$B = \frac{R_1}{R_1 + R_2}$$

$$I = \frac{V_{in} - BV_{out}}{R_{in}} = \frac{V_{in}}{R_{in}} (1 - BG)$$


$$G = \frac{V_{out}}{V_{in}} = \frac{A}{1 + BA}$$

$$\frac{V_{in}}{I} = \frac{R_{in}}{(1 - BG)} = \frac{R_{in}}{(1 - \frac{AB}{1 + BA})}$$

$$= \underline{R_{in}(1 + BA)}$$

an intrinsically large value increased even more.

# Inverting Amp: Input/Output Impedance

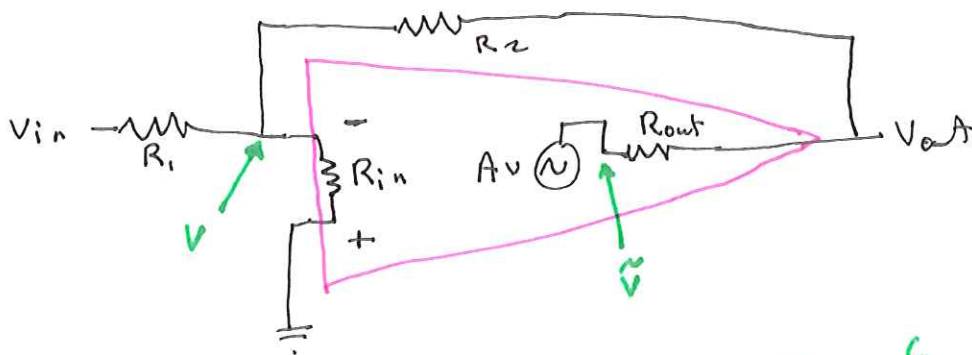

open loop gain  $A$

closed loop gain  $G = \frac{V_o}{V_i}$

loop gain  $AB$

$$B = \frac{R_1}{R_1 + R_2}$$

$$V = \frac{V_i}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_{in}}} = -\frac{1}{A} V_o \Rightarrow \frac{\frac{1}{R_1} + \frac{1}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_{in}}} = -\frac{G}{A}$$

$$\text{math} \Rightarrow G = - \left( \frac{A R_2 R_{in}}{R_1 R_2 + R_{in} R_1 (A+1) + R_{in} R_2} \right)$$

$$\xrightarrow{R_{in} \rightarrow \infty} \frac{-A R_2}{R_1 (A+1) + R_2} = \frac{-A (1-B)}{AB+1} \xrightarrow{A \rightarrow \infty} \frac{-(1-B)}{B} = -\frac{R_2}{R_1}$$

$$I_{in} = \frac{(V_{in} - V)}{R_1} = \frac{(V_{in} + \frac{1}{A} V_{out})}{R_1} = \frac{V_{in} (1 + \frac{G}{A})}{R_1}$$

$$\frac{R_1}{(1 + G/A)} = \frac{V_{in}}{I_{in}} = R_1 + R_{in} \parallel \frac{R_2}{(1+A)} \quad (\text{math})$$

Ignore  $R_{in}$ , Ground  $V_{in}$ , Apply voltage  $V_o$  to output, measure inflowing current  $I_o$

$$V = \frac{V_o}{\frac{1}{R_1} + \frac{1}{R_2}}; \quad -Av = \tilde{V}$$

$$I_{out} = \frac{(\tilde{V} - V_o)}{R_{out}} = \frac{-V_o}{R_{out}} \left\{ \frac{A}{R_2} + 1 \right\}$$

$$\left\{ \frac{A/R_2}{1/R_1 + 1/R_2} + 1 \right\} \frac{R_{out}}{R_2 + R_1} = \frac{-V_o}{I_{out}} = \frac{R_{out}}{AB+1}$$

$$\frac{A R_1}{R_2 + R_1} + 1 = AB + 1$$

Solve[(1/R1+G/R2)/(1/R1+1/R2+1/Ri)=-G/A,G]

Out[1]= {{G -> -( $\frac{A R_2 R_i}{R_1 R_2 + R_1 R_i + A R_1 R_i + R_2 R_i}$ )}}

R1/(1+G/A) /. First[%]

Simplify[%]

Out[3]=  $\frac{R_2 R_i + R_1 (R_2 + R_i + A R_i)}{R_2 + R_i + A R_i}$

R1+Ri R2/(1+A)/(Ri+R2/(1+A))

Simplify[%]

Out[5]=  $\frac{R_2 R_i + R_1 (R_2 + R_i + A R_i)}{R_2 + R_i + A R_i}$

# Vocabulary

AC or DC amp

bandwidth (f-3dB) ; "mid band" gain

inverting / non inverting

clipping

differential amp (out =  $A_d(V_+ - V_-)$ )

- common mode gain (where  $V_+ = V_- = V_{cm}$ )  $A_c$

- differential gain (where  $V_+ - V_- = V_{dm}$ )  $A_d$

- common mode rejection ratio =  $\frac{A_d}{A_c}$  (often in dB)

noise - note odd unit  $\mu V / \sqrt{Hz}$  or  $PA / \sqrt{Hz}$

For op-Amps

Gain - Bandwidth product [note compensated op-Amps]


slew rate

"rail-to-rail" or limited out put voltage swing

input offset voltage - "as if"


input bias current

open loop gain

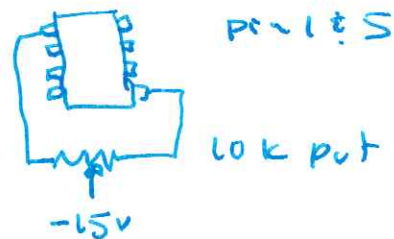


Current sources — supplies a fixed current — if  $R$  is big a big voltage results; if  $R$  small  $\rightarrow$  small voltage.  
 Every current source has its limits — if  $R$  is too big will not be able to produce required voltage.

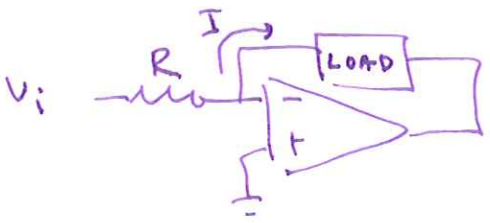[contrast: voltage sources supply fixed voltage — if  $R$  is big a small current results; if  $R$  small  $\rightarrow$  large current.  
 Every voltage source has its limits — if  $R$  is too small will not be able to produce required current]




$$I = \frac{V_i}{R}$$

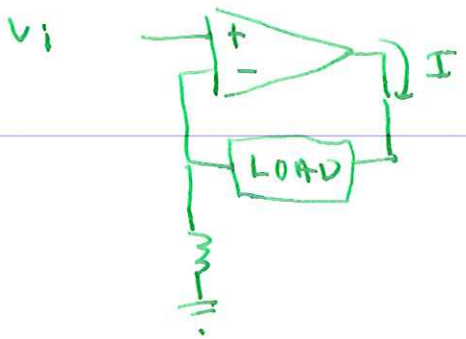

$$I = \frac{V_i}{R}$$

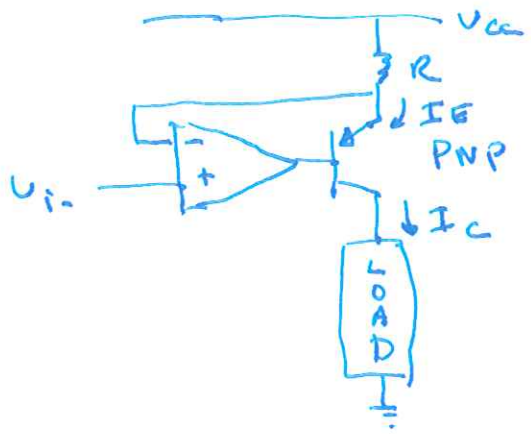Always require a "floating" load — often want load connected to ground. Also always limited by current output of op-amp  $\rightarrow$  a few mA



Since  $I_E \approx I_C$

$$I_C \approx \frac{V_{CC} - V_{in}}{R}$$