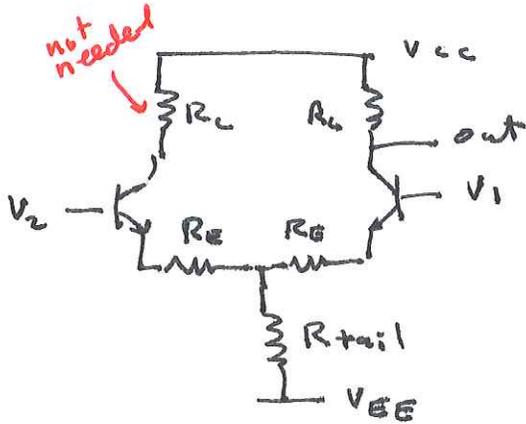


Differential Amp - long tail pair



$$\Delta V_2 = -V$$

Differential gain: $\Delta V_o = +V$

the current thru tail in this symmetric situation is unchanged so the top of tail is at a fixed voltage - it's just like common emitter amp

$$v \rightarrow \Delta V_1 \quad \frac{\Delta \text{out}}{\Delta V_1} = -\frac{R_C}{r_e + R_E}$$

But for differential mode: $\Delta(V_1 - V_2) = 2V$

$$\text{so } \frac{\Delta \text{out}}{\Delta(V_1 - V_2)} = \frac{\Delta \text{out}}{2V} = -\frac{R_C}{2(r_e + R_E)}$$

Common Mode: $\frac{\Delta V_2}{\Delta V_1} = +V$ - the current thru tail

is doubled \rightarrow seems like $2 \times R_{\text{tail}}$ otherwise just like common



$$\frac{\Delta \text{out}}{V} = \frac{-R_C}{2R_{\text{tail}} + R_E + r_e}$$

$$\text{CMRR} = \frac{\text{diff gain}}{\text{common gain}} = \frac{2R_{\text{tail}} + R_E + r_e}{R_E + r_e}$$

Plan: using a current source for R_{tail} will hugely reduce common mode gain

use a "current mirror" for R_C - has property that for differential signals $R \rightarrow \infty$ but for common mode signals $R \rightarrow 0$

Current Sources

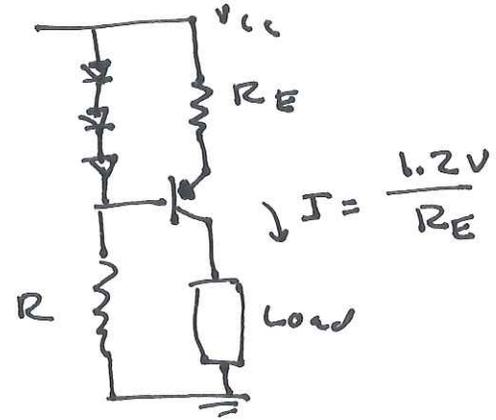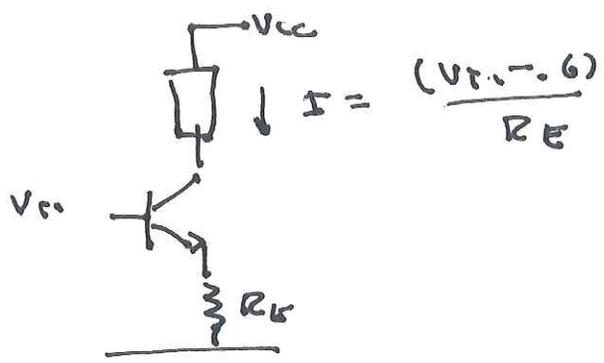

Early Effect ($10^{-4} = h_{re}$) \rightarrow V_{CE} affects the on voltage of BE diode.

Temp also affects V_{BE}
Compliance? Bias circuit?

Current mirrors \leftarrow Rule #3 devices

