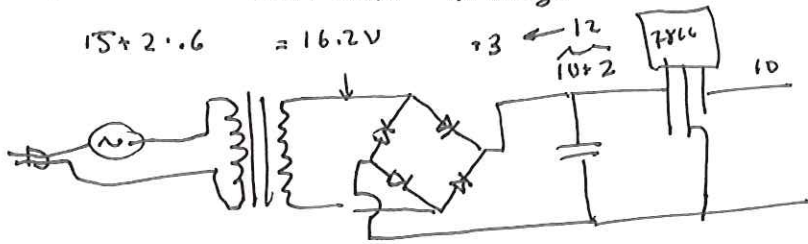


1) My choice: Full wave bridge

$$15 + 2 \cdot 0.6 = 16.2 \text{ V}$$



$$C \cdot V = Q = I_T \cdot \frac{1}{120}$$

$$C = \frac{\frac{1}{2} \cdot \frac{1}{120}}{3} = 1.39 \text{ mF}$$

flux:  $120 \cdot I = 16.2 \cdot \frac{1}{2}$   
 $I = .0675 \text{ A}$   
 (brass)

$$\text{RMS: } \frac{16.2}{\sqrt{2}} = 11.5 \text{ V}$$

$$\text{Power} = \left(\frac{3}{2} + 2\right) (1.5) = 1.75 \text{ W}$$

2)  $X_L = \omega L = 2\pi \cdot 3500 \cdot .01 = 220 \Omega$   
 $X_C = \frac{1}{\omega C} = \frac{1}{2\pi \cdot 3500 \cdot 10^{-7}} = 455 \Omega$

$$\frac{1}{Z_T} = j\omega C + \frac{1}{i\omega L + R}$$

$$Z_T = 440 + 14.5i$$

$$439.4 \quad 14.2$$

$$= 440 \angle 1.9^\circ$$

↑  
V leads!

$$I = \frac{V}{Z}$$

$$= \frac{5}{440} \angle -1.9^\circ$$

↑  
11.4 mA

$$I_{\text{left}} = \frac{V}{i\omega L + R} = \frac{5}{220 + 220i}$$

$$= (11.4 - 11.4i) \text{ mA}$$


$$= 16.1 \text{ mA} \angle -45^\circ$$

↑  
I = (A)

$$V_1 = |I_{\text{left}}| \cdot |\omega L| = 16.1 \cdot 220 = 3.54 \text{ V}$$


↑ same for  $V_2$  as  $\omega L = R$

(3)

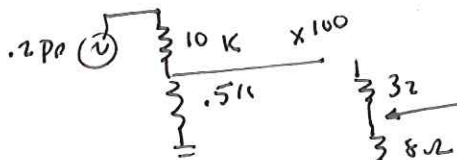


$$\frac{8}{40} \cdot 100 \cdot \frac{.5}{10.5} \left(\frac{.2}{2\sqrt{2}}\right) = 67.3 \text{ mV}$$
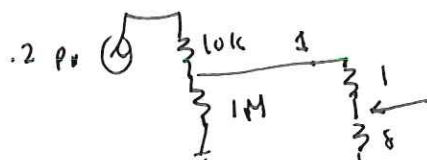
$$\text{Power} = \frac{V_{\text{rms}}^2}{R} = \frac{(67.3 \text{ mV})^2}{8} = .567 \text{ mW}$$



$$\frac{8}{9} \left(\frac{.2}{2\sqrt{2}}\right) = 62.9 \text{ mV}$$
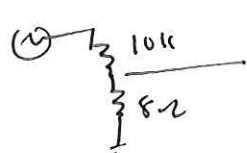
$$\text{Power} = \frac{V_{\text{rms}}^2}{R} = .494 \text{ mW}$$



$$\frac{8}{10,008} \left(\frac{.2}{2\sqrt{2}}\right) = 56.5 \mu\text{V} \rightarrow \text{Power} = 4 \times 10^{-10} \text{ W}$$

