

$$I = \frac{12}{6} = 2 \text{ mA}$$

$\frac{V}{kR} = m A$   
every resistor

$$V_1 = IR_1 = 2 \text{ V}$$

$$V_2 = IR_2 = 4 \text{ V}$$

$$V_3 = IR_3 = \frac{6 \text{ V}}{12 \text{ V}}$$

$$P = \frac{V^2}{R} = \frac{12^2}{6 k\Omega} = 24 \text{ mW}$$



$$V = 12 \text{ V} \leftarrow \text{emv resoh}$$

$$I_1 = \frac{V}{R_1} = 12 \text{ mA}$$

$$I_2 = \frac{V}{R_2} = 6 \text{ mA}$$

$$I_3 = \frac{V}{R_3} = \frac{4 \text{ mA}}{22 \text{ mA}}$$

$$P = V \cdot I = 12 \cdot 22 \text{ mA}$$

$$\rightarrow 264 \text{ mW}$$

$$5) \quad 5 \parallel 3 \parallel 2 = \frac{1}{\frac{1}{5} + \frac{1}{3} + \frac{1}{2}} = .9677$$

current thru 7:  $\frac{15}{7+} = 1.883 \text{ mA}$

volt across 7:  $7 \cdot \downarrow = 13.18 \text{ V} \Rightarrow 15 - 13.18 \text{ across } 5, 3, 2$   
 $= 1.822 \text{ V}$

current thru 5:  $\frac{1.822}{5} = .364 \text{ mA}$

$$3 = \frac{1.822}{3} = .6073$$

$$2 = \frac{1.822}{2} = \frac{.9104}{1.883 \text{ mA}}$$

current thru 11 =  $\frac{15 \text{ V}}{11} = 1.364 \text{ mA}$

$$6) \quad P = \frac{V^2}{R} \Rightarrow R = \frac{V^2}{P} = \frac{120^2}{160} = 144 \Omega$$

$$11) \quad V = A \sin(\omega t + \phi) + B$$

$$a) \quad \text{DC off} = B = 1 \text{ V}$$

$$b) \quad \text{amp} = A = 5 \text{ V}$$

$$c) \quad \text{peak} = A + B = 6 \text{ V}$$

$$d) \quad \text{p-p} = 2A = 10 \text{ V}$$

$$e) \quad \text{rms} = \frac{A}{\sqrt{2}} = 3.54 \text{ V}$$

$$f) \quad V = A \sin(\phi) + B = 5 \sin(.45^\circ) + 1 \\ = 3.175 \text{ V}$$

$$g) \quad f = \frac{\omega}{2\pi} = \frac{1000}{2\pi} = 159 \text{ Hz}$$

$$h) \quad T = \frac{1}{f} = 6.28 \text{ ms}$$

$$13) \quad I = \frac{V}{X_L} = \frac{V}{\omega L} \xrightarrow[2\pi \cdot 60]{120V} \Rightarrow L = \frac{120V}{20\pi \cdot 2\pi \cdot 60} = 15.9 \text{ mH}$$

$$= \frac{V}{X_C} = \omega C V \Rightarrow C = \frac{I}{\omega V} = \frac{20A}{2\pi \cdot 60 \cdot 120} = 442 \mu F$$

zero power consumed -  $V \neq I$   $90^\circ$  out-of-phase  $\angle VI = 0$

i.e. phase angle  $= 90^\circ$  &  $\cos(90^\circ) = 0$

$$14) \quad Z_T = R + Z_C + Z_L = 1000 \Omega + i \left( \frac{\omega_0 Z}{2\pi \cdot 1000} - \frac{1}{\omega C} \right) \xrightarrow[6.28 \times 10^3]{1.26K} 1.59K$$

$$= (1, -0.335) K$$

$$I = \frac{10}{Z} = (8.99, 3.01) \xrightarrow{mA} 9.48 \angle -32^\circ \text{ mA}$$

phase diff + inv

$$V_R = R I = (8.99, 3.01) V$$

$$= 9.48 \text{ V rms}$$

$$V_L = j \omega L \xrightarrow{R} (8.99, 3.01) = (-3.78, 11.3) = 11.9 \angle 109^\circ V$$

$$2\pi \cdot 1000 \cdot 2 \Rightarrow 1.257 \text{ k}\Omega$$

$$V_C = -\frac{j}{\omega C} (8.99, 3.01) = (4.79, -14.3) = 15.1 V \angle -71^\circ V$$

water to add all:  $(10, 0)$  = source!

17) High Pass



$$f_{-3dB} = \frac{1}{2\pi RC} = 1.59 \text{ kHz}$$

$$a) \quad I = \frac{V}{R - \frac{j}{\omega C}} = \frac{V/R}{1 - \frac{j}{\omega RC}} = \frac{V/R}{1 - j \frac{f_{-3dB}}{f}} = \frac{1 \text{ mA}}{1 - j \frac{1.59}{1}}$$

phase reverse  
V\_in + V\_out

$$= \frac{1 \text{ mA}}{1.88 \angle -58^\circ} = .532 \text{ mA} \angle +58^\circ$$

$$b) \quad V_R = IR = \frac{V}{1 - j \frac{f_{-3dB}}{f}} = \frac{10V}{1 - j \frac{1.59}{1}} = \frac{10V}{1.88 \angle -58^\circ} = 5.32 V \angle +58^\circ V$$

$$c) \quad V_C = I \left( \frac{-j}{\omega C} \right) = \frac{V}{1 - j \frac{f_{-3dB}}{f}} \left( -j \frac{f_{-3dB}}{f} \right) = -j \frac{10 \left( \frac{1.59}{1} \right)}{1 - j \frac{1.59}{1}} = \frac{15.9 \angle -90^\circ}{1.88 \angle -58^\circ}$$

$$= 8.46 \angle -32^\circ V$$

18) Low Pass

$$f_{-3dB} = \frac{1}{2\pi RC} = 468 \text{ Hz} = .468 \text{ kHz}$$

$$50 \quad 6.8 \times 10^{-6}$$

$$\frac{1}{2\pi RC} = \frac{f_{-3dB}}{\varphi}$$

$$I = \frac{V}{R - \frac{j}{\omega C}} = \frac{V/R}{1 - \frac{j}{\omega RC}} = \frac{V/R}{1 - j \frac{f_{-3dB}}{f}} = \frac{1/50}{1 - j \frac{468}{1}}$$

$$= \frac{.1/50}{1.104 \angle -25^\circ} = 1.81 \text{ mV} \angle +25^\circ$$

$$V_R = I \cdot 50 = .0906 \text{ V}$$

$$V_C = \frac{-j}{\omega C} I = \frac{-j}{\omega RC} \frac{V}{1 - \frac{j}{\omega RC}} = -j \frac{f_{-3dB}}{f} \frac{V}{1 - \frac{j}{\omega RC}}$$

$$= \frac{(.1)(.468) \angle -90^\circ}{1.104 \angle -25^\circ} = .6424 \angle -65^\circ \checkmark$$

angle between  
V<sub>out</sub> & V<sub>in</sub>

23)

$$P = I^2 R \Rightarrow R = 14.6 \Omega$$

$$V_R = (1.46)(.37) = 54 \text{ V}$$

$$I = \frac{V}{R + j\omega L} \Rightarrow |I| = \frac{|V|}{\sqrt{R^2 + \omega^2 L^2}} \quad \text{or} \quad R^2 + \omega^2 L^2 = \frac{V^2}{I^2}$$

$$\omega^2 L^2 = \frac{V^2}{I^2} - R^2$$

$$L = \frac{1}{\omega} \sqrt{\frac{V^2}{S^2} - R^2}$$

$$= \frac{1}{2\pi \cdot 50} \sqrt{\left(\frac{240}{.37}\right)^2 - 146^2}$$

$$63.2$$

$$= \boxed{2.01 \text{ H}}$$

25) Require  $(R + j\omega L) \parallel \frac{-j}{\omega C}$  to be real

$$Z_{\text{net}} = \frac{(R + j\omega L)(-\frac{j}{\omega C})}{R + j(\omega L - \frac{1}{\omega C})} = \frac{\frac{R}{C} - j \frac{R}{\omega C}}{R + j(\omega L - \frac{1}{\omega C})}$$

$$= R^2 \left( \frac{\frac{L}{R^2 C} - j \frac{1}{\omega R C}}{R \left( 1 + j \left( \frac{\omega L}{R} - \frac{1}{\omega R C} \right) \right)} \right) = \frac{\frac{L}{C} \left( 1 - j \frac{R}{\omega L} \right)}{R \left( 1 + j \left( \frac{\omega L}{R} - \frac{1}{\omega R C} \right) \right)}$$

If this is going to be real top & bottom must have same phase  $\Rightarrow \frac{R}{\omega L} = \frac{1}{\omega R C} - \frac{\omega L}{R}$

$$\omega = 2\pi \cdot 5$$

$$L = 2$$

$$R = 146 \Omega$$

$$\frac{R}{\omega L} + \frac{\omega L}{R} = \frac{1}{\omega R C}$$

$$\omega R C = \frac{1}{\frac{R}{\omega L} + \frac{\omega L}{R}}$$

$$C = \frac{\frac{1}{\omega R}}{\frac{R}{\omega L} + \frac{\omega L}{R}} = \frac{\frac{1}{2\pi \cdot 50 \cdot 146}}{\frac{2\pi \cdot 50 \cdot 2}{146}} = 4.3$$

$$= \frac{21.8 \mu F}{4.536} = 4.81 \mu F$$

$$1000 = 1K$$


$$26) Z = R + j(\omega L - \frac{1}{\omega C}) = 75 + j \left( 10^5 \cdot 10^{-2} - \frac{1}{10^{-8} \cdot 10^5} \right)$$


$$= 75 \Omega$$

$$V_L = X_L \cdot I = 1K \Omega \cdot \frac{5}{75} = 66.7 V \quad (\text{resonance})$$

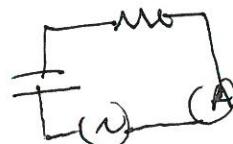(A) shorts out L so circuit is


$$I = \frac{V}{\sqrt{R^2 + (\frac{1}{\omega C})^2}} = \frac{V}{\sqrt{75^2 + 1000^2}} \approx 5 \text{ mA}$$



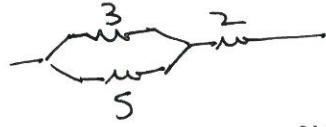28) (A)  $V_{TH} = \frac{5}{8} \cdot 12 = 7.5 \text{ V}$   $R_{TH} =$  

$$3/15 + 2 = \underline{3.875 \text{ k}\Omega}$$


(B)  $V_{TH} = \Delta V = \left( \frac{1}{2.5} - \frac{3}{5} \right) 15 \text{ V}$   
 $= \left( \frac{2}{5} - \frac{3}{2} \right) 15 \text{ V} = -\frac{1}{5} \cdot 15 = \frac{-3}{5} \text{ V}$  not depends  
on which terms  
you call "ref"

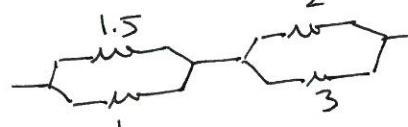$R_{TH} =$  

$$1/1.5 + 2/3 = 1.8 \text{ k}\Omega$$

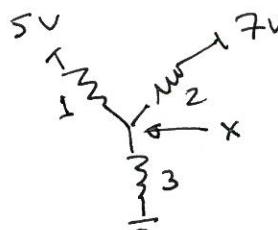(C)  $R_{TH} \rightarrow \text{easy: } 1 \parallel 2 \parallel 3 = \underline{546 \text{ k}\Omega}$

$V_{TH} \rightarrow \text{harder - K's Law or I'll use node formula}$



$$\frac{(5-x)}{1} + \frac{(7-x)}{2} + \frac{(10-x)}{3} = 0$$

$$5 + \frac{7}{2} + 0 = \left( \frac{1}{1} + \frac{1}{2} + \frac{1}{3} \right) x$$


$$\frac{5 + \frac{7}{2}}{\left( \frac{1}{1} + \frac{1}{2} + \frac{1}{3} \right)} = x = \underline{4.63 \text{ V}}$$

29)  $R_{TH} = 2 \parallel 4 = 1.33 \text{ k}\Omega$

find  $V_{TH}$  from current =  $\frac{5 \text{ V}}{6 \text{ }\Omega} \rightarrow V_{TH} = 4 \cdot \frac{5}{6} = 3.333$



charges  $\rightarrow$  current =  $\frac{\Delta V = 2 \parallel 3}{R = 4/3} = \frac{7/3}{4/3} = \frac{7}{4} \text{ mA}$

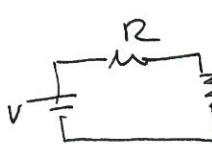1.11: 

$$P_{\text{Power}} = I^2 R = \left[ \frac{V}{(R+x)} \right]^2 \cdot x = \frac{V^2}{R} \cdot \frac{x}{(1+y)^2}$$

generic

$f(y) = \frac{y}{(1+y)^2}$

$f'(y) = \frac{1}{(1+y)^2} - \frac{2y}{(1+y)^3} = \frac{1+y-2y}{(1+y)^3} = \frac{1-y}{(1+y)^3}$

$= 0 \leftrightarrow y = 1$

