

Problems: POF : 34-37, 32, 41, 50
 1.25 p46
 1.20 p33 chapt

$$(32) \quad Z_C = \frac{1}{j\omega C} = -j 1.941 \text{ k}\Omega$$

$$2\pi \cdot 10^3 \cdot 0.82 \times 10^{-3}$$

$$Z_L = j \omega \frac{R}{79 \times 10^{-3}} = j 0.4964 \text{ k}\Omega$$

$$V_A = \frac{Z_C}{R + Z_C} V_{in} = \frac{(0.1 - j 1.941)}{(1.1 - j 1.941)} \mid 2 = (0.8889 \angle -27.3^\circ) \mid 2$$

$$V_B = \frac{Z_C}{R + Z_C} V_{in} = \frac{(0.1 + j 0.64)}{(1.1 - j 0.64)} \mid 2 = (0.4446 \angle 63.6^\circ) \mid 2$$

$$= \frac{0.336 \angle 63.6^\circ}{5.336 \angle 63.6^\circ} \quad \checkmark$$

$$V_A - V_B = (7.11, -9.67) = 12 \angle -54^\circ$$

$$Z_{TH} = Z_C \parallel R + Z_L \parallel R = \frac{988 \Omega - j 8.89 \Omega}{R} = \frac{988 \angle -51^\circ}{R}$$

$$I = \frac{V_{TH}}{Z_{TH} + R} = \frac{(7.11, -9.67)}{(1.988, -8.89)} = 18 \text{ mA}$$

$$= (3.69 - 4.85) \text{ mA} = \boxed{6.04 \text{ mA} \angle -53^\circ}$$

(41) Take the following data
 3 octaves $\left\{ \begin{array}{l} 1 \text{ kHz} \\ 0.1 \text{ kHz} \end{array} \right\} \rightarrow 0 \text{ dB} \quad \left\{ \begin{array}{l} 0.04 \text{ mA} \angle -36^\circ \\ 0.016 \text{ mA} \angle -35.9 \text{ dB} \end{array} \right\} \rightarrow 0 \text{ dB}$


$$\frac{q_1}{q_2} = A \frac{f_1^B}{f_2^B} \Rightarrow \frac{q_1}{q_2} = \left(\frac{f_1}{f_2} \right)^B$$

$$\log \left(\frac{q_1}{q_2} \right) = B \log \left(\frac{f_1}{f_2} \right)$$

$$\log \left(\frac{0.016}{0.04} \right) = B \approx 2$$

$$1.99 = \frac{\log \left(\frac{0.016}{0.04} \right)}{\log \left(\frac{1}{8} \right)} = \frac{\log \left(\frac{0.016}{0.04} \right)}{\log \left(\frac{1}{8} \right)}$$
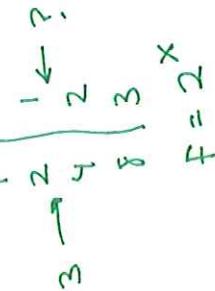
$$(50) \quad \frac{+ve}{-ve} \quad f = 2^x \quad 3 = 2^x \Rightarrow x = \frac{\log 3}{\log 2} = 1.59 \text{ octaves}$$



$$\text{Sequence: } V_{in} = A(1 \sin(\omega t) + \frac{1}{3} \sin(3\omega t))$$

$$V_{out} = B(1 \sin(\omega t) + .01 \sin(3\omega t))$$

$$\text{attenuation} = \frac{B}{A} = \frac{B}{A(1/\sqrt{3})} = \frac{B}{A} \cdot \sqrt{3}$$

$$\Delta dB = 20 \log_{10} \left(\frac{B/A}{1/\sqrt{3}} \right)$$

$$\Delta dB = 20 \log_{10} (B/A)$$

$$\Delta dB = 20 \left[\log_{10} (B/A) - \log \left(\frac{B/A}{\sqrt{3}} \right) \right]$$

$$= 20 \left[1.08 \left\{ \frac{B/A}{B/A \cdot 10^{0.5}} \right\} \right]$$

$$= 20 \log_{10} \left(\frac{3}{100} \right)$$

$$\# \text{ oct} = 1.59$$

$$\Rightarrow \frac{\Delta dB}{\# \text{ oct}} = \frac{20 \log_{10} \left(\frac{3}{100} \right)}{1.59} = -19.2 \frac{\text{dB}}{\text{oct}}$$

$$\text{Triangle: } V_{in} = A \left(1 \sin(\omega t) - \frac{1}{9} \sin(3\omega t) \right)$$


$$V_{out} = B \left(1 \sin(\omega t) - .01 \sin(3\omega t) \right)$$

$$\text{attenuation} = \frac{B}{A} = \frac{.01 \cdot B}{A} = \frac{B}{A} \cdot \frac{100}{9}$$

$$\Delta dB = 20 \log_{10} \left(\frac{9}{100} \right)$$

$$\Delta dB = \frac{20 \log_{10} \left(\frac{9}{100} \right)}{1.59} = -13.2 \frac{\text{dB}}{\text{oct}}$$

Diagram of a circuit for question 1. It shows a bridge rectifier connected to a 3.3V DC source. The output of the rectifier is connected to a Zener diode (ZD) and a voltage-controlled voltage source (VSV). The VSV has a gain of 1.5. The output of the VSV is connected to a load of 3.3 ohms. The circuit also includes a 3.3335 ohm resistor and a 3.3 ohm resistor.

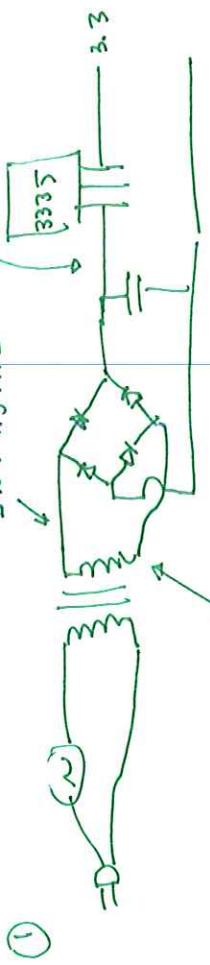

$$V_{rms} = \frac{V_0}{\sqrt{2}} = \frac{6.5}{\sqrt{2}} = \frac{4.60\text{ V}}{\sqrt{2}}$$

$$120 \cdot T = (6.5)(.25) \rightarrow T = \frac{6.5 \cdot .25}{120} = .0135 \text{ A}$$

$$\text{Tr} \gamma = \frac{z_L - z_C}{z_L + z_C} = \frac{(62.83)(63.66)}{(62.83 - 63.66)} = -0.312$$

$$Z_C = \frac{1}{j\omega C} = -j 63.66 \Omega$$

$$Z_L || Z_C + R = 10^3 + j4.82 \times 10^3 \rightarrow \text{in } \text{KCL} (1, 4.82) =$$

$$\pi = \sqrt{2.03m^4} \angle -78.3^\circ$$

$$V_{out} = \frac{Z_L || Z_C}{Z_L + Z_C} V_{in} = \frac{(0.4 \cdot 82)}{(1 + 82)} 10 = 0.79 V < 11.70$$

279 / 11.70

$$\frac{V_{out}}{V} = \frac{g \cdot F_{av}}{15 \cdot m} \rightarrow \text{longer than total!}$$

15

$$R_{\text{ext}} + \frac{100}{S} = R_{\text{ext}} + 100 = \frac{100 \cdot 6}{100+6} = \frac{100 \cdot 6}{106} = 5.6 \Omega$$

$$P = I^2 R = \left(\frac{6}{2}\right)^2 \cdot 10 = 180 \text{ W}$$

Should read $\sqrt{3 - 4i} = \sqrt{7} e^{i\pi/6}$

Look at phase difference
 $V_2 = R(3 - 4i)$ should LAG
 $b = +\tan\left(\frac{4i}{3}\right) = 53^\circ$

二

