
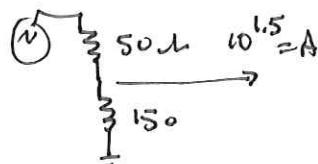


Problems: 38-40, 42-46

38 a)

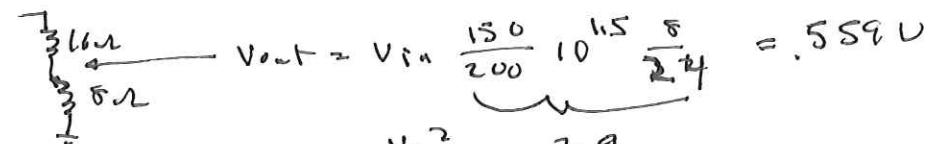


$$V_{in\text{ rms}} = \frac{.2}{2\sqrt{2}} V = .0707 V$$



$$\text{Power} = \frac{V_{out}^2}{R}$$

$$= \frac{(559)^2}{8} = 39 \text{ mW}$$


b)

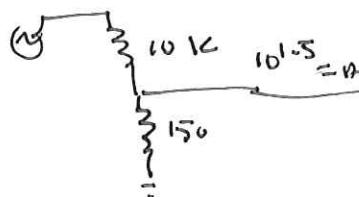

$$V_{out} = V_{in} \frac{150}{10k} 10^{1.5} \frac{5}{24} = .0112 V$$

$$\text{Power} = \frac{V_{out}^2}{R} = 15.2 \mu W$$


c)

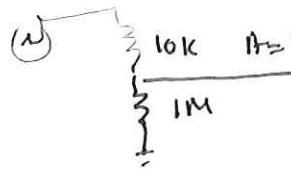

$$V_{out} = V_{in} \frac{1M}{1M+150} \cdot \frac{8}{9} = 62.9 \mu V$$

$$\text{Power} = \frac{V_{out}^2}{R} = 494 \mu W$$

d)

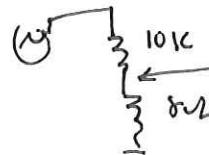

$$V_{out} = V_{in} \frac{8}{10,000} = 56.5 \mu V$$

e)

$$\text{Power} = \frac{V_{out}^2}{R} = 400 \text{ pW}$$

39 a)  $\left( \frac{R_{in}}{R_{in}+R_{out}} \right)^2 A^3$

b) high freq  $\Rightarrow C_{ap} = L_{int}$   $g_{out} = \left( \frac{R_{in}}{R_{in}+R_{out}} \right) A^2$

in general:

5

$$\frac{R_{out}}{R_{in}} = \frac{R_{in}}{R_{in}+R_{out}} = \frac{\frac{1000}{1100 - i_c}}{\frac{1000}{1100 - i_c} + \frac{i_c}{w_c}} \xrightarrow{\text{max}} \frac{1000}{\sqrt{(1100)^2 + (w_c)^2}}$$

at 3dB terms equal 1.



c) at low freq  $Z_C \rightarrow \infty \Rightarrow g_{out} = A^2$

$$1100 = \frac{1}{w_c}$$

$$f = \frac{1}{2\pi \cdot 1100 \cdot 10^{-7}}$$

$$\frac{1}{200 \text{ pF}} = \frac{\frac{1}{w_c}}{100 \cdot 200 + 10^{-12}} \xrightarrow{i_F=1 \Rightarrow \sqrt{2}} = 1.45 \text{ kHz}$$
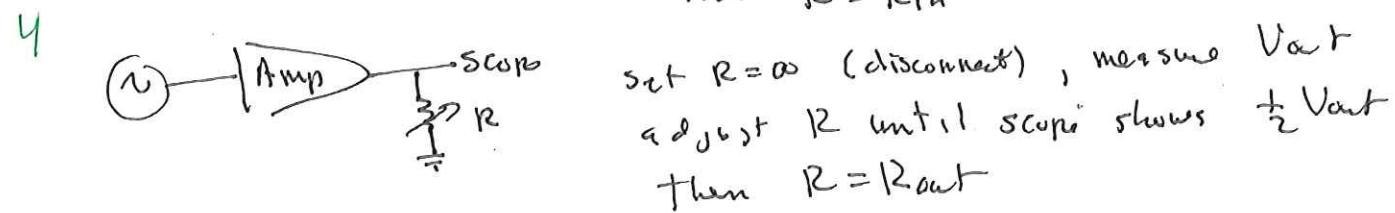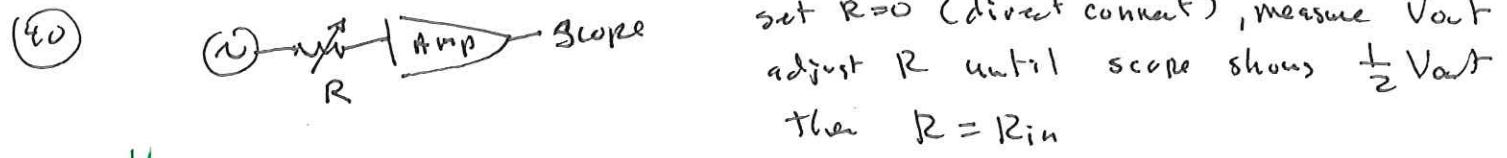
$$f = \frac{1}{2\pi w_c} = \frac{1}{2\pi \cdot 100 \cdot 200 + 10^{-12}} = 7.96 \text{ MHz}$$





(42)  $\text{gain} = -5 \text{ so } V_{\text{out}} = (-5)(1.5) = -7.5V$

3  $V = \text{zero}$  (golden rule)

$I = \frac{1.5 \text{ V}}{10 \text{ k}\Omega} = 15 \text{ mA}$

(43) a) inverting:  $\text{gain} = -\frac{25}{5} = -5 \quad Z_{in} = 5 \text{ k}\Omega$

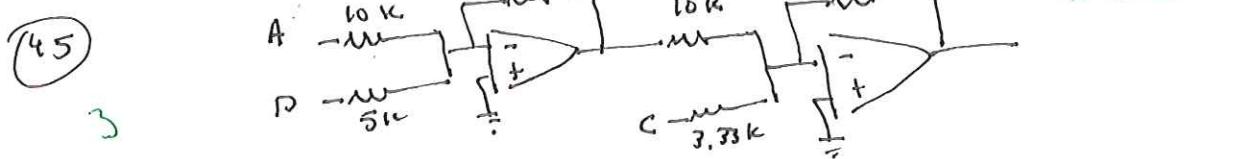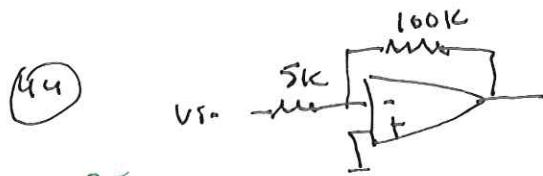b) non invert:  $\text{gain} = 1 + \frac{25}{5} = 6 \quad Z_{in} = \infty$



(46) a)  $\frac{6 \text{ V}}{0.1 \text{ V}} = 60 \quad \text{b) } \frac{3 \text{ mV}}{10 \text{ V}} = 3 \times 10^{-4}$

4 c)  $\frac{60}{3 \times 10^{-4}} = 200,000 \Rightarrow 20 \log_{10}(200,000) = 106 \text{ dB}$