

problems.pdf: 65, 66, 71a, 75, 68

65: $I_b = \frac{20 - 0.6}{1M} = 19.4 \mu A$

$I_c = \beta I_b = 2.91 mA \Rightarrow r_e = \frac{25}{I_c} = 8.6 \Omega$
 $V_{out} = 20 - \frac{3.3}{R_c} \cdot I_c = 10.4 V$

$A_v = \frac{-R_c}{r_e} = \frac{-3300}{8.6} = -384$

$Z_{in} = 1M \parallel (\beta + 1)r_e = (\beta + 1)r_e = (151)(8.6) = 1.3 k\Omega$

7 $C_{in} = \frac{10}{\omega Z_{in}} = \frac{10}{2\pi \cdot 60 \cdot 1300} = 20 \mu F$

$C_{out} = \frac{1}{\omega R_c} = \frac{1}{2\pi \cdot 60 \cdot 3300} = .8 \mu F$

66: $V_B = \frac{R_{B2}}{R_{B1} + R_{B2}} V_{CC} = \frac{2}{10} \cdot 20 = 4V \rightarrow V_E = 3.4V \rightarrow I_c = \frac{3.4V}{330\Omega} = 10.3 mA$

$V_C = V_{CC} - R_c I_c = 20 - 1k(10.3 mA) = 9.7V$

if $\beta < \infty$ then $V_B \downarrow \Rightarrow V_E \downarrow \Rightarrow I_c \downarrow \Rightarrow V_C \uparrow$

10 if $V_C = 10.7V \Rightarrow I_c = \frac{9.3V}{1k} = 9.3 mA \Rightarrow V_E = 330 \cdot I_c = 3.07V$

$V_B = 3.67V$ (ie droop = .33V)

8k + 2k: $4V$ $R_{TH} = 1.6k$ $R_{TH} \cdot I_B \Rightarrow I_B = \frac{.33V}{1.6k} = .206 mA$

$\beta = \frac{9.3 mA}{.206 mA} = 45$




$I_B = .0206 mA$ $\beta = 450$

71a



7

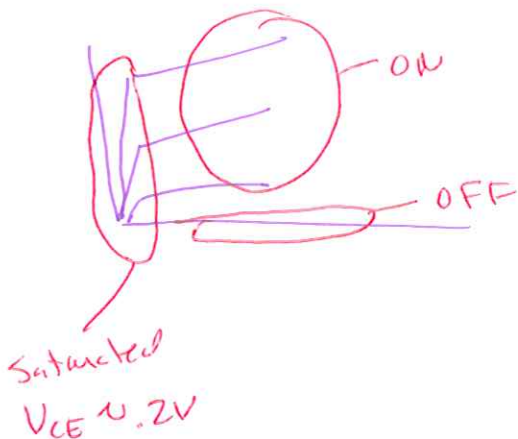

75) $V_{CC} = 20V$ $V_B = 2V$ $I_B = 20\mu A$ $\beta R_E = 70K$ $I_C = 2mA$

(A) $R_{B1} \parallel R_{B2} = 7K \rightarrow \frac{V_B}{V_{CC}} = \frac{2}{20} = \frac{R_{B1} \parallel R_{B2}}{R_{B1}} = \frac{7K}{R_{B1}} \Rightarrow R_{B1} = 70K$

$R_{B2} : \frac{1}{R_{B2}} = \frac{1}{R_{B1} \parallel R_{B2}} - \frac{1}{R_{B1}} = \frac{1}{7K} - \frac{1}{70K} \Rightarrow R_{B2} = 7.77K$

droop = $(R_{B1} \parallel R_{B2}) I_B = (7K)(20\mu A) = .14V$

so $V_{out} = 2 - .14 = 1.86V \Rightarrow V_E = 1.26$

$\frac{\Delta V_E}{V_E} = \frac{.14}{1.4} = 10\%$

$40\mu A \rightarrow .28V \rightarrow \frac{.28}{1.4} = 20\%$

(B) $R_{B2} = \frac{2V}{9 \times 20\mu A} = 11.1K\Omega$ } $R_{B1} \parallel R_{B2} = 9.89K$
 $R_{B1} = \frac{18V}{10 \times 20\mu A} = 90K\Omega$

$V_{out} = \frac{11.1}{101.1} 20 = 2.196$ ← "droop" up
 $\frac{\Delta V_E}{V_E} = \frac{.2}{1.4} = 14\%$

droop = $\frac{(9.89K)(40\mu A) = .396}{1.800}$ ← droop ~~the~~ below: 14%

Note: (B) gives high input impedance but also more sensitive to β changes. However the changes are balanced i.e. with (A) V_B is always smaller than "design" value as with (B) if $\beta \uparrow$ V_B above design } in some sense
if $\beta \downarrow$ V_B below design } this gives more room for error.

68) $A_v = -10 = -\frac{R_c}{R_e} \Rightarrow R_e = 500 \Omega$

$I_c = \frac{V_{cc}/2}{R_c + R_e} = \frac{10V}{5.5k} = 1.82 \text{ mA} \Rightarrow r_e = \frac{25}{1.82} = 13.8$
↑
not with
corrected R_e

↳ Remark: actual values might be $5.1k \approx 510 \Omega \Rightarrow I_c = 1.78$

$V_E = (1.82 \text{ mA})(500) = .91 \text{ V}$

$r_e = 14 \Omega$

$V_B = V_E \times 6 = \underline{1.51 \text{ V}}$

$I_B = \frac{1.82 \text{ mA}}{150} = \underline{12 \mu\text{A}}$

Method 1 $(\beta+1)(r_e + R_E) = 150 \cdot 500 = 75k \rightarrow R_{B1} \parallel R_{B2} = 7.5k$

$\frac{V_B}{V_{cc}} = \frac{1.51}{20} = \frac{R_{B1} \parallel R_{B2}}{R_{B1}} \Rightarrow R_{B1} = \frac{7.5k}{1.51/20} = 99k$

$R_{B2}: \frac{1}{R_{B2}} = \frac{1}{R_{B1} \parallel R_{B2}} - \frac{1}{R_{B1}} \Rightarrow R_{B2} = 8.1k$

$Z_{in} = R_{B1} \parallel R_{B2} \parallel (\beta+1)(r_e + R_E) = 6.8k$
↑ 99 ↑ 8.1 75k
~~drop = .276V~~ $I_B = \frac{.274}{7.5k} = 36.8 \mu\text{A}$

if $V_E = .7 (0.91) = .637 \Rightarrow V_B = 1.237$

whereas voltage divider zero current output = $\frac{8.1}{107.1} \cdot 20 = 1.513$

$I_c = \frac{.637V}{.5k} = 1.27 \text{ mA}$ $\beta = \frac{1.27 \text{ mA}}{.0368} = \boxed{35}$

Method 2

$R_{B2} = \frac{1.51V}{9 \times 12 \mu\text{A}} = 14k$

$R_{B1} = \frac{20 - 1.51}{10 \times 12 \mu\text{A}} = 154k$

$R_{B1} \parallel R_{B2} = 12.8k$

$V_T = \frac{14}{168} \cdot 20 = 1.667 \text{ V}$

if $V_B \text{ actual} = 1.237$ drop = $1.667 - 1.237 = .430 \text{ V}$
 $= (R_{B1} \parallel R_{B2}) I_B$ } $I_B = 33.6 \mu\text{A}$

$\beta = \frac{1.27 \text{ mA}}{.0336 \text{ mA}} = \boxed{38}$

it is highly unlikely that a transistor spec "typical" $\beta = 150$ would in fact have $\beta = 35$ so these circuits should be OK for all such transistors

68 caps — $C_{out} = \frac{1}{\omega R_c} = \frac{1}{2\pi \cdot 20 \cdot 5000} = 1.6 \mu F$

$$C_{in} = \frac{10}{\omega Z_{in}} = \frac{10}{2\pi \cdot 20 \cdot 6800} = 12 \mu F$$

Method 1: 6.8k

method 2: $\frac{1}{14} + \frac{1}{15k} + \frac{1}{75} \Rightarrow 11k$

$$\Rightarrow \frac{10}{2\pi \cdot 20 \cdot 11,000} = 7.2 \mu F$$