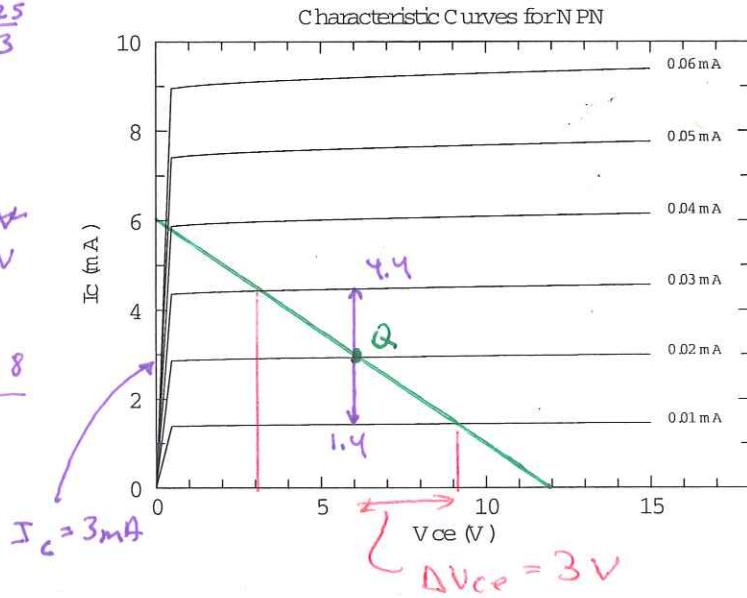


72. Consider the below characteristic curves of an npn bipolar transistor. Calculate $h_{fe} = \beta$. Assume the npn transistor is part of a common emitter amplifier with a supply voltage of 12 V. Directly on the below plot, draw in the load line for a 2 k Ω collector resistor, and mark a nice operating point Q . At Q , what is the change in the collector voltage ΔV_{CE} for a change in the base current $\Delta I_B = .01$ mA? Calculate h_{ie} using your operating point's base current. What change in the base voltage ΔV_{BE} will accompany the change in the base current $\Delta I_B = .01$ mA? Calculate the ac voltage gain: $\Delta V_{CE}/\Delta V_{BE}$. At your operating point, how much power is dissipated in the transistor?

$$h_{re} = (\beta + 1) r_e = 151 \frac{25}{3} \approx 1.26 \text{ k}\Omega$$

$$\Delta I_B h_{ie} = \Delta V_B \\ (.01)(1.26 \text{ k}\Omega) \approx 1.26 \text{ mV} \\ \therefore 0.126 \text{ V}$$

$$\text{gain} = \frac{3}{.0126} = 23.8$$



$$h = \frac{4.4 - 1.4 \text{ mA}}{.02 \text{ mA}} \\ = 150$$

$$P_{\text{diss}} = (6 \text{ V})(3 \text{ mA}) \\ = 18 \text{ mW}$$

- 74
- A source follower
 - B common emitter amp
 - C differential Amp
 - D emitter follower

- E current mirror
- F push-pull follower
- G common source amp
- H common emitter amp

- I FET current source
- J BJT current source

Problems.pdf: 67, 72, 74

$$67: Z_{out} = 5k \Rightarrow R_C = 5k; \text{ by } \frac{V_{CC}}{3} \Rightarrow R_E1 = 5k$$

$$G_m = -20 = -\frac{R_C}{R_{E2} + r_e} \Rightarrow R_{E2} + r_e = \frac{5k}{20} = 250\Omega$$

$$\text{Select } V_{CC} = 15V \text{ so } V_E = 5V \text{ so } I_E = 1mA \text{ so } r_e = 250\Omega$$

$$I_B \approx \frac{1}{600} 1mA = .01mA$$

$$R_{E2} = 220\Omega$$

\uparrow
standard value

$$V_B = \frac{V_{CC}}{3} + .6 = 5.6V$$

$$HH: R_{B1} \parallel R_{B2} = \frac{1}{10} (B+1) (r_e + R_E1) = 10 \cdot 5k = 50k$$

$$\frac{V_B}{V_{CC}} = \frac{R_{B1} \parallel R_{B2}}{R_{B1}} \Rightarrow R_{B1} = \frac{R_{B1} \parallel R_{B2}}{\frac{V_B}{V_{CC}}} = \frac{50}{5.6/15} = 134$$

$$\frac{1}{R_{B2}} = \frac{1}{R_{B1} \parallel R_{B2}} - \frac{1}{R_{B1}} = \frac{1}{50} - \frac{1}{134} \Rightarrow R_{B2} = 80k$$

$$\text{if } B = \infty \quad V_B = V_C \quad \frac{R_{B1}}{R_{B1} + R_{B2}} = 5.6 \quad (\text{as designed})$$

$$\text{if } B = 100 \rightarrow I_B = .01mA \quad \text{droop} = (R_{B1} \parallel R_{B2}) I_B = 50k \cdot .01mA = .5V$$

$$V_B = 5.6 - .5 = 5.1$$

$$\frac{\Delta V_E}{V_E} = \frac{.5}{5} = 10\%$$

$$TK: R_{B1} = \frac{V_{CC} - V_B}{10 \cdot I_B} = \frac{15 - 5.6}{.1mA} = 94k \quad \left. \begin{array}{l} \\ R_{B1} \parallel R_{B2} = 37k \end{array} \right\}$$

$$R_{B2} = \frac{V_B}{9 \cdot I_B} = \frac{5.6}{.09mA} = 62k$$

$S = 60$ (pure voltage divider)

$$\frac{6.2}{6.2 + 84} 12 = 5.96$$

$$\frac{\Delta V_E}{V_E} = \frac{.36}{5} = 7\%$$

$$\text{droop} = (37) (.01) = .37$$

$$C_{out} = \frac{1}{2\pi \cdot 1600 \cdot 5000} = .03\mu F \quad f_{min} = 1000Hz \quad 5.6 \text{ (as designed)}$$

$$Z_{in} (TK) = 37k \parallel \underbrace{(B+1) R_{E2}}_{24.8k} = 14.8k \leftarrow \text{slight miss}$$

$$Z_{in} (HH) = 50k \parallel (B+1) R_{E2} = 16.6 \approx 0k$$

$$C_{in} = \frac{10}{2\pi f \cdot 16.6 \cdot 10^3} = .01\mu F \quad C_E = \frac{10}{2\pi f \cdot 220} = 7.2\mu F$$