

$$V = IR + L \frac{dI}{dt} + \frac{I}{C}$$

$$0 = iR + L \dot{i} + \frac{I}{C}$$

$$0 = \ddot{i} + \frac{R}{L} \dot{i} + \frac{1}{LC} I$$

\uparrow 2β ω_0^2

$$0 = \ddot{i} + 2\beta \dot{i} + \omega_0^2 I$$

$$0 = r^2 + 2\beta r + \omega_0^2$$

$$r = \frac{-2\beta \pm \sqrt{(2\beta)^2 - 4\omega_0^2}}{2}$$

$$= -\beta \pm i \sqrt{\omega_0^2 - \beta^2}$$

ω'

$$I = A e^{-\beta t} e^{+i\omega' t}$$

$$+ B e^{-\beta t} e^{-i\omega' t}$$

$$= \underline{\underline{A e^{-\beta t} \cos(\omega' t + \phi)}}$$



$$"R" = i\omega L$$

$$"B" = \frac{1}{i\omega C}$$

$$R = R$$

$$V_0 = |V| e^{i\phi}$$

$$\textcircled{\sim} \omega = 2\pi f$$

$$\textcircled{\int \Delta}$$

$$\uparrow e^{i\omega t}$$

$$\underline{\underline{\cos(\omega t + \phi)}}$$

$$V = V_0 e^{i\omega t}$$

\sim $V_{rms} = \frac{V_0}{\sqrt{2}}$

$$V = RI + L \frac{dI}{dt} + \frac{\int I dt}{C}$$

$$I = I_0 e^{i\omega t}$$

\downarrow
 $i\omega L I$

\downarrow
 $\frac{1}{i\omega C} I$

$$V = (R + i\omega L + \frac{1}{i\omega C}) I_0 e^{i\omega t}$$


$e^{i\pi/2}$ $e^{-2\pi/2}$

$$V_0 = (R + i\omega L + \frac{1}{i\omega C}) I_0$$

$$Z = |Z| e^{i\phi}$$

$$|V_0| = |Z| |I_0|$$

$$V = |Z| I_0 e^{i(\omega t + \phi)}$$

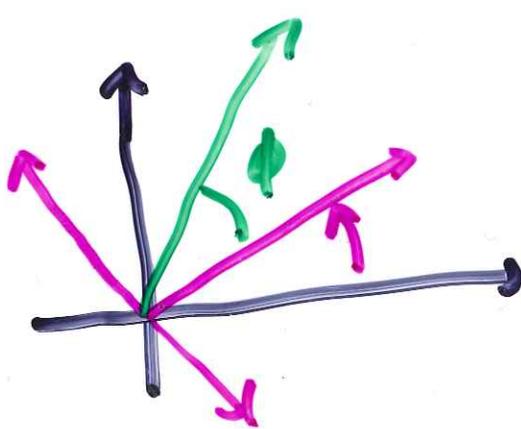

$e^{i\omega t}$

$$\boxed{\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}}$$





$$\leftarrow \frac{1}{i\omega C}$$

$$i\omega L$$

$$C = C_1 + C_2$$

$$\frac{1}{Y_{i\omega C}} = \frac{1}{Y_{i\omega C_1}} + \frac{1}{Y_{i\omega C_2}}$$


$$C = C_1 + C_2$$

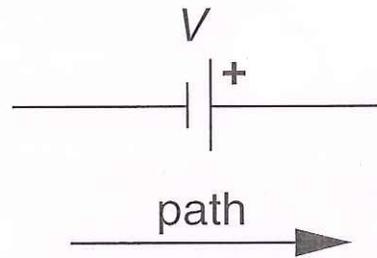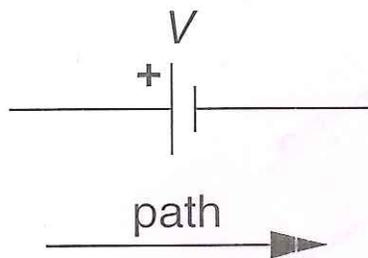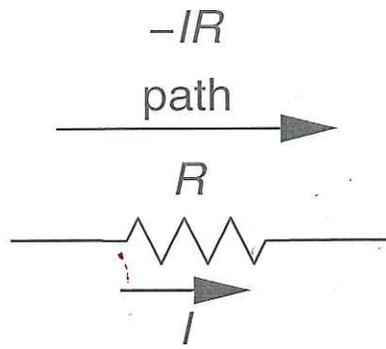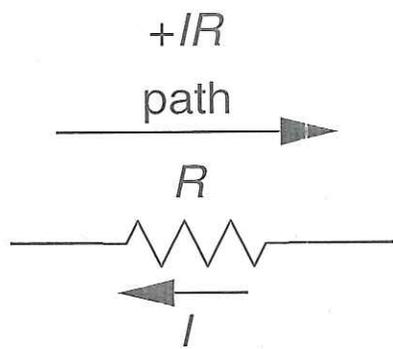


mesh
 \uparrow
Loop

node voltage

$+R_2(I_2 + I_1)$

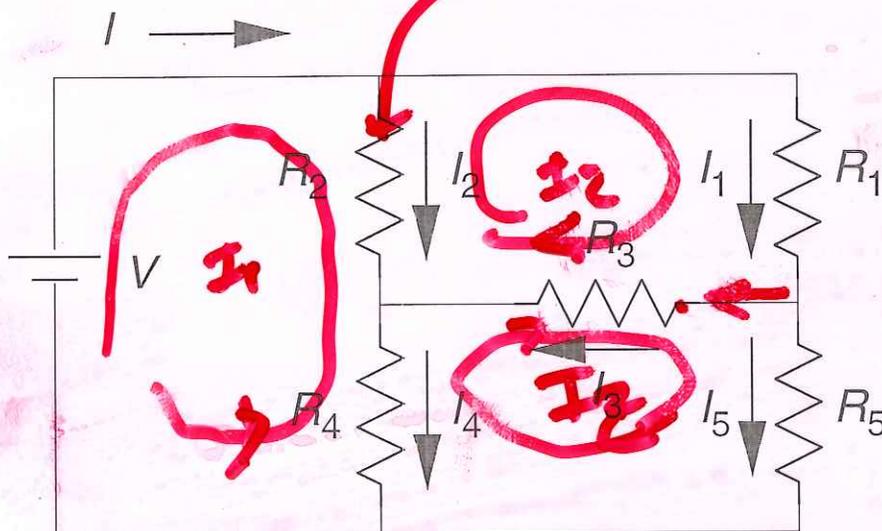

$R_3(I_2 + I_3)$

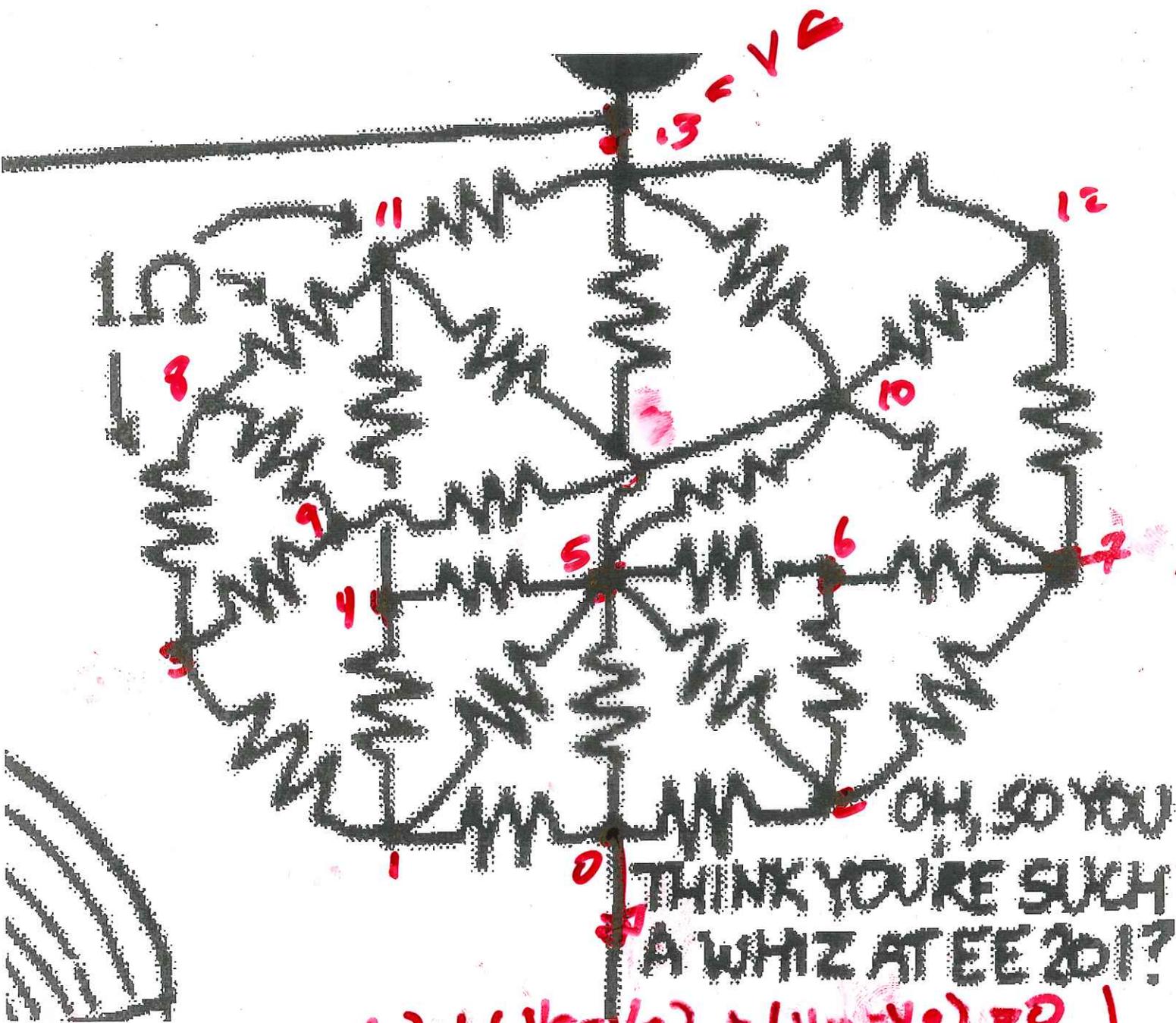

$$\begin{aligned}
 (V_3 - V_a) + (V_5 - V_a) + (V_{10} - V_a) &= 0 \\
 (0 - V_5) + (V_1 - V_5) + (V_4 - V_5) + (V_{11} - V_5) \\
 + (V_{13} - V_5) + (V_{12} - V_5) + (V_6 - V_5) & \\
 R = \frac{V}{I} = \frac{(V_1 - 0) + (V_2 - 0) + (V_5 - 0) + (V_2 - 0)}{I} &= 0
 \end{aligned}$$

