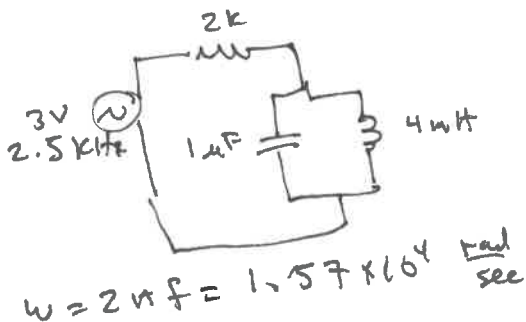


32)



$$Z_{eq} = R + \frac{1}{i\omega C + \frac{1}{i\omega L}}$$

$$= R + \frac{i}{\frac{1}{\omega L} - \omega C} \quad \left. \begin{matrix} \\ \end{matrix} \right\} 2.075 \times 10^{-4}$$

$$= (2 + i4.819) \text{ k}\Omega$$

$$= 5217 \angle 67.5^\circ$$

$$V = \frac{i4.819}{2 + i4.819} \cdot 3 = (.853 + i.354) \text{ V}$$

$$= (.924 \angle 22.5^\circ) \text{ V} = 2.77 \text{ V} \angle 22.5^\circ$$

$$I = \frac{V}{\omega L} = \frac{2.77}{\omega L} = \frac{2.77}{49.1} = 5.64 \text{ mA}$$

24) Mathematica would be a faster solution - but lets do this "by hand"

$$\frac{1}{Z_T} = \frac{1}{i\omega C + R} + \frac{1}{i\omega L + R} = \frac{R + \frac{i}{\omega C}}{R^2 + (\frac{1}{\omega C})^2} + \frac{R - i\omega L}{R^2 + (\omega L)^2}$$

$$= \frac{(R + \frac{i}{\omega C})(R^2 + (\omega L)^2) + (R - i\omega L)(R^2 + (\frac{1}{\omega C})^2)}{(R^2 + (\frac{1}{\omega C})^2)(R^2 + (\omega L)^2)}$$

start by looking at imaginary part of numerator -

$$\frac{i}{\omega C} (R^2 + (\omega L)^2) - i\omega L (R^2 + (\frac{1}{\omega C})^2) = i \left[ R^2 (\frac{1}{\omega C} - \omega L) + \frac{1}{C} (\omega L - \frac{1}{\omega C}) \right]$$

$$= i \left[ (R^2 - \frac{1}{C}) (\frac{1}{\omega C} - \omega L) \right] \quad \text{so } \dots = 0 \text{ if } R^2 = 1/C$$


now look at real part:  $R \left[ 2R^2 + (\omega L)^2 + (\frac{1}{\omega C})^2 \right]$

compare to denominator:  $R^2 \left[ R + \frac{1}{R} \left( \frac{1}{(\omega L)^2} \right) \left[ R + \frac{(\omega L)^2}{R} \right] \right]$

$$= R^2 \left[ R^2 + \frac{1}{(\omega C)^2} + (\omega L)^2 + \frac{(\omega C)^2}{R^2} \right]$$

so:  $\frac{1}{Z_T} = \frac{R}{R^2} \Rightarrow Z_T = R \checkmark$

#32

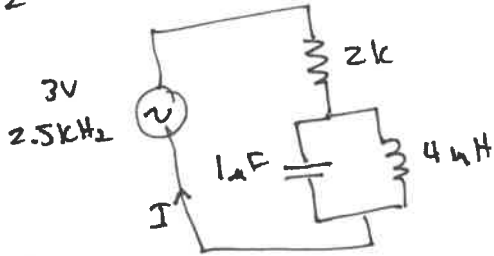

$$\omega = 2\pi \cdot 2.5 \times 10^3 = 1.57 \times 10^4 \text{ rad/sec}$$

$$X_L = \omega L = 62.8 \Omega$$

$$X_C = \frac{1}{\omega C} = 63.7 \Omega$$

$$Z_{eq} = R + \frac{1}{\frac{1}{i\omega C} + i\omega L}$$

$$= R + \frac{i}{\frac{1}{\omega C} - \omega L}$$

$$= 2000 + i 4819 \Omega$$

$$I = \frac{3V}{2000 + i 4819}$$

$$= (.220 - i .531) \times 10^{-3} A$$

$$= 5.75 \times 10^{-4} A \angle -67^\circ$$

voltage leads

voltage across



From  $Z = i 4819$  &  $I = 5.75 \times 10^{-4} A$   
 $V = 4819 \cdot 5.75 \times 10^{-4} = 2.77 V$

current thru



$$= \frac{V}{\omega L} = \frac{2.77}{62.8} = 44.1 \text{ mA}$$

(Complex values not requested or wanted)