

$$I = \frac{\mathcal{E}}{R} (1 - e^{-t/\tau}) \quad \tau = \frac{L}{R}$$

$$= \frac{5}{3} (1 - e^{-t/2/3}) \quad = \frac{2}{3} \text{ sec}$$


@ $t = .35 \quad I = .604 \text{ A}$
 $t = 1 \text{ s} \quad = 1.29 \text{ A}$
 $t = 4 \text{ s} \quad = 1.66 \text{ A}$

$$\frac{dI}{dt} = 1.59 \text{ A/s}$$

$$= .558 \text{ A/s}$$

$$= 6.2 \text{ mA/s}$$
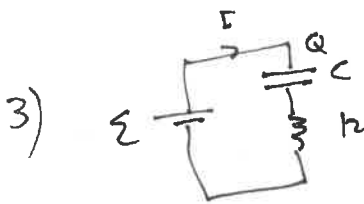
$$\frac{dI}{dt} = \frac{\mathcal{E}}{R} \frac{1}{\tau} e^{-t/\tau} = \frac{\mathcal{E}}{L} e^{-t/\tau}$$




$$\mathcal{E} = \frac{Q}{C} + R \frac{dQ}{dt}$$

homo soluti: $Q = Q_0 e^{-t/RC}$
 particular soluti: $Q = \mathcal{E} C$

B.C. $Q = 0$ @ $t = 0$
 $Q = \mathcal{E} C (1 - e^{-t/RC})$

#31

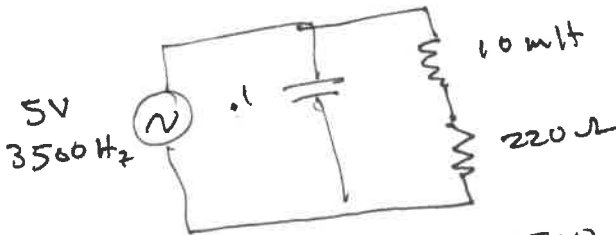

$$\omega = 2\pi f = 2\pi \cdot 3500$$

For part b) the capacitor does not matter

$$I = \frac{5}{R + i\omega L} = .01137 - .01136 i$$

$$\tau .01607 \text{ A} = A$$

$$V_R = 220 \cdot I = 3.54 \text{ V} = V_2$$

$$V_L = \omega L I = 3.54 \text{ V} = V_1$$

$$\frac{1}{Z} = i\omega C + \frac{1}{220 + i\omega L}$$

↳ mathematic

$$Z = 439.4 + 14.2 i$$

$$I = \frac{5}{Z} = .01137 - .000368 i$$

current less voltage
 $= 11.4 \text{ mA} \angle -1.9^\circ$