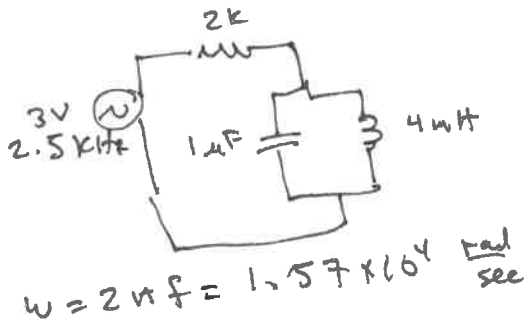


32)



$\omega = 2\pi f = 1.57 \times 10^4 \frac{\text{rad}}{\text{sec}}$

$$Z_{\text{eq}} = R + \frac{1}{i\omega C + \frac{1}{i\omega L}}$$

$$= R + \frac{i}{\frac{1}{\omega L} - \omega C} \quad 2.075 \times 10^{-4}$$

$$= (2 + i4.819) \text{ k}\Omega$$

$$= 5217 \angle 67.5^\circ$$

$$V = \frac{i4.819}{2 + i4.819} \cdot 3 = (.853 + i.354) 3$$

↑ volt lead

$$= (.924 \angle 22.5^\circ) 3 = 2.77 \text{ V} \angle 22.5^\circ$$

$$I = \frac{V}{\omega L} = \frac{2.77}{\omega L} = 17.6 \text{ mA}$$

24) Mathematica would be a faster solution - but lets do this "by hand"

$$\frac{1}{Z_T} = \frac{1}{i\omega C + R} + \frac{1}{i\omega L + R} = \frac{R + \frac{i}{\omega C}}{R^2 + (\frac{1}{\omega C})^2} + \frac{R - i\omega L}{R^2 + (\omega L)^2}$$

$$= \frac{(R + \frac{i}{\omega C})(R^2 + (\omega L)^2) + (R - i\omega L)(R^2 + (\frac{1}{\omega C})^2)}{(R^2 + (\frac{1}{\omega C})^2)(R^2 + (\omega L)^2)}$$

start by looking at imaginary part of numerator -

$$\frac{i}{\omega C} (R^2 + (\omega L)^2) - i\omega L (R^2 + (\frac{1}{\omega C})^2) = i \left[R^2 (\frac{1}{\omega C} - \omega L) + \frac{L}{C} (\omega L - \frac{1}{\omega C}) \right]$$

$$= i \left[(R^2 - \frac{L}{C}) (\frac{1}{\omega C} - \omega L) \right] \text{ so } \dots = 0 \text{ if } R^2 = \frac{L}{C}$$

now look at real part: $R [2R^2 + (\omega L)^2 + (\frac{1}{\omega C})^2]$

compare to denominator: $R^2 [R + \frac{1}{R} (\frac{1}{\omega C})^2] [R + \frac{(\omega L)^2}{R}]$

$$= R^2 \left[R^2 + \frac{1}{(\omega C)^2} + (\omega L)^2 + \frac{(\omega C)^2}{R^2} \right]$$

so: $\frac{1}{Z_T} = \frac{R}{R^2} \Rightarrow Z_T = R \checkmark$